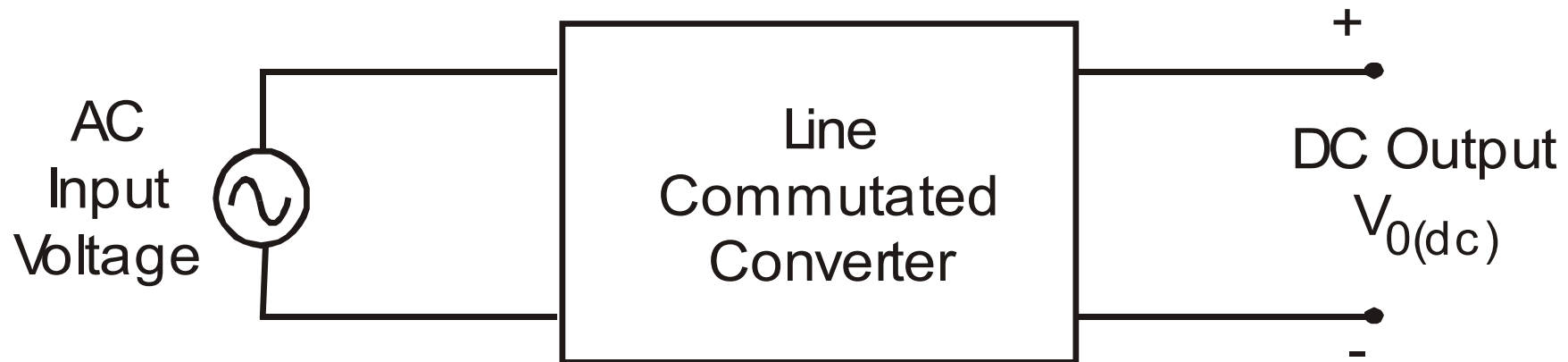




# Controlled Rectifiers

*(Line Commutated AC to DC  
converters)*



- Type of input: Fixed voltage, fixed frequency ac power supply.
- Type of output: Variable dc output voltage
- Type of commutation: Natural / AC line commutation



# Different types of Line Commutated Converters

- AC to DC Converters (Phase controlled rectifiers)
- AC to AC converters (AC voltage controllers)
- AC to AC converters (Cyclo converters) at low output frequency.



# Differences Between Diode Rectifiers & Phase Controlled Rectifiers





- The diode rectifiers are referred to as uncontrolled rectifiers .
- The diode rectifiers give a fixed dc output voltage .
- Each diode conducts for one half cycle.
- Diode conduction angle =  $180^0$  or  $\pi$  radians.
- We can not control the dc output voltage or the average dc load current in a diode rectifier circuit.



Single phase half wave diode rectifier gives an

$$\text{Average dc output voltage } V_{O(dc)} = \frac{V_m}{\pi}$$

Single phase full wave diode rectifier gives an

$$\text{Average dc output voltage } V_{O(dc)} = \frac{2V_m}{\pi}$$



# Applications of Phase Controlled Rectifiers

- DC motor control in steel mills, paper and textile mills employing dc motor drives.
- AC fed traction system using dc traction motor.
- Electro-chemical and electro-metallurgical processes.
- Magnet power supplies.
- Portable hand tool drives.



# Classification of Phase Controlled Rectifiers

- Single Phase Controlled Rectifiers.
- Three Phase Controlled Rectifiers.





# Different types of Single Phase Controlled Rectifiers.

- Half wave controlled rectifiers.
- Full wave controlled rectifiers.
  - Using a center tapped transformer.
  - Full wave bridge circuit.
    - Semi converter.
    - Full converter.



# Different Types of Three Phase Controlled Rectifiers


- Half wave controlled rectifiers.
- Full wave controlled rectifiers.
  - Semi converter (half controlled bridge converter).
  - Full converter (fully controlled bridge converter).




# Principle of Phase Controlled Rectifier Operation


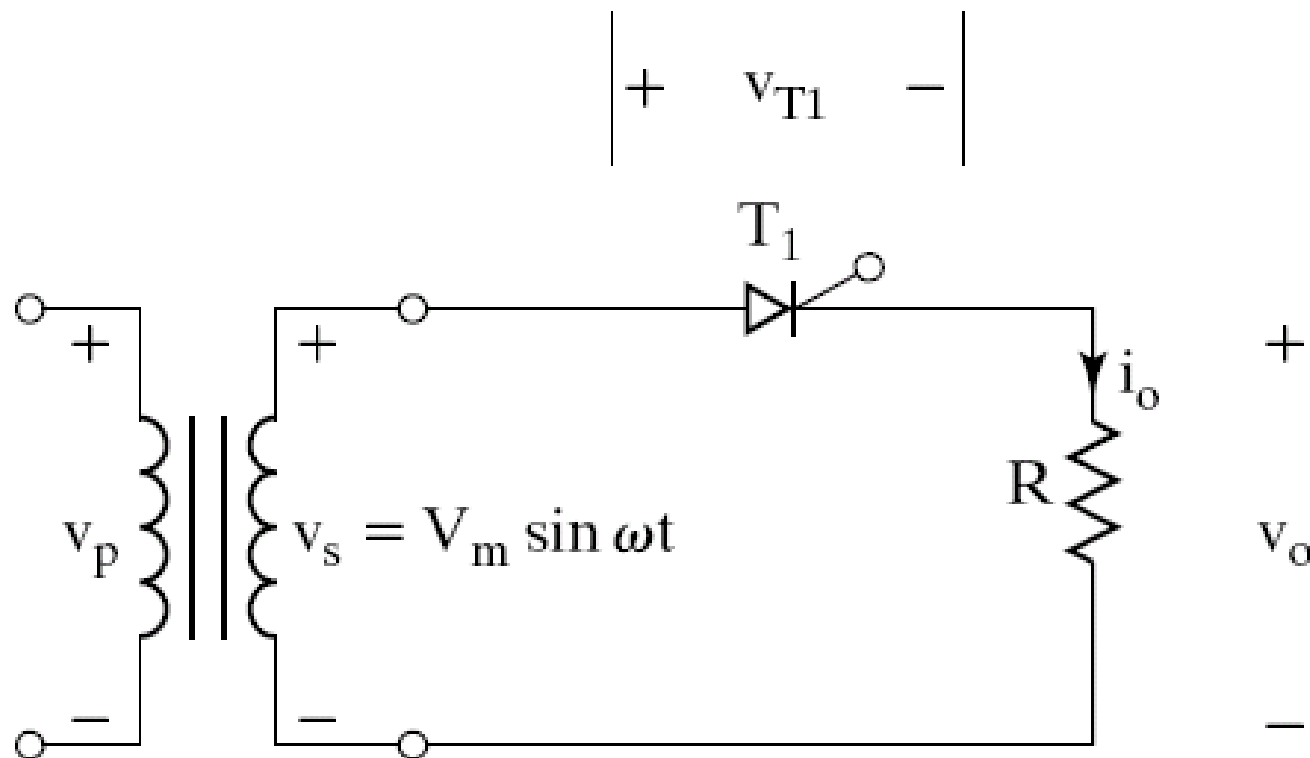
# Single Phase Half-Wave Thyristor Converter with a Resistive Load



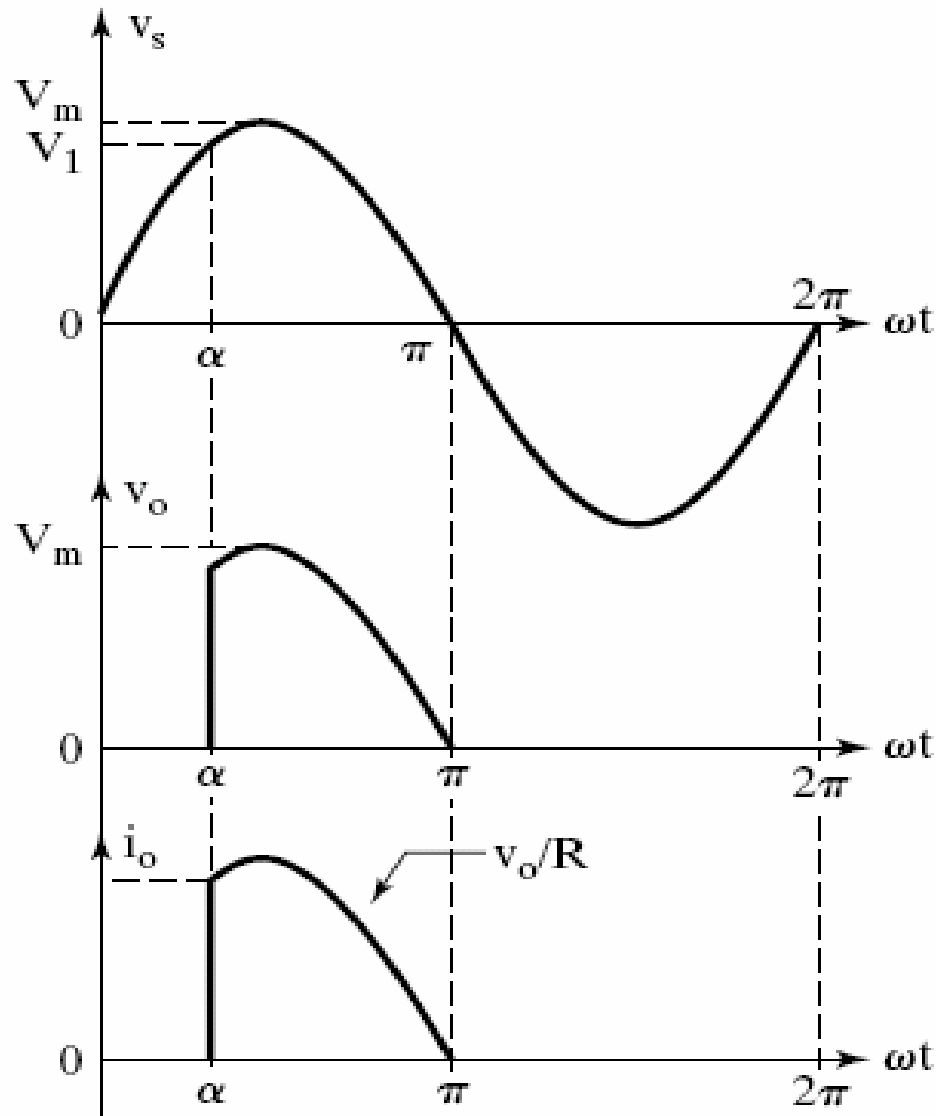


Supply Voltage

Output Voltage

Output (load)  
Current



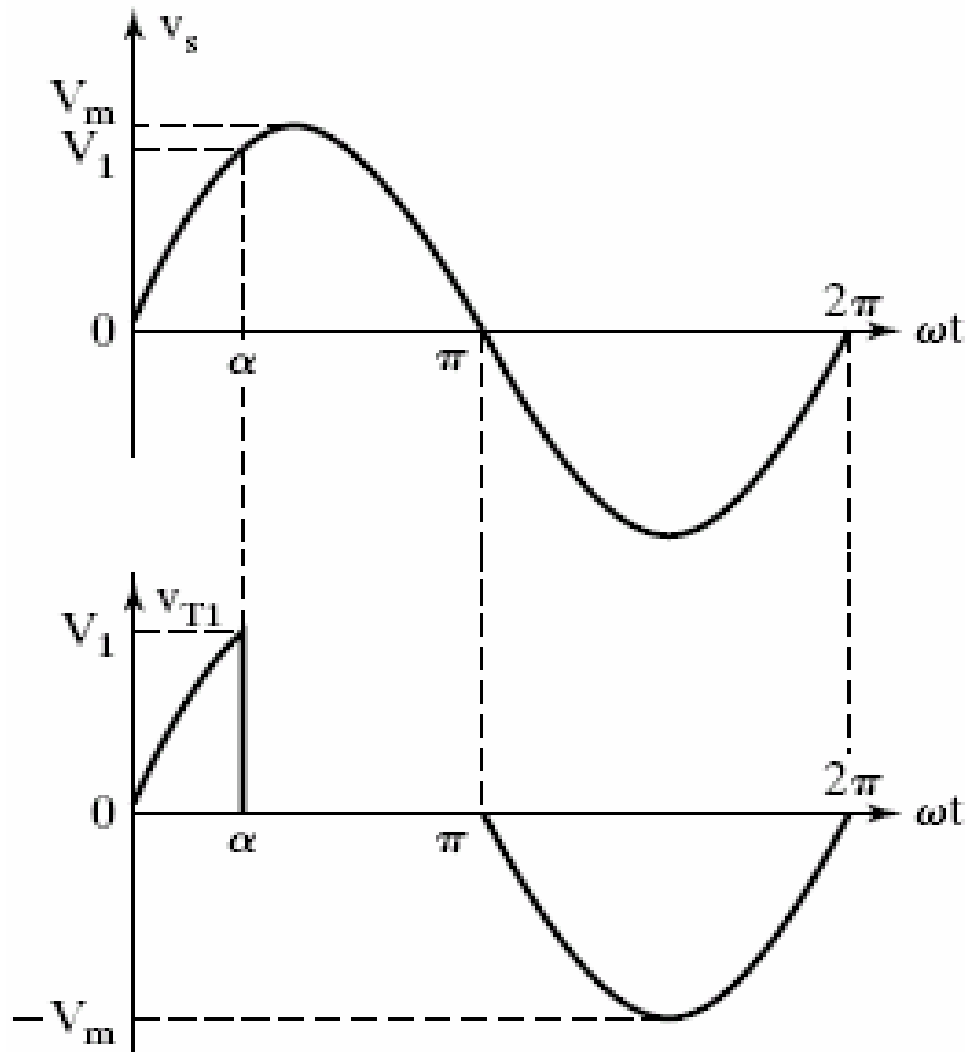

Supply Voltage

Thyristor Voltage



## Equations

$v_s = V_m \sin \omega t =$  i/p ac supply voltage

$V_m =$  max. value of i/p ac supply voltage

$V_S = \frac{V_m}{\sqrt{2}} =$  RMS value of i/p ac supply voltage

$v_O = v_L =$  output voltage across the load



When the thyristor is triggered at  $\omega t = \alpha$

$$v_O = v_L = V_m \sin \omega t; \omega t = \alpha \text{ to } \pi$$

$$i_O = i_L = \frac{v_O}{R} = \text{Load current}; \omega t = \alpha \text{ to } \pi$$

$$i_O = i_L = \frac{V_m \sin \omega t}{R} = I_m \sin \omega t; \omega t = \alpha \text{ to } \pi$$

Where  $I_m = \frac{V_m}{R} = \text{max. value of load current}$





To Derive an Expression for the  
Average (DC)  
Output Voltage Across The Load



$$V_{O(dc)} = V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} v_o \cdot d(\omega t);$$

$$v_o = V_m \sin \omega t \text{ for } \omega t = \alpha \text{ to } \pi$$

$$V_{O(dc)} = V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$



$$V_{O(dc)} = \frac{V_m}{2\pi} \int_{\alpha}^{\pi} \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \left[ -\cos \omega t \Big/_{\alpha}^{\pi} \right]$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \left[ -\cos \pi + \cos \alpha \right]; \quad \cos \pi = -1$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \left[ 1 + \cos \alpha \right]; \quad V_m = \sqrt{2}V_s$$



Maximum average (dc) o/p  
voltage is obtained when  $\alpha = 0$   
and the maximum dc output voltage

$$V_{dc(\max)} = V_{dm} = \frac{V_m}{2\pi} (1 + \cos 0); \cos(0) = 1$$

$$\therefore V_{dc(\max)} = V_{dm} = \frac{V_m}{\pi}$$



$$V_{O(dc)} = \frac{V_m}{2\pi} [1 + \cos \alpha] ; V_m = \sqrt{2}V_s$$

The average dc output voltage can be varied by varying the trigger angle  $\alpha$  from 0 to a maximum of  $180^\circ$  ( $\pi$  radians)

We can plot the control characteristic

( $V_{O(dc)}$  vs  $\alpha$ ) by using the equation for  $V_{O(dc)}$



# Control Characteristic of Single Phase Half Wave Phase Controlled Rectifier with Resistive Load



The average dc output voltage is given by the expression

$$V_{O(dc)} = \frac{V_m}{2\pi} [1 + \cos \alpha]$$

We can obtain the control characteristic by plotting the expression for the dc output voltage as a function of trigger angle  $\alpha$




Trigger angle $\alpha$ in degrees	$V_{O(dc)}$	%
0	$V_{dm} = \frac{V_m}{\pi}$	100% $V_{dm}$
30 <sup>0</sup>	0.933 $V_{dm}$	93.3 % $V_{dm}$
60 <sup>0</sup>	0.75 $V_{dm}$	75 % $V_{dm}$
90 <sup>0</sup>	0.5 $V_{dm}$	50 % $V_{dm}$
120 <sup>0</sup>	0.25 $V_{dm}$	25 % $V_{dm}$
150 <sup>0</sup>	0.06698 $V_{dm}$	6.69 % $V_{dm}$
180 <sup>0</sup>	0	0

$$V_{dm} = \frac{V_m}{\pi} = V_{dc(max)}$$





# Control Characteristic

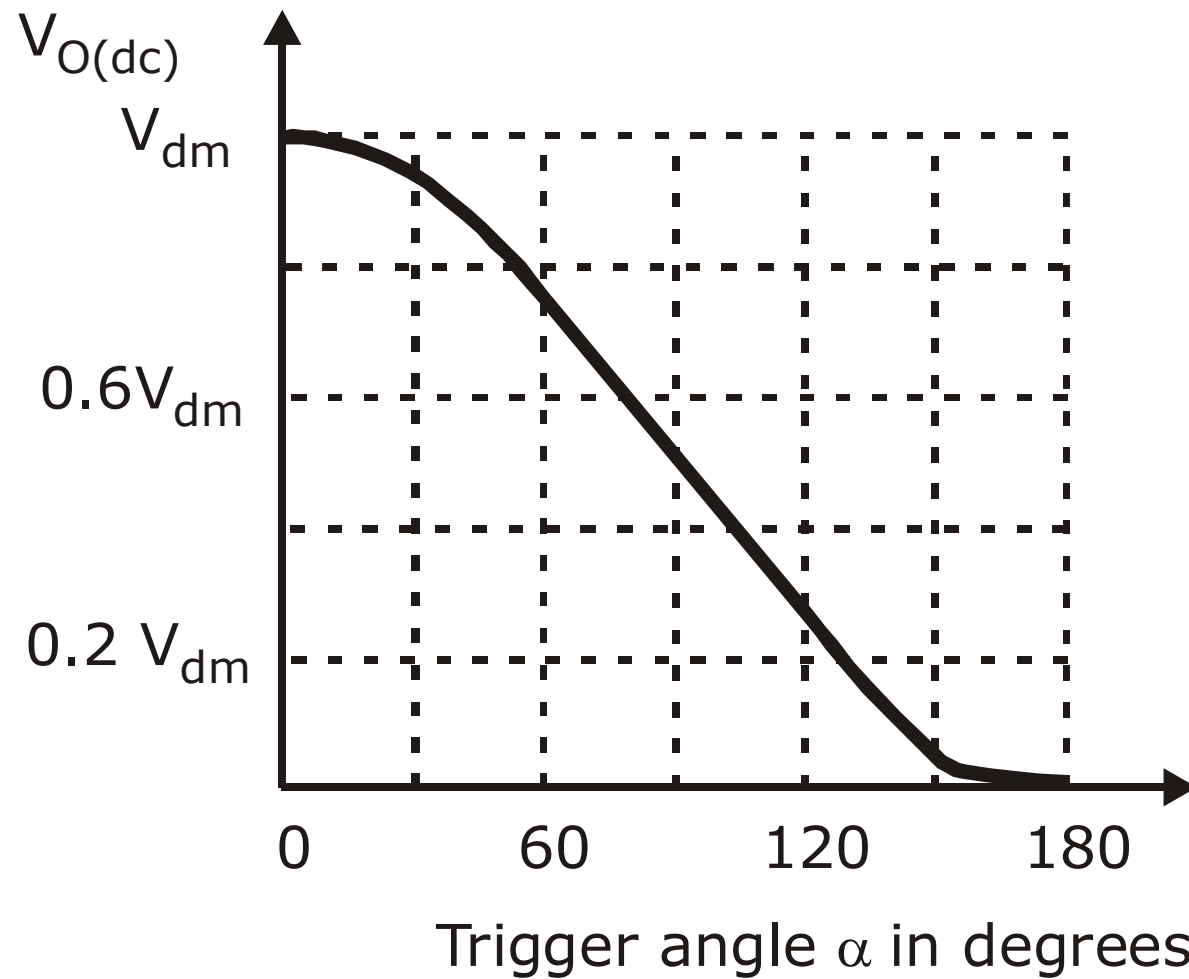



Normalizing the dc output  
voltage with respect to  $V_{dm}$ , the  
Normalized output voltage

$$V_n = \frac{V_{dc}}{V_{dm}} = \frac{\frac{V_m}{2\pi} (1 + \cos \alpha)}{\frac{V_m}{\pi}}$$

$$V_n = \frac{V_{dc}}{V_{dm}} = \frac{1}{2} (1 + \cos \alpha) = V_{dcn}$$



To Derive An  
Expression for the  
RMS Value of Output Voltage  
of a  
Single Phase Half Wave Controlled  
Rectifier With Resistive Load



The RMS output voltage is given by

$$V_{O(RMS)} = \left[ \frac{1}{2\pi} \int_0^{2\pi} v_o^2 \cdot d(\omega t) \right]$$

Output voltage  $v_o = V_m \sin \omega t$  ; for  $\omega t = \alpha$  to  $\pi$

$$V_{O(RMS)} = \left[ \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]^{\frac{1}{2}}$$



By substituting  $\sin^2 \omega t = \frac{1 - \cos 2\omega t}{2}$ , we get

$$V_{O(RMS)} = \left[ \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \frac{(1 - \cos 2\omega t)}{2} d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \left[ \frac{V_m^2}{4\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \left[ \frac{V_m^2}{4\pi} \left\{ \int_{\alpha}^{\pi} d(\omega t) - \int_{\alpha}^{\pi} \cos 2\omega t d(\omega t) \right\} \right]^{\frac{1}{2}}$$



$$V_{O(RMS)} = \frac{V_m}{2} \left[ \frac{1}{\pi} \left\{ (\omega t) \Big|_{\alpha}^{\pi} - \left( \frac{\sin 2\omega t}{2} \right) \Big|_{\alpha}^{\pi} \right\} \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{2} \left[ \frac{1}{\pi} \left( (\pi - \alpha) - \frac{(\sin 2\pi - \sin 2\alpha)}{2} \right) \right]^{\frac{1}{2}} ; \sin 2\pi = 0$$

$$V_{O(RMS)} = \frac{V_m}{2} \left[ \frac{1}{\pi} \left( (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \left( (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right)^{\frac{1}{2}}$$



# Performance Parameters Of Phase Controlled Rectifiers



Output dc power (avg. or dc o/p  
power delivered to the load)

$$P_{O(dc)} = V_{O(dc)} \times I_{O(dc)} ; \text{ i.e., } P_{dc} = V_{dc} \times I_{dc}$$

Where

$$V_{O(dc)} = V_{dc} = \text{avg./ dc value of o/p voltage.}$$

$$I_{O(dc)} = I_{dc} = \text{avg./dc value of o/p current}$$





Output ac power

$$P_{O(ac)} = V_{O(RMS)} \times I_{O(RMS)}$$

Efficiency of Rectification (Rectification Ratio)

$$\text{Efficiency } \eta = \frac{P_{O(dc)}}{P_{O(ac)}}; \quad \% \text{ Efficiency } \eta = \frac{P_{O(dc)}}{P_{O(ac)}} \times 100$$

The o/p voltage consists of two components

The dc component  $V_{O(dc)}$

The ac /ripple component  $V_{ac} = V_{r(rms)}$



The total RMS value of output voltage is given by

$$V_{O(RMS)} = \sqrt{V_{O(dc)}^2 + V_{r(rms)}^2}$$

$$\therefore V_{ac} = V_{r(rms)} = \sqrt{V_{O(RMS)}^2 - V_{O(dc)}^2}$$

Form Factor (FF) which is a measure of the shape of the output voltage is given by

$$FF = \frac{V_{O(RMS)}}{V_{O(dc)}} = \frac{\text{RMS output (load) voltage}}{\text{DC load output (load) voltage}}$$



The Ripple Factor (RF) w.r.t. o/p voltage w/f

$$r_v = RF = \frac{V_{r(rms)}}{V_{O(dc)}} = \frac{V_{ac}}{V_{dc}}$$

$$r_v = \frac{\sqrt{V_{O(RMS)}^2 - V_{O(dc)}^2}}{V_{O(dc)}} = \sqrt{\left[ \frac{V_{O(RMS)}}{V_{O(dc)}} \right]^2 - 1}$$

$$\therefore r_v = \sqrt{FF^2 - 1}$$



$$\text{Current Ripple Factor } r_i = \frac{I_{r(rms)}}{I_{O(dc)}} = \frac{I_{ac}}{I_{dc}}$$

$$\text{Where } I_{r(rms)} = I_{ac} = \sqrt{I_{O(RMS)}^2 - I_{O(dc)}^2}$$

$V_{r(pp)}$  = peak to peak ac ripple output voltage

$$V_{r(pp)} = V_{O(max)} - V_{O(min)}$$

$I_{r(pp)}$  = peak to peak ac ripple load current

$$I_{r(pp)} = I_{O(max)} - I_{O(min)}$$




## Transformer Utilization Factor (TUF)

$$TUF = \frac{P_{O(dc)}}{V_S \times I_S}$$

Where

$V_S$  = RMS supply (secondary) voltage

$I_S$  = RMS supply (secondary) current

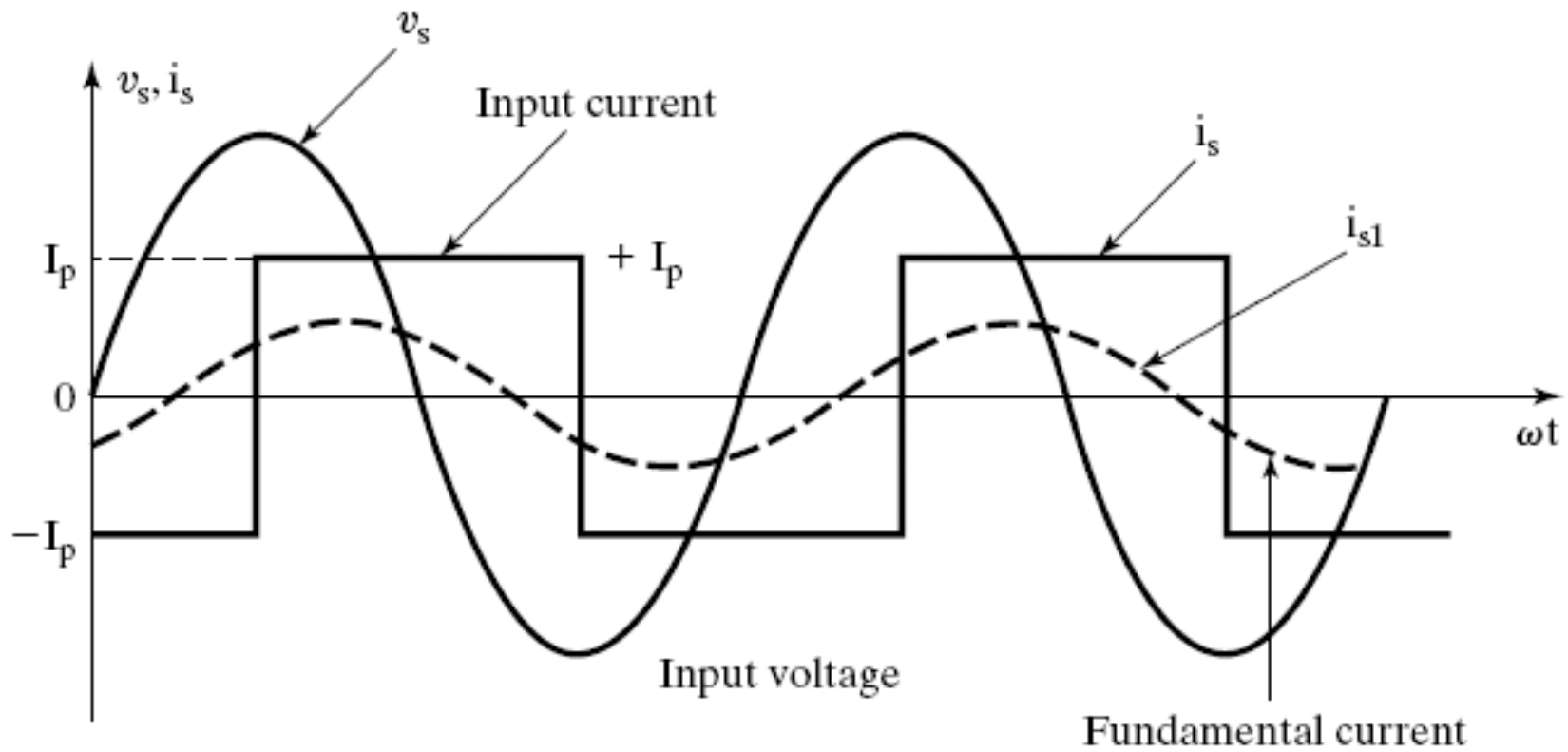



Where

$v_s$  = Supply voltage at the transformer secondary side

$i_s$  = i/p supply current

(transformer secondary winding current)

$i_{s1}$  = Fundamental component of the i/p supply current

$I_P$  = Peak value of the input supply current

$\phi$  = Phase angle difference between (sine wave components) the fundamental components of i/p supply current & the input supply voltage.



$\phi$  = Displacement angle (phase angle)

For an RL load

$\phi$  = Displacement angle = Load impedance angle

$$\therefore \phi = \tan^{-1} \left( \frac{\omega L}{R} \right) \text{ for an RL load}$$

Displacement Factor (DF) or

Fundamental Power Factor

$$DF = \cos \phi$$





Harmonic Factor (HF) or  
Total Harmonic Distortion Factor ; THD

$$HF = \left[ \frac{I_S^2 - I_{S1}^2}{I_{S1}^2} \right]^{\frac{1}{2}} = \left[ \left( \frac{I_S}{I_{S1}} \right)^2 - 1 \right]^{\frac{1}{2}}$$

Where

$I_S$  = RMS value of input supply current.

$I_{S1}$  = RMS value of fundamental component of  
the i/p supply current.



## Input Power Factor (PF)

$$PF = \frac{V_S I_{S1}}{V_S I_S} \cos \phi = \frac{I_{S1}}{I_S} \cos \phi$$

## The Crest Factor (CF)

$$CF = \frac{I_{S(\text{peak})}}{I_S} = \frac{\text{Peak input supply current}}{\text{RMS input supply current}}$$


## For an Ideal Controlled Rectifier

$$FF = 1; \eta = 100\%; V_{ac} = V_{r(\text{rms})} = 0; TUF = 1;$$

$$RF = r_v = 0; HF = THD = 0; PF = DPF = 1$$



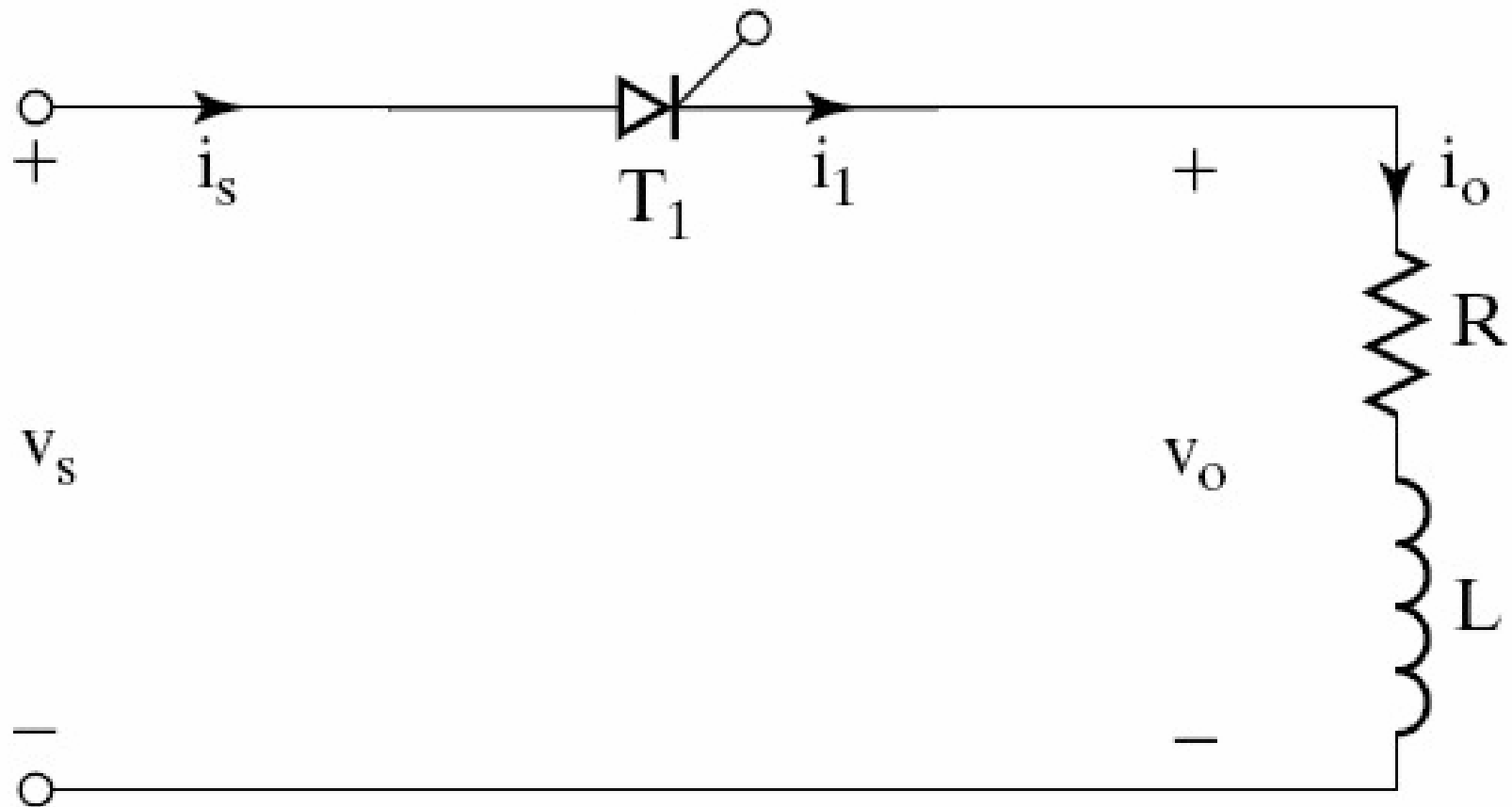
# Single Phase Half Wave Controlled Rectifier With An RL Load





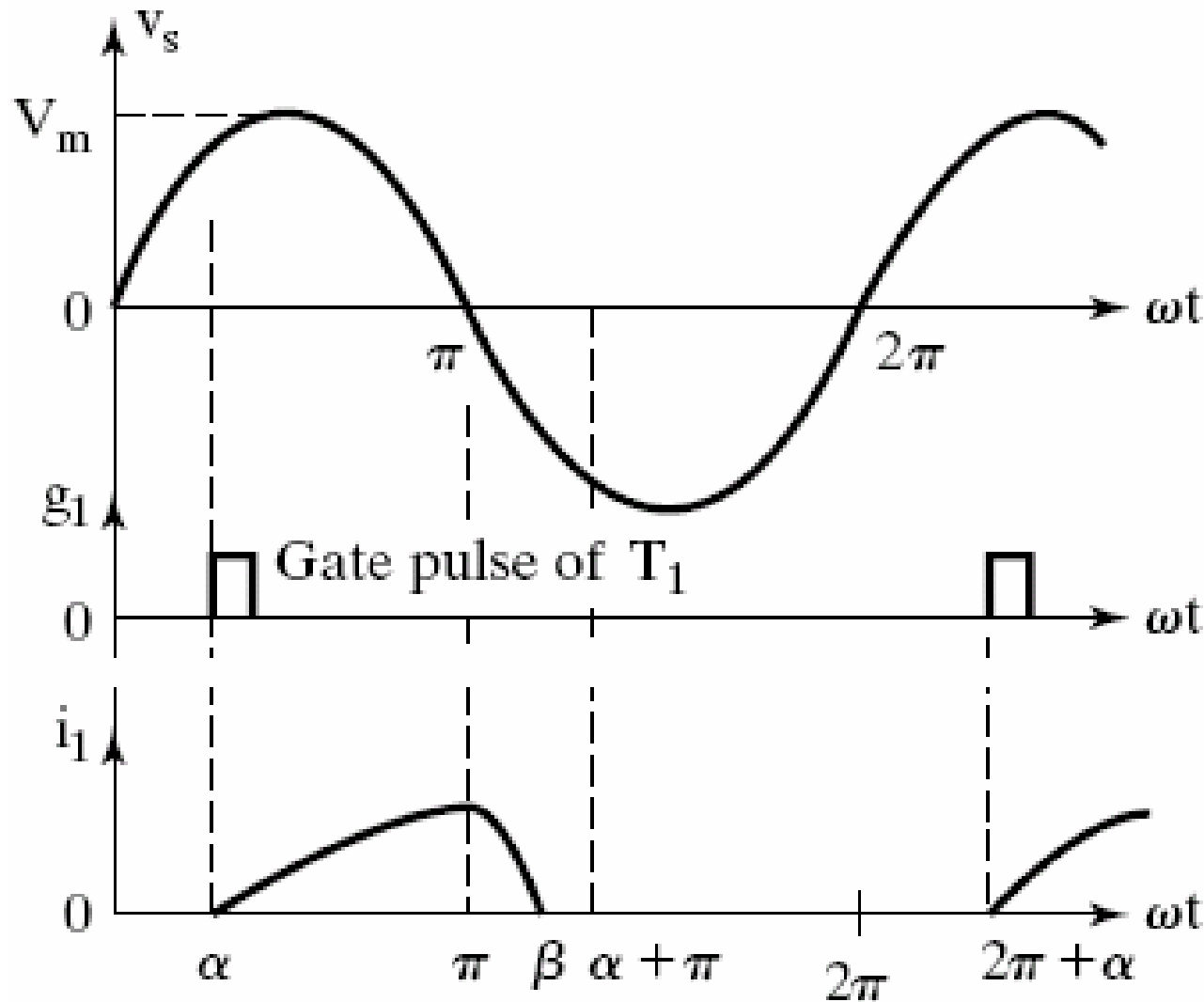
# Input Supply Voltage ( $V_s$ ) & Thyristor (Output) Current Waveforms





# Output (Load) Voltage Waveform

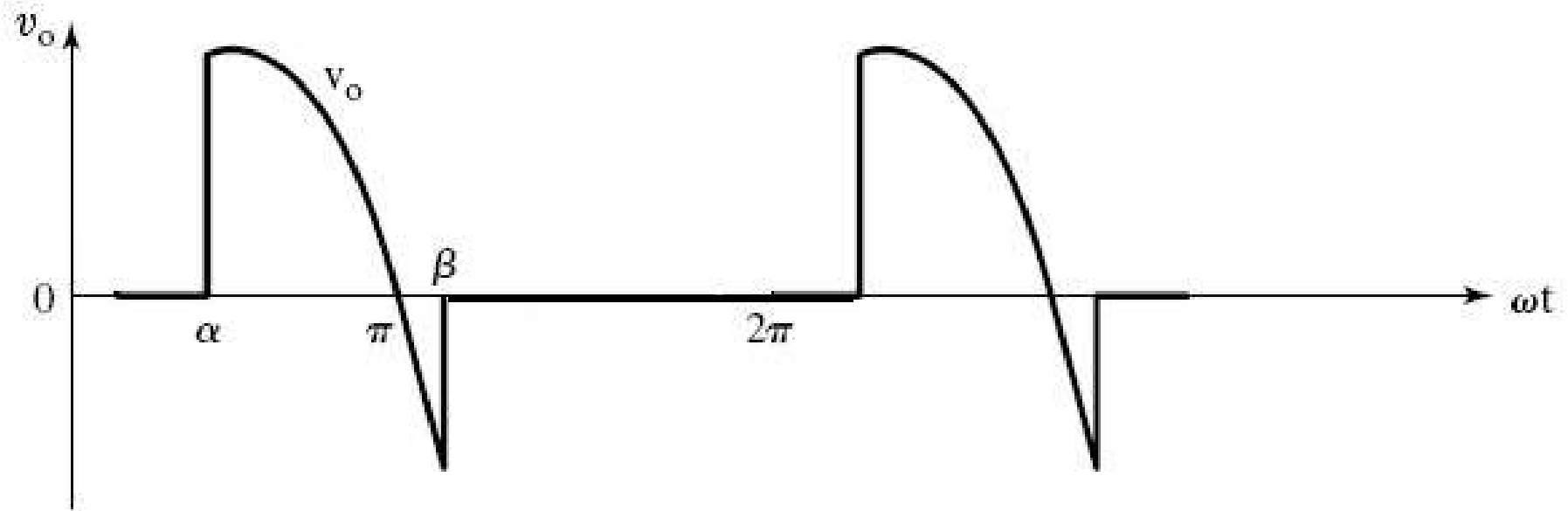



To Derive An Expression For  
The Output  
(Load) Current, During  $\omega t = \alpha$  to  $\beta$   
When Thyristor  $T_1$  Conducts





Assuming  $T_1$  is triggered  $\omega t = \alpha$ ,  
we can write the equation,

$$L \left( \frac{di_o}{dt} \right) + Ri_o = V_m \sin \omega t ; \alpha \leq \omega t \leq \beta$$

General expression for the output current,

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-t}{\tau}}$$



$$V_m = \sqrt{2}V_s = \text{maximum supply voltage.}$$

$$Z = \sqrt{R^2 + (\omega L)^2} = \text{Load impedance.}$$

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right) = \text{Load impedance angle.}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$

∴ general expression for the output load current

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-R}{L} t}$$



Constant  $A_1$  is calculated from

initial condition  $i_o = 0$  at  $\omega t = \alpha$  ;  $t = \left( \frac{\alpha}{\omega} \right)$

$$i_o = 0 = \frac{V_m}{Z} \sin(\alpha - \phi) + A_1 e^{\frac{-R}{L} t}$$

$$\therefore A_1 e^{\frac{-R}{L} t} = \frac{-V_m}{Z} \sin(\alpha - \phi)$$

We get the value of constant  $A_1$  as

$$A_1 = e^{\frac{R(\alpha)}{\omega L}} \left[ \frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$



Substituting the value of constant  $A_1$  in the general expression for  $i_o$

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + e^{\frac{-R}{\omega L}(\omega t - \alpha)} \left[ \frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

$\therefore$  we obtain the final expression for the inductive load current

$$i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right];$$

Where  $\alpha \leq \omega t \leq \beta$



Extinction angle  $\beta$  can be calculated by using the condition that  $i_o = 0$  at  $\omega t = \beta$

$$i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right] = 0$$

$$\therefore \sin(\beta - \phi) = e^{\frac{-R}{\omega L}(\beta - \alpha)} \times \sin(\alpha - \phi)$$

$\beta$  can be calculated by solving the above eqn.



To Derive An Expression  
For  
Average (DC) Load Voltage of a  
Single Half Wave Controlled  
Rectifier with  
RL Load



$$V_{O(dc)} = V_L = \frac{1}{2\pi} \int_0^{2\pi} v_O \cdot d(\omega t)$$

$$V_{O(dc)} = V_L = \frac{1}{2\pi} \left[ \int_0^{\alpha} v_O \cdot d(\omega t) + \int_{\alpha}^{\beta} v_O \cdot d(\omega t) + \int_{\beta}^{2\pi} v_O \cdot d(\omega t) \right]$$

$v_O = 0$  for  $\omega t = 0$  to  $\alpha$  & for  $\omega t = \beta$  to  $2\pi$

$$\therefore V_{O(dc)} = V_L = \frac{1}{2\pi} \left[ \int_{\alpha}^{\beta} v_O \cdot d(\omega t) \right];$$

$v_O = V_m \sin \omega t$  for  $\omega t = \alpha$  to  $\beta$



$$V_{O(dc)} = V_L = \frac{1}{2\pi} \left[ \int_{\alpha}^{\beta} V_m \sin \omega t . d(\omega t) \right]$$

$$V_{O(dc)} = V_L = \frac{V_m}{2\pi} \left[ -\cos \omega t \Big|_{\alpha}^{\beta} \right]$$

$$V_{O(dc)} = V_L = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

$$\therefore V_{O(dc)} = V_L = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$





## Effect of Load Inductance on the Output

During the period  $\omega t = \pi$  to  $\beta$  the instantaneous o/p voltage is negative and this reduces the average or the dc output voltage when compared to a purely resistive load.





## Average DC Load Current

$$I_{O(dc)} = I_{L(Avg)} = \frac{V_{O(dc)}}{R_L} = \frac{V_m}{2\pi R_L} (\cos \alpha - \cos \beta)$$


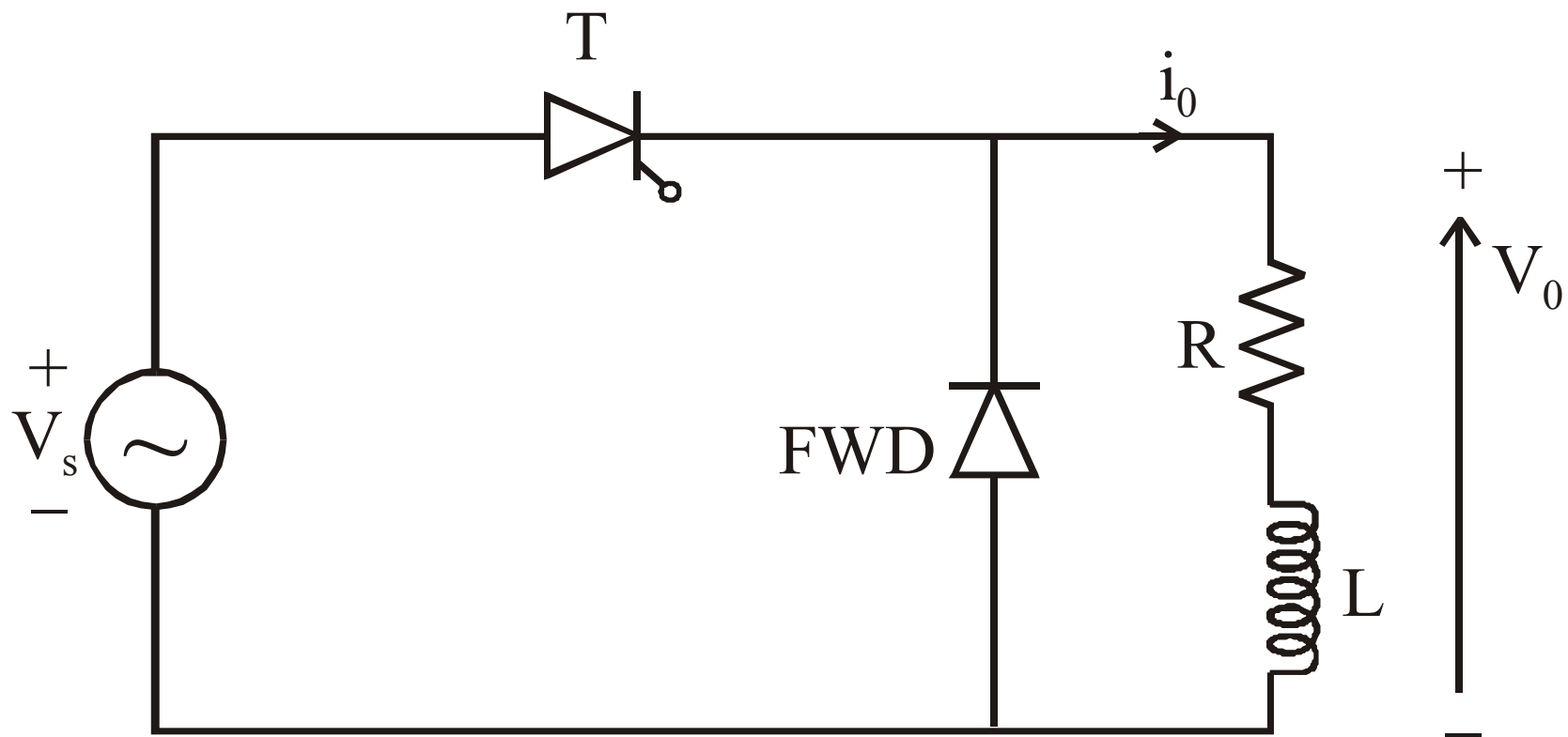
# Single Phase Half Wave Controlled Rectifier With RL Load & Free Wheeling Diode



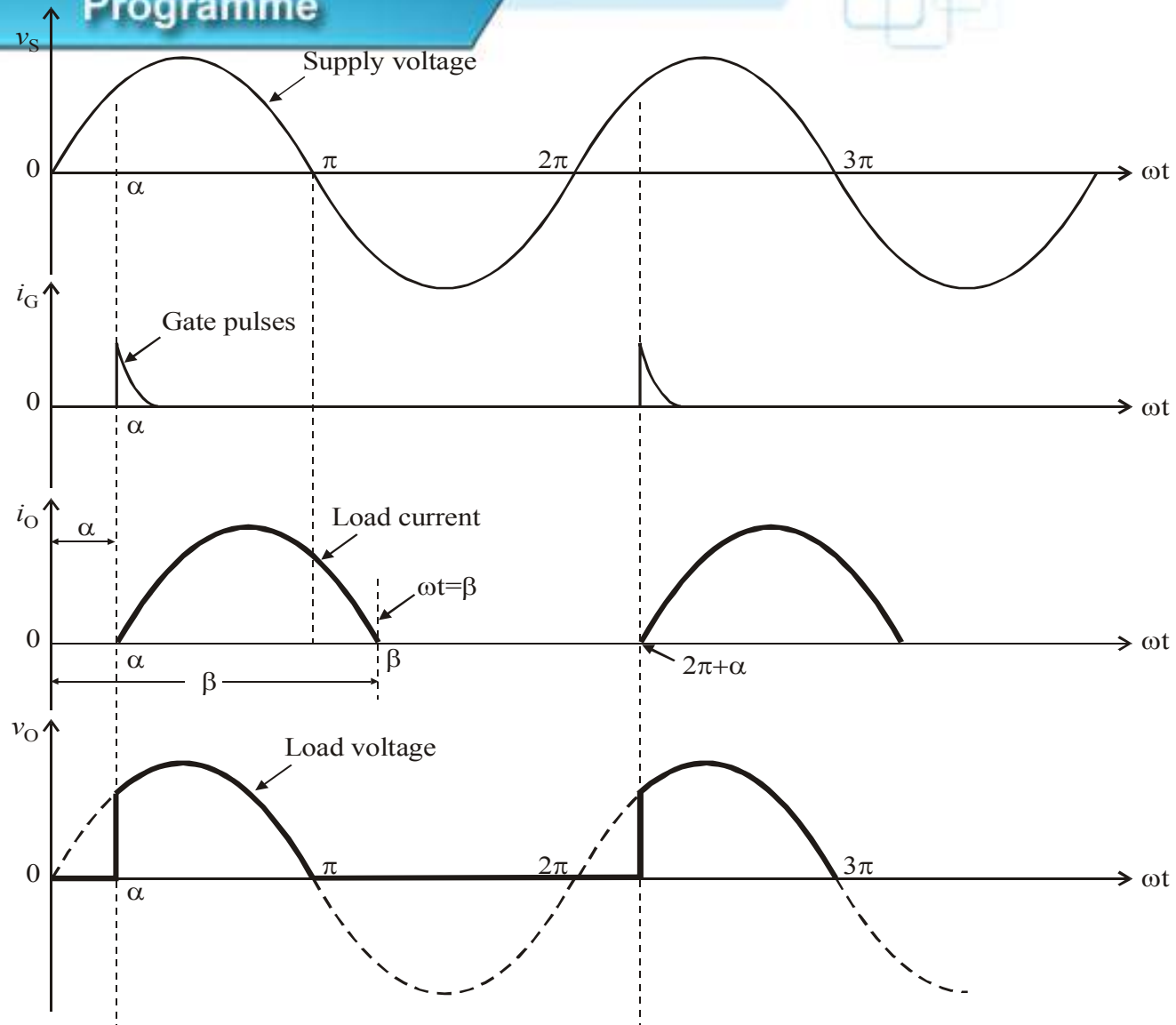



The average output voltage

$V_{dc} = \frac{V_m}{2\pi} [1 + \cos \alpha]$  which is the same as that  
of a purely resistive load.

**The following points are to be noted**

For low value of inductance, the load current  
tends to become discontinuous.



During the period  $\alpha$  to  $\pi$


the load current is carried by the SCR.

During the period  $\pi$  to  $\beta$  load current is carried by the free wheeling diode.

The value of  $\beta$  depends on the value of R and L and the forward resistance of the FWD.



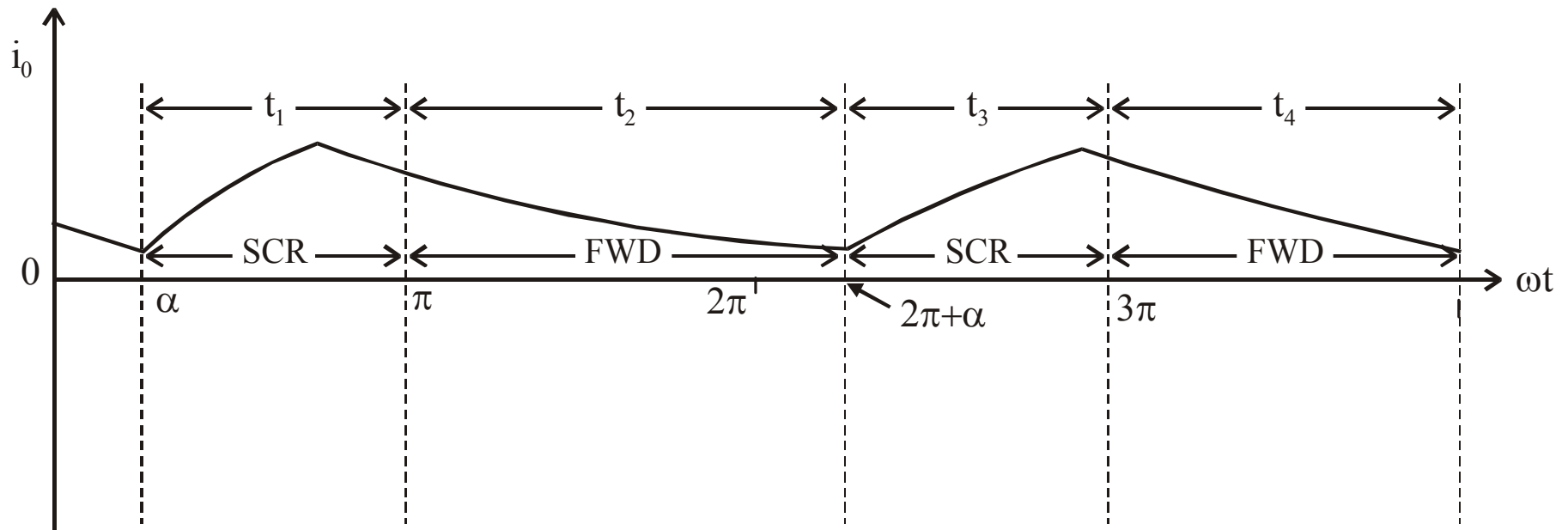
For Large Load Inductance  
the load current does not reach zero, &  
we obtain continuous load current






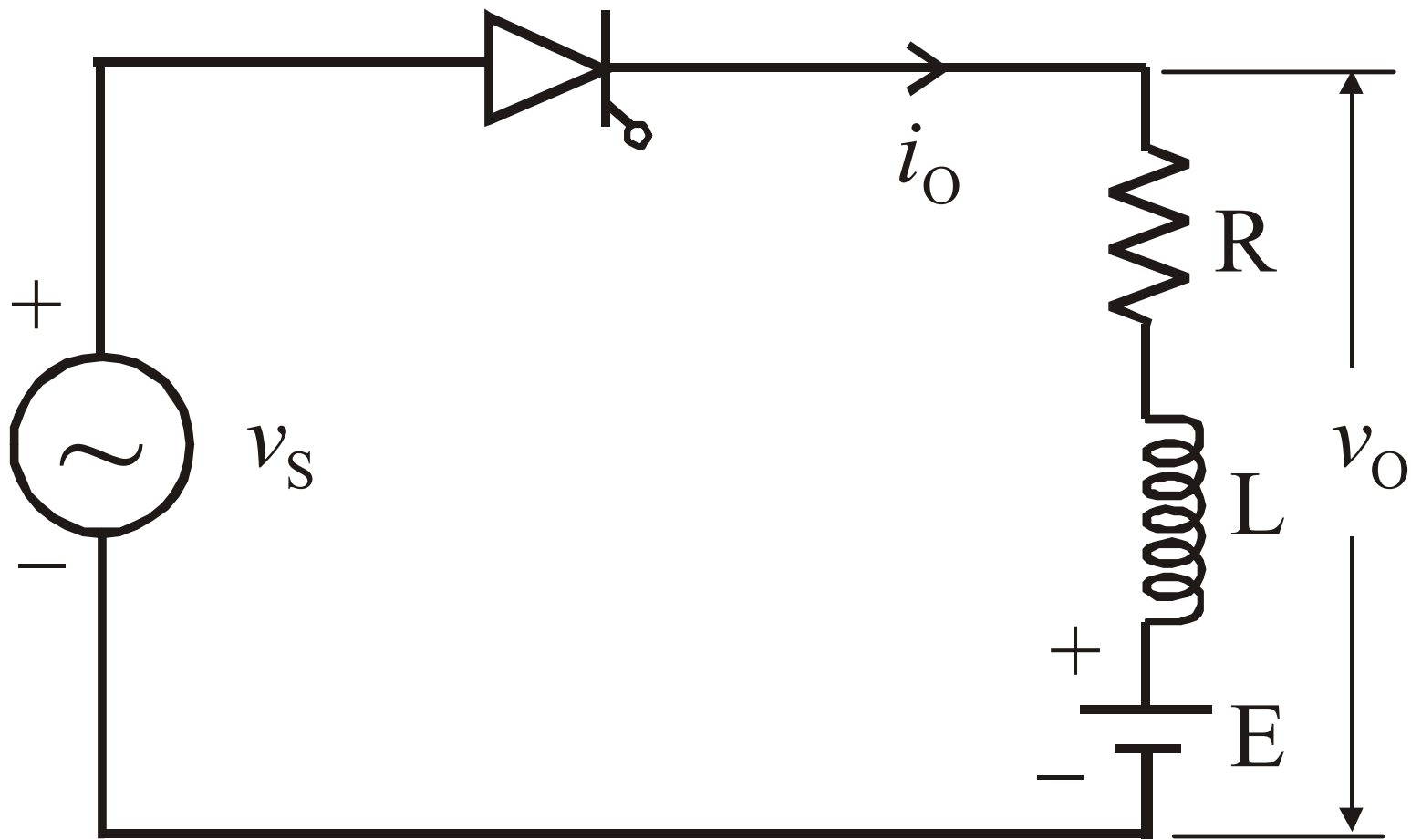
# Single Phase Half Wave Controlled Rectifier With A General Load






$$\gamma = \sin^{-1} \left( \frac{E}{V_m} \right)$$

For trigger angle  $\alpha < \gamma$ ,

the Thyristor conducts from  $\omega t = \gamma$  to  $\beta$

For trigger angle  $\alpha > \gamma$ ,

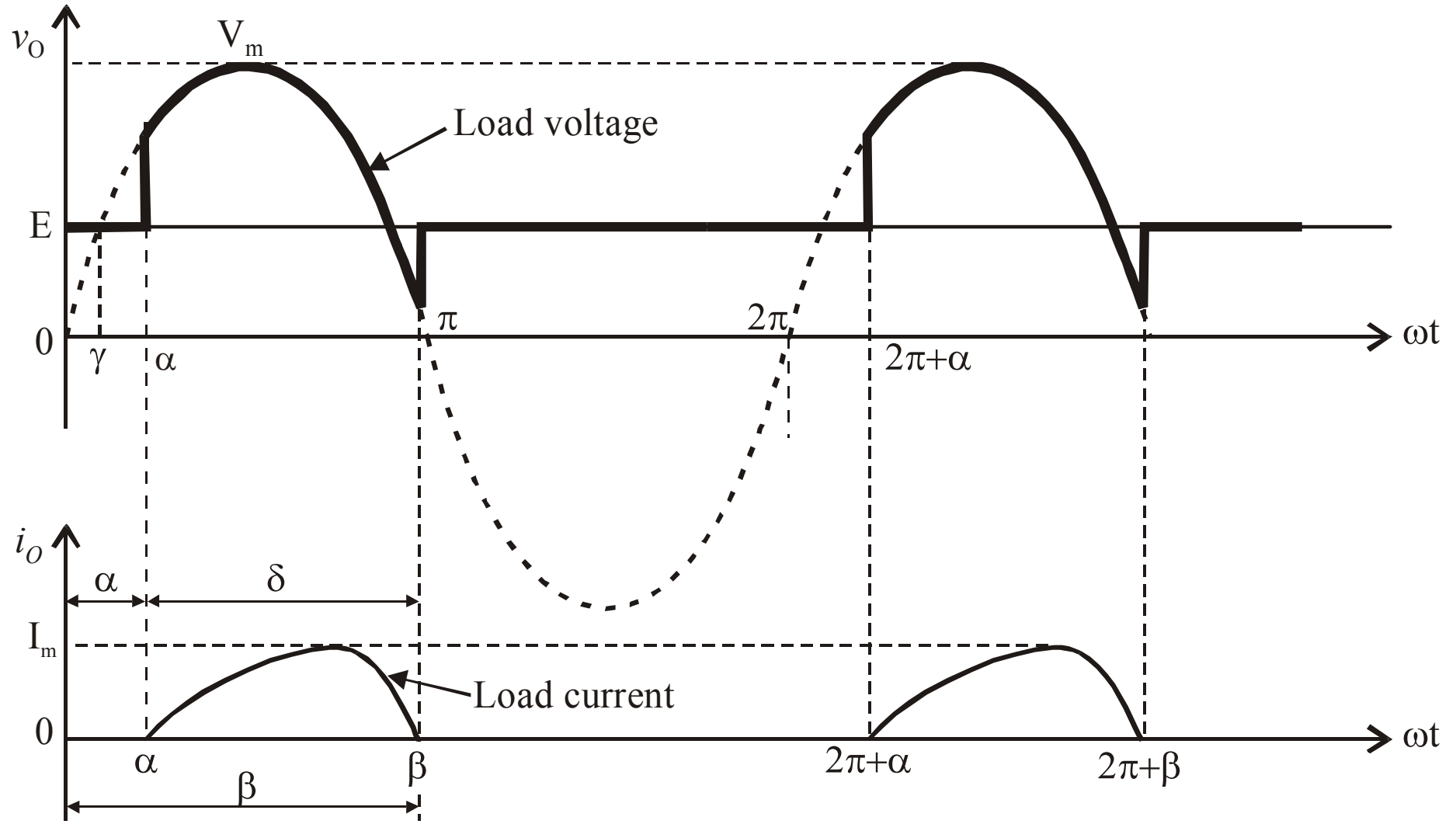the Thyristor conducts from  $\omega t = \alpha$  to  $\beta$





## Equations

$v_S = V_m \sin \omega t =$  Input supply voltage.

$v_O = V_m \sin \omega t =$  o/p (load) voltage

for  $\omega t = \alpha$  to  $\beta$ .

$v_O = E$  for  $\omega t = 0$  to  $\alpha$  &

for  $\omega t = \beta$  to  $2\pi$ .



## Expression for the Load Current

When the thyristor is triggered at a delay angle of  $\alpha > \gamma$ , the eqn. for the circuit can be written as

$$V_m \sin \omega t = i_o \times R + L \left( \frac{di_o}{dt} \right) + E ; \alpha \leq \omega t \leq \beta$$

The general expression for the output load current can be written as

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + Ae^{\frac{-t}{\tau}}$$



Where

$$Z = \sqrt{R^2 + (\omega L)^2} = \text{Load Impedance.}$$

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right) = \text{Load impedance angle.}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$

The general expression for the o/p current can

be written as 
$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + Ae^{\frac{-R}{L}t}$$



To find the value of the constant 'A' apply the initial conditions at  $\omega t = \alpha$ , load current  $i_o = 0$ , Equating the general expression for the load current to zero at  $\omega t = \alpha$ , we get

$$i_o = 0 = \frac{V_m}{Z} \sin(\alpha - \phi) - \frac{E}{R} + Ae^{\frac{-R}{L} \times \frac{\alpha}{\omega}}$$





We obtain the value of constant 'A' as

$$A = \left[ \frac{E}{R} - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{\frac{R}{\omega L} \alpha}$$

Substituting the value of the constant 'A' in the expression for the load current; we get the complete expression for the output load current as

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + \left[ \frac{E}{R} - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{\frac{-R}{\omega L}(\omega t - \alpha)}$$



To Derive  
An  
Expression For The Average  
Or  
DC Load Voltage



$$V_{O(dc)} = \frac{1}{2\pi} \int_0^{2\pi} v_o \cdot d(\omega t)$$

$$V_{O(dc)} = \frac{1}{2\pi} \left[ \int_0^{\alpha} v_o \cdot d(\omega t) + \int_{\alpha}^{\beta} v_o \cdot d(\omega t) + \int_{\beta}^{2\pi} v_o \cdot d(\omega t) \right]$$

$v_o = V_m \sin \omega t =$  Output load voltage for  $\omega t = \alpha$  to  $\beta$

$v_o = E$  for  $\omega t = 0$  to  $\alpha$  & for  $\omega t = \beta$  to  $2\pi$

$$V_{O(dc)} = \frac{1}{2\pi} \left[ \int_0^{\alpha} E \cdot d(\omega t) + \int_{\alpha}^{\beta} V_m \sin \omega t + \int_{\beta}^{2\pi} E \cdot d(\omega t) \right]$$



$$V_{O(dc)} = \frac{1}{2\pi} \left[ E(\omega t) \Big|_0^\alpha + V_m (-\cos \omega t) \Big|_\alpha^\beta + E(\omega t) \Big|_\beta^{2\pi} \right]$$
$$V_{O(dc)} = \frac{1}{2\pi} \left[ E(\alpha - 0) - V_m (\cos \beta - \cos \alpha) + E(2\pi - \beta) \right]$$
$$V_{O(dc)} = \frac{V_m}{2\pi} \left[ (\cos \alpha - \cos \beta) \right] + \frac{E}{2\pi} \left[ (2\pi - \beta + \alpha) \right]$$
$$V_{O(dc)} = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta) + \left[ \frac{2\pi - (\beta - \alpha)}{2\pi} \right] E$$




Conduction angle of thyristor  $\delta = (\beta - \alpha)$

RMS Output Voltage can be calculated  
by using the expression

$$V_{O(RMS)} = \sqrt{\frac{1}{2\pi} \left[ \int_0^{2\pi} v_o^2 \cdot d(\omega t) \right]}$$


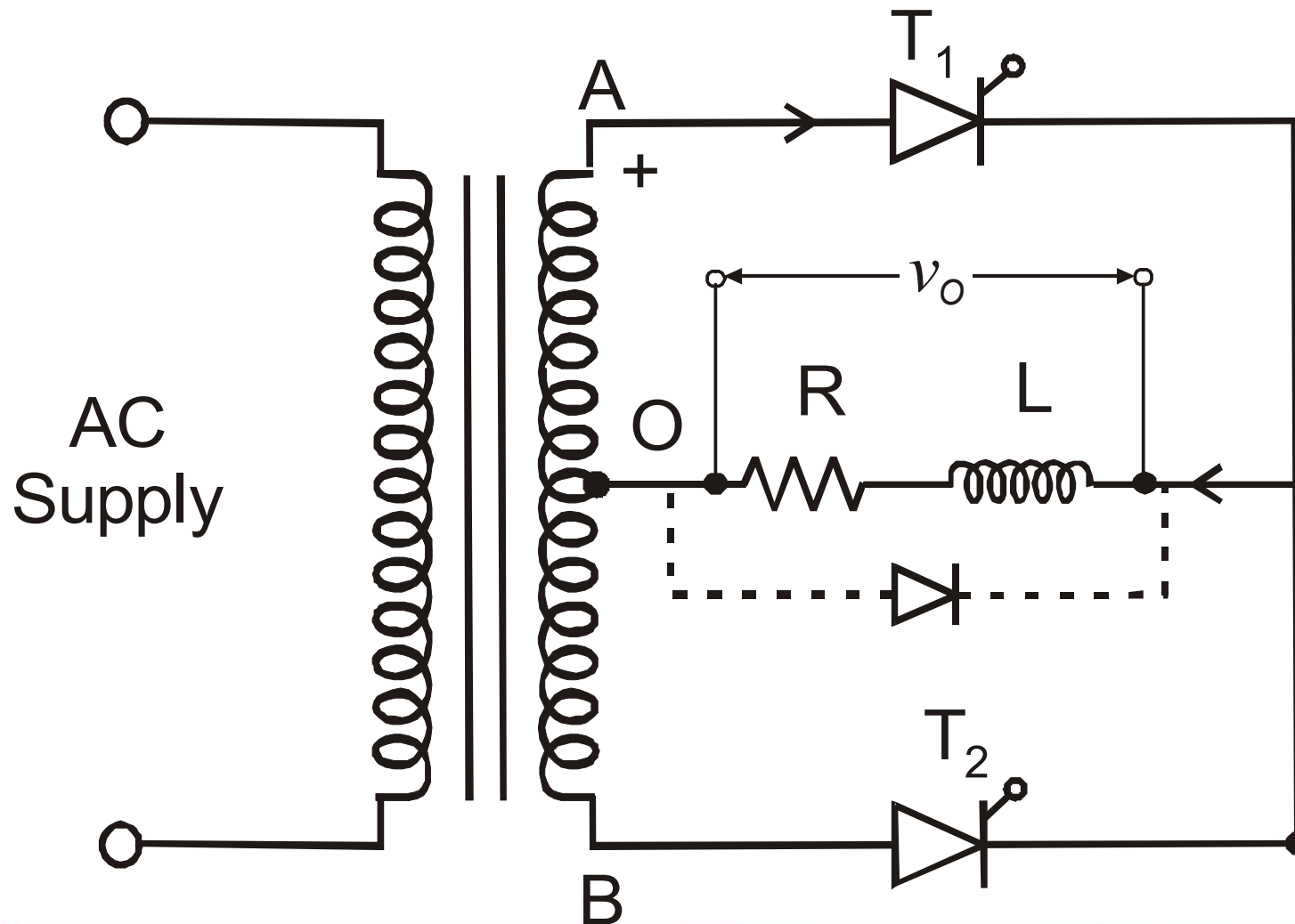
# Single Phase Full Wave Controlled Rectifier Using A Center Tapped Transformer






# Discontinuous Load Current Operation without FWD for

$$\pi < \beta < (\pi + \alpha)$$



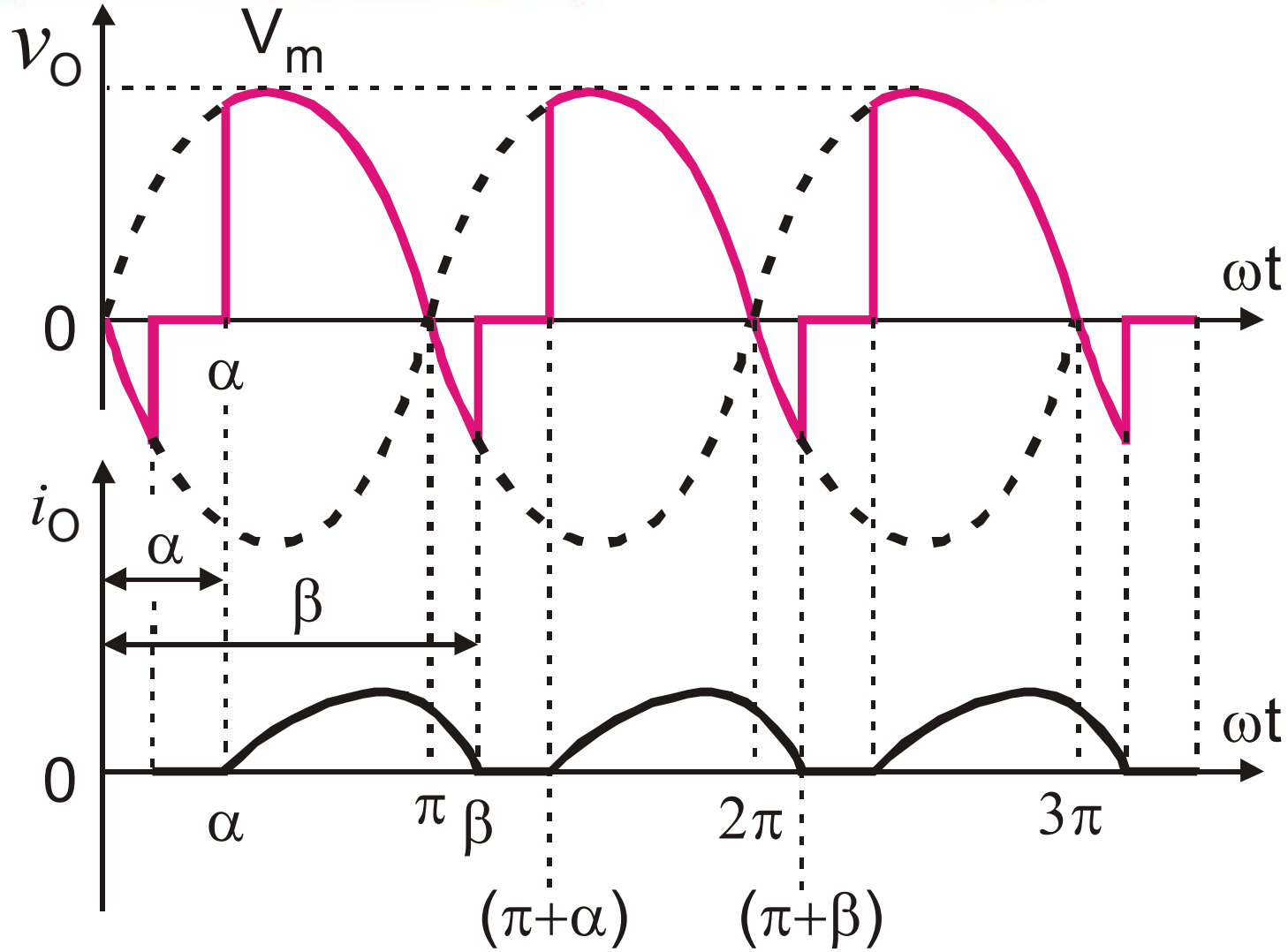



To Derive An Expression For  
The Output  
(Load) Current, During  $\omega t = \alpha$  to  $\beta$   
When Thyristor  $T_1$  Conducts



Assuming  $T_1$  is triggered  $\omega t = \alpha$ ,  
we can write the equation,

$$L \left( \frac{di_o}{dt} \right) + Ri_o = V_m \sin \omega t ; \alpha \leq \omega t \leq \beta$$

General expression for the output current,

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-t}{\tau}}$$



$$V_m = \sqrt{2}V_s = \text{maximum supply voltage.}$$

$$Z = \sqrt{R^2 + (\omega L)^2} = \text{Load impedance.}$$

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right) = \text{Load impedance angle.}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$

$\therefore$  general expression for the output load current

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-R}{L} t}$$



Constant  $A_1$  is calculated from

initial condition  $i_o = 0$  at  $\omega t = \alpha$  ;  $t = \left( \frac{\alpha}{\omega} \right)$

$$i_o = 0 = \frac{V_m}{Z} \sin(\alpha - \phi) + A_1 e^{\frac{-R}{L} t}$$

$$\therefore A_1 e^{\frac{-R}{L} t} = \frac{-V_m}{Z} \sin(\alpha - \phi)$$

We get the value of constant  $A_1$  as

$$A_1 = e^{\frac{R(\alpha)}{\omega L}} \left[ \frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$



Substituting the value of constant  $A_1$  in the general expression for  $i_o$

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + e^{\frac{-R}{\omega L}(\omega t - \alpha)} \left[ \frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

$\therefore$  we obtain the final expression for the inductive load current

$$i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right];$$

Where  $\alpha \leq \omega t \leq \beta$



Extinction angle  $\beta$  can be calculated by using the condition that  $i_o = 0$  at  $\omega t = \beta$

$$i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right] = 0$$


$$\therefore \sin(\beta - \phi) = e^{\frac{-R}{\omega L}(\beta - \alpha)} \times \sin(\alpha - \phi)$$

$\beta$  can be calculated by solving the above eqn.



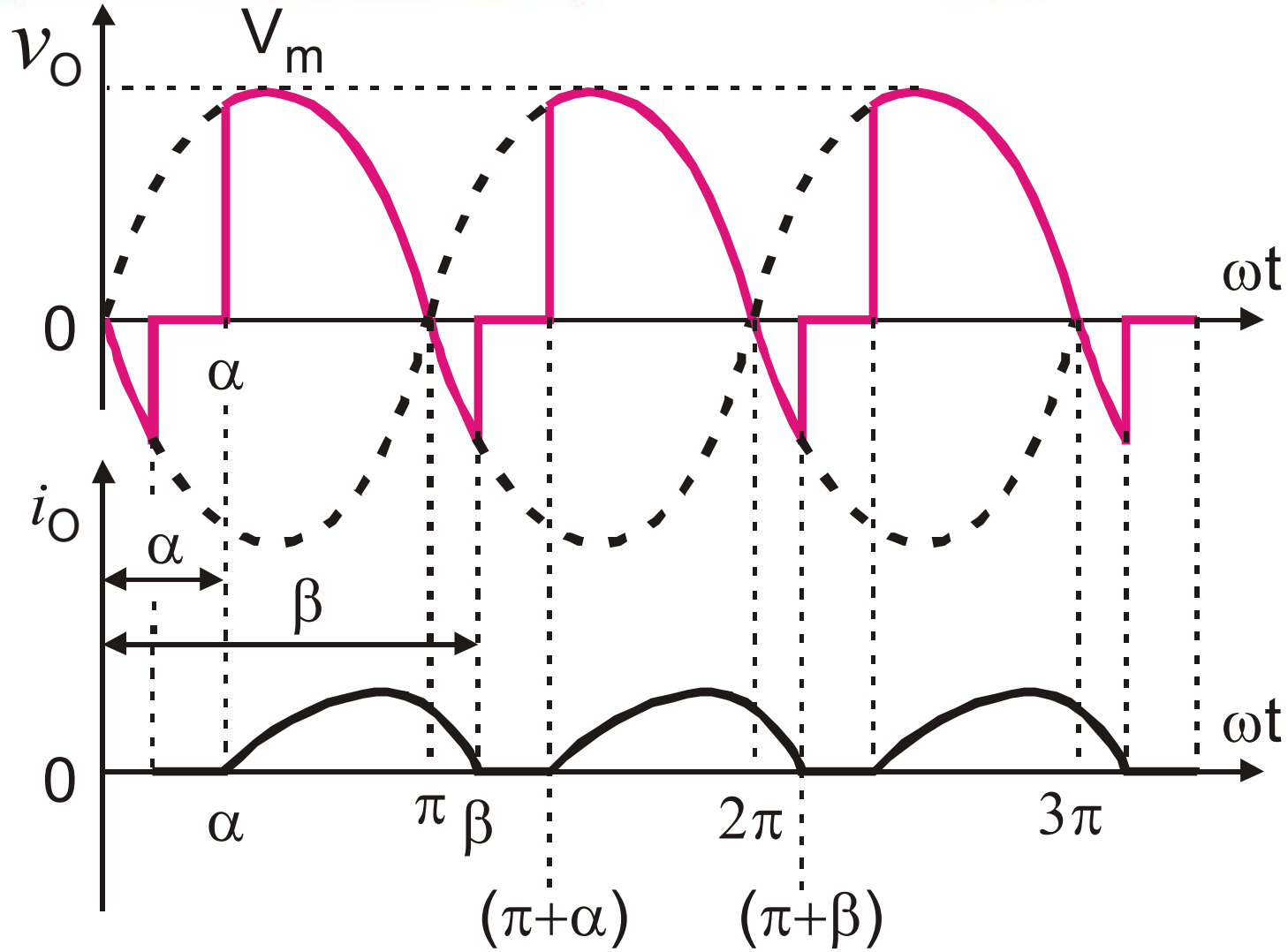To Derive An Expression For The DC  
Output Voltage Of  
A Single Phase Full Wave Controlled  
Rectifier With RL Load  
*(Without FWD)*







$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t = \alpha}^{\beta} v_o \cdot d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \left[ \int_{\alpha}^{\beta} V_m \sin \omega t \cdot d(\omega t) \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ -\cos \omega t \Big|_{\alpha}^{\beta} \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} (\cos \alpha - \cos \beta)$$



When the load inductance is negligible( i.e.,  $L \approx 0$ )

Extinction angle  $\beta = \pi$  radians

Hence the average or dc output voltage for R load

$$V_{O(dc)} = \frac{V_m}{\pi} (\cos \alpha - \cos \pi)$$

$$V_{O(dc)} = \frac{V_m}{\pi} (\cos \alpha - (-1))$$

$$V_{O(dc)} = \frac{V_m}{\pi} (1 + \cos \alpha); \text{ for R load, when } \beta = \pi$$




To calculate the RMS output voltage we use the expression

$$V_{O(RMS)} = \sqrt{\frac{1}{\pi} \left[ \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]}$$


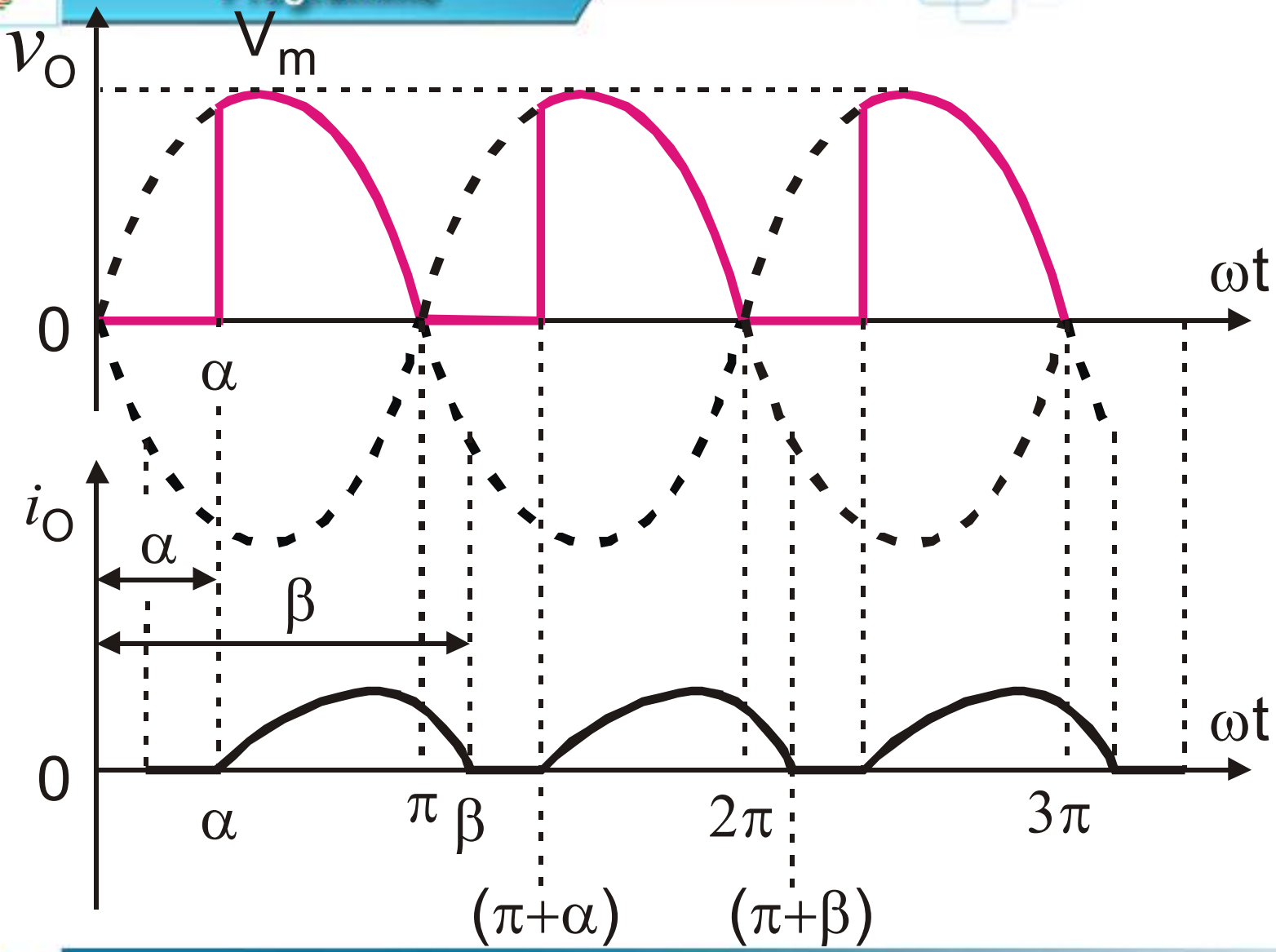
# Discontinuous Load Current Operation with FWD





Thyristor  $T_1$  is triggered at  $\omega t = \alpha$ ;

$T_1$  conducts from  $\omega t = \alpha$  to  $\pi$

Thyristor  $T_2$  is triggered at  $\omega t = (\pi + \alpha)$ ;

$T_2$  conducts from  $\omega t = (\pi + \alpha)$  to  $2\pi$

FWD conducts from  $\omega t = \pi$  to  $\beta$  &

$v_o \approx 0$  during discontinuous load current.



To Derive an Expression  
For The  
DC Output Voltage For  
A  
Single Phase Full Wave Controlled  
Rectifier  
With RL Load & FWD





$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t=0}^{\pi} v_o \cdot d(\omega t)$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ -\cos \omega t \Big|_{\alpha}^{\pi} \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ -\cos \pi + \cos \alpha \right] ; \cos \pi = -1$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} (1 + \cos \alpha)$$




- The load current is discontinuous for low values of load inductance and for large values of trigger angles.
- For large values of load inductance the load current flows continuously without falling to zero.
- Generally the load current is continuous for large load inductance and for low trigger angles.



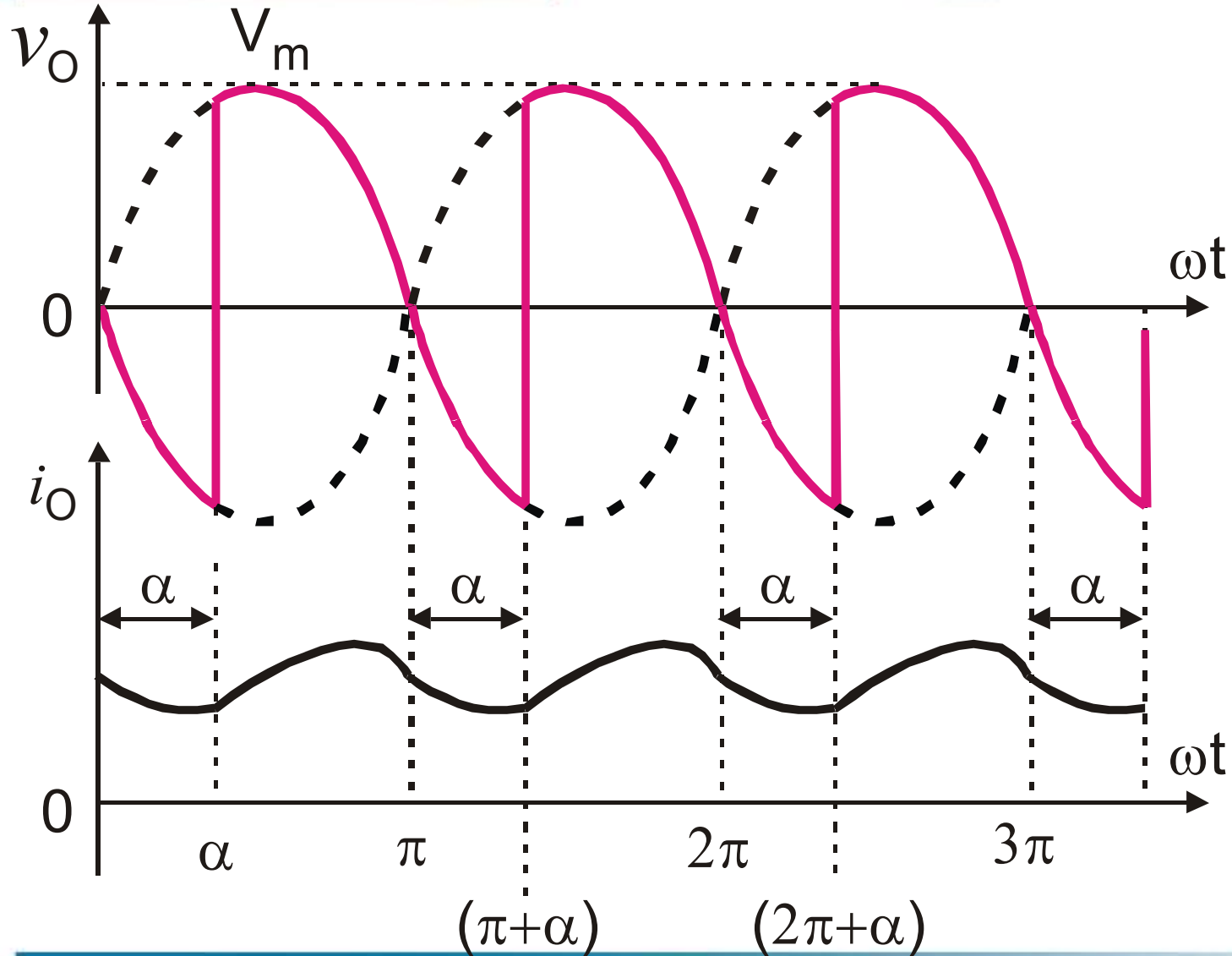
# Continuous Load Current Operation (Without FWD)







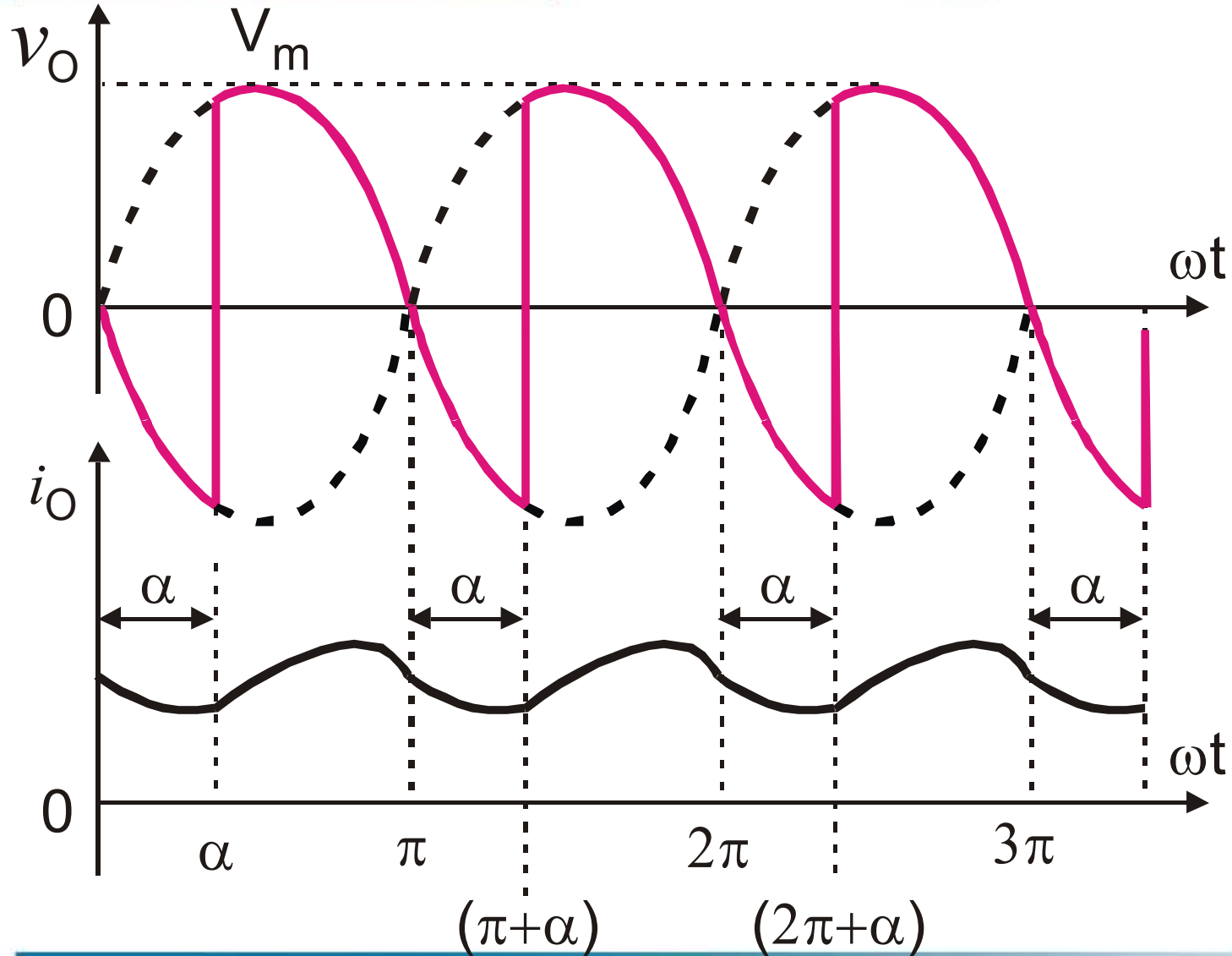To Derive  
An Expression For  
Average / DC Output Voltage  
Of  
Single Phase Full Wave Controlled  
Rectifier For Continuous Current  
Operation without FWD





$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t = \alpha}^{(\pi + \alpha)} v_o \cdot d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \left[ \int_{\alpha}^{(\pi + \alpha)} V_m \sin \omega t \cdot d(\omega t) \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ -\cos \omega t \Big/_{\alpha}^{(\pi + \alpha)} \right]$$



$$V_{O(dc)} = V_{dc}$$

$$= \frac{V_m}{\pi} \left[ \cos \alpha - \cos(\pi + \alpha) \right];$$

$$\cos(\pi + \alpha) = -\cos \alpha$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ \cos \alpha + \cos \alpha \right]$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{2V_m}{\pi} \cos \alpha$$






- By plotting  $V_{O(dc)}$  versus  $\alpha$ , we obtain the control characteristic of a single phase full wave controlled rectifier with RL load for continuous load current operation without FWD



Trigger angle $\alpha$ in degrees	$V_{O(dc)}$	Remarks
0	$V_{dm} = \left( \frac{2V_m}{\pi} \right)$	Maximum dc output voltage $V_{dc(max)} = V_{dm} = \left( \frac{2V_m}{\pi} \right)$
30°	0.866 $V_{dm}$	$V_{dc} = V_{dm} \times \cos \alpha$
60°	0.5 $V_{dm}$	
90°	0 $V_{dm}$	
120°	-0.5 $V_{dm}$	
150°	-0.866 $V_{dm}$	
180°	$-V_{dm} = -\left( \frac{2V_m}{\pi} \right)$	



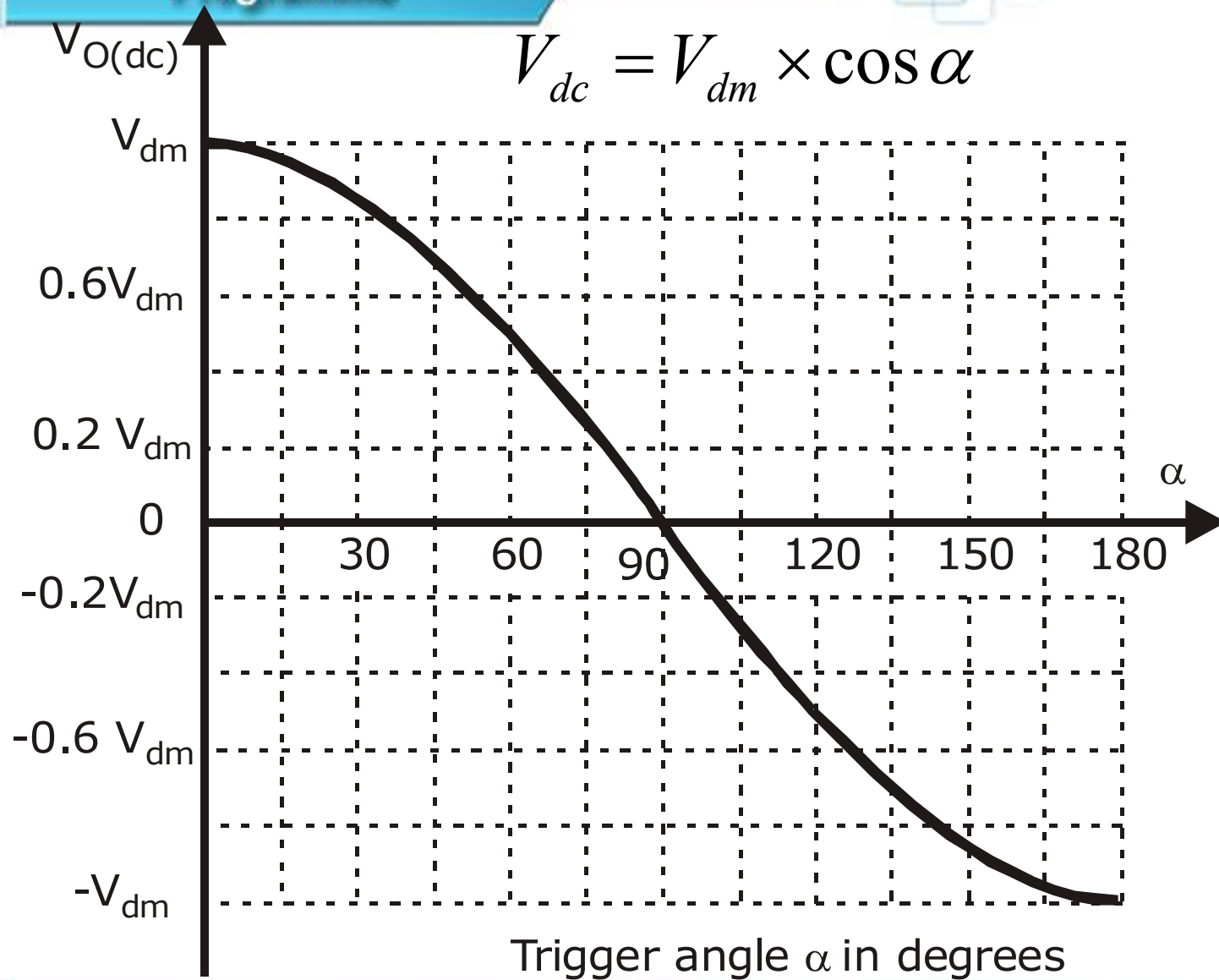



By varying the trigger angle we can vary the output dc voltage across the load. Hence we can control the dc output power flow to the load.

For trigger angle  $\alpha$ , 0 to  $90^\circ$  (*i.e.*,  $0 \leq \alpha \leq 90^\circ$ );

$\cos \alpha$  is positive and hence  $V_{dc}$  is positive

$V_{dc}$  &  $I_{dc}$  are positive ;  $P_{dc} = (V_{dc} \times I_{dc})$  is positive

Converter operates as a **Controlled Rectifier**.

Power flow is from the ac source to the load.



For trigger angle  $\alpha$ ,  $90^\circ$  to  $180^\circ$

$$(i.e., 90^\circ \leq \alpha \leq 180^\circ),$$

$\cos\alpha$  is negative and hence

$V_{dc}$  is negative;  $I_{dc}$  is positive ;

$$P_{dc} = (V_{dc} \times I_{dc}) \text{ is negative.}$$

In this case the converter operates

as a **Line Commutated Inverter.**

Power flows from the load ckt. to the i/p ac source.

The inductive load energy is fed back to the

i/p source.



## Drawbacks Of Full Wave Controlled Rectifier With Centre Tapped Transformer

- We require a centre tapped transformer which is quite heavier and bulky.
- Cost of the transformer is higher for the required dc output voltage & output power.
- Hence full wave bridge converters are preferred.



# Single Phase Full Wave Bridge Controlled Rectifier

2 types of FW Bridge Controlled Rectifiers are


- Half Controlled Bridge Converter  
(Semi-Converter)
- Fully Controlled Bridge Converter  
(Full Converter)

*The bridge full wave controlled rectifier does not  
require a centre tapped transformer*


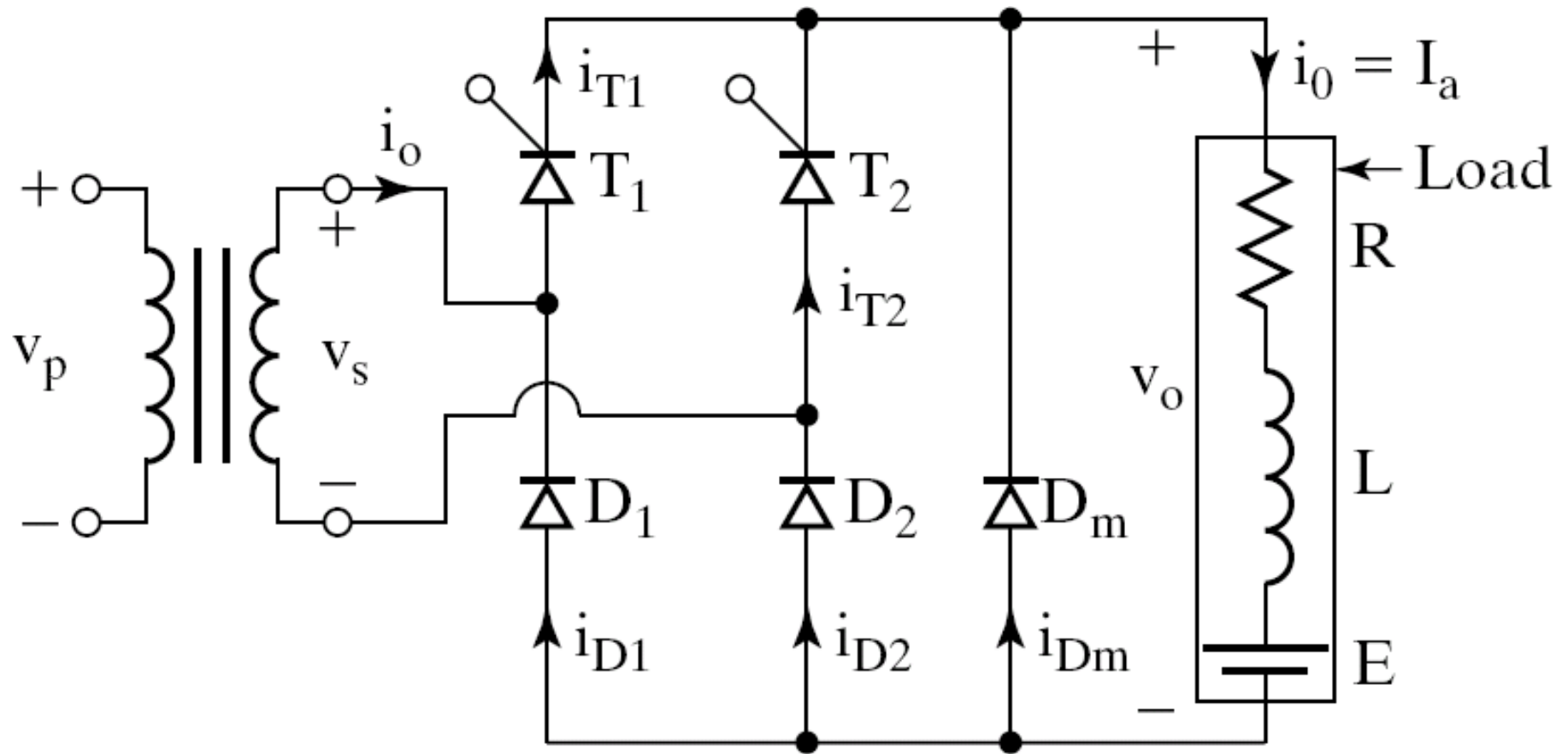
# Single Phase Full Wave Half Controlled Bridge Converter (Single Phase Semi Converter)







## Trigger Pattern of Thyristors

*Thyristor  $T_1$  is triggered at*

$$\omega t = \alpha, \text{ at } \omega t = (2\pi + \alpha), \dots$$

*Thyristor  $T_2$  is triggered at*



$$\omega t = (\pi + \alpha), \text{ at } \omega t = (3\pi + \alpha), \dots$$

*The time delay between the gating*


*signals of  $T_1$  &  $T_2 = \pi$  radians or  $180^\circ$*




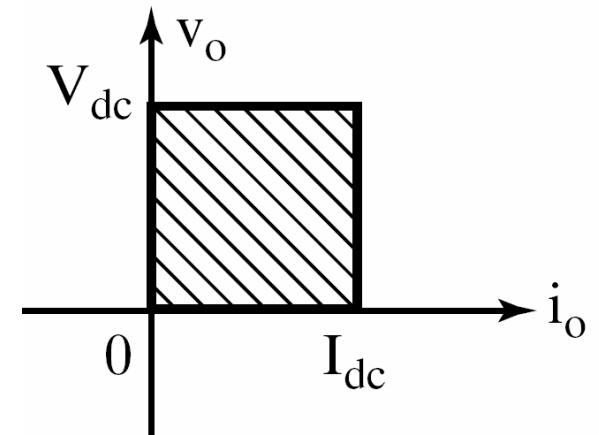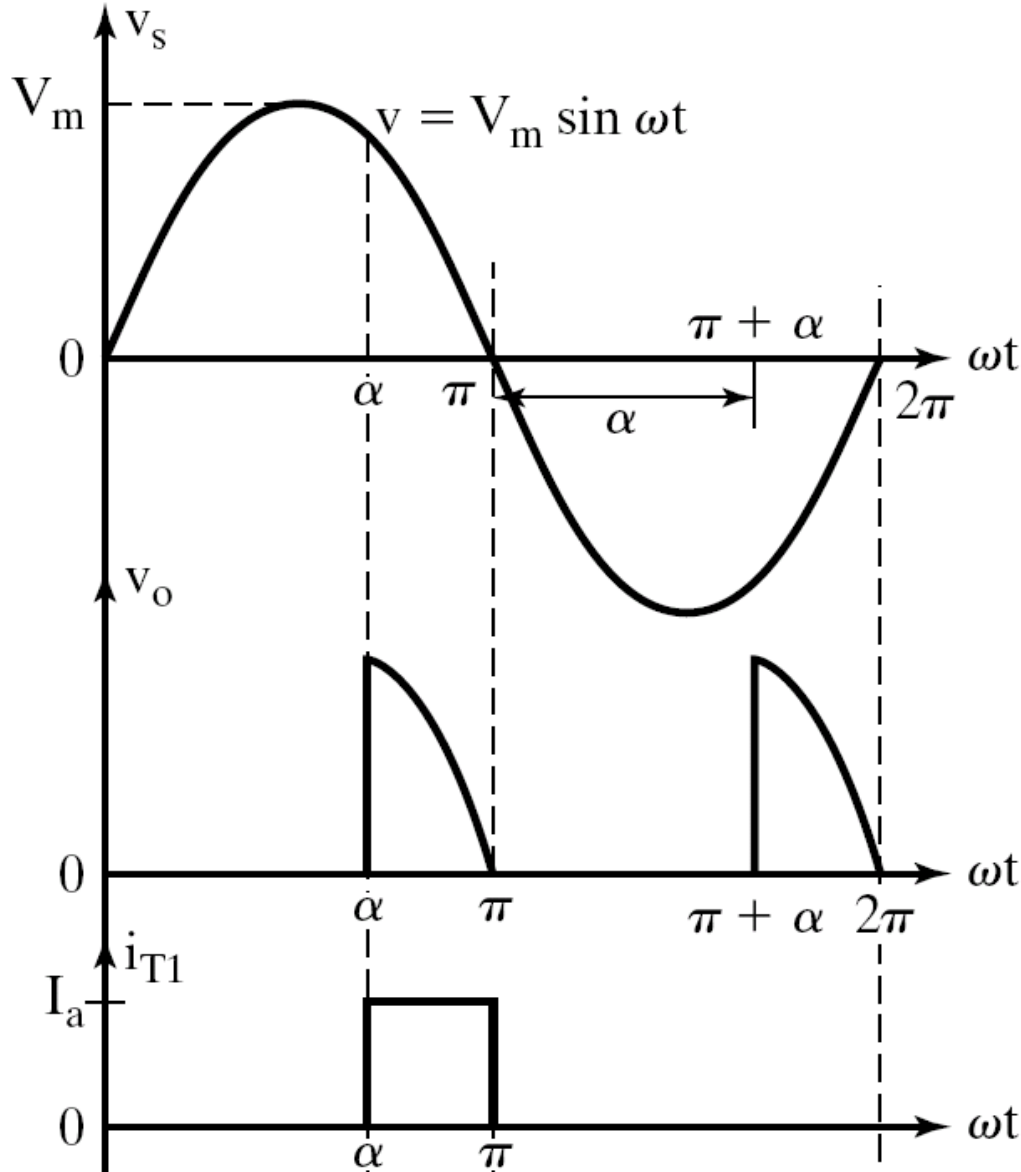Waveforms of  
single phase semi-converter  
with general load & FWD  
for  $\alpha > 90^\circ$



## Single Quadrant Operation

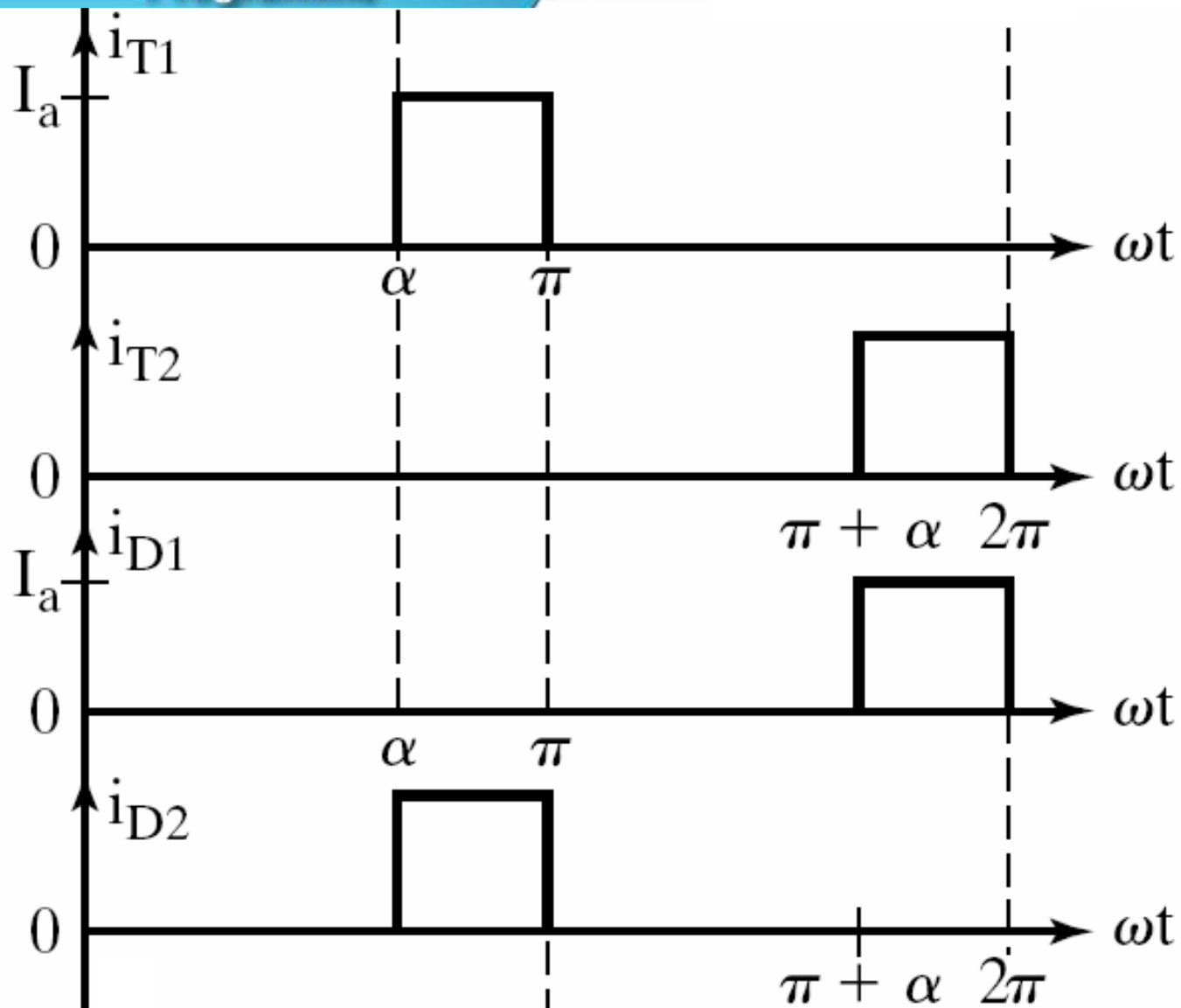

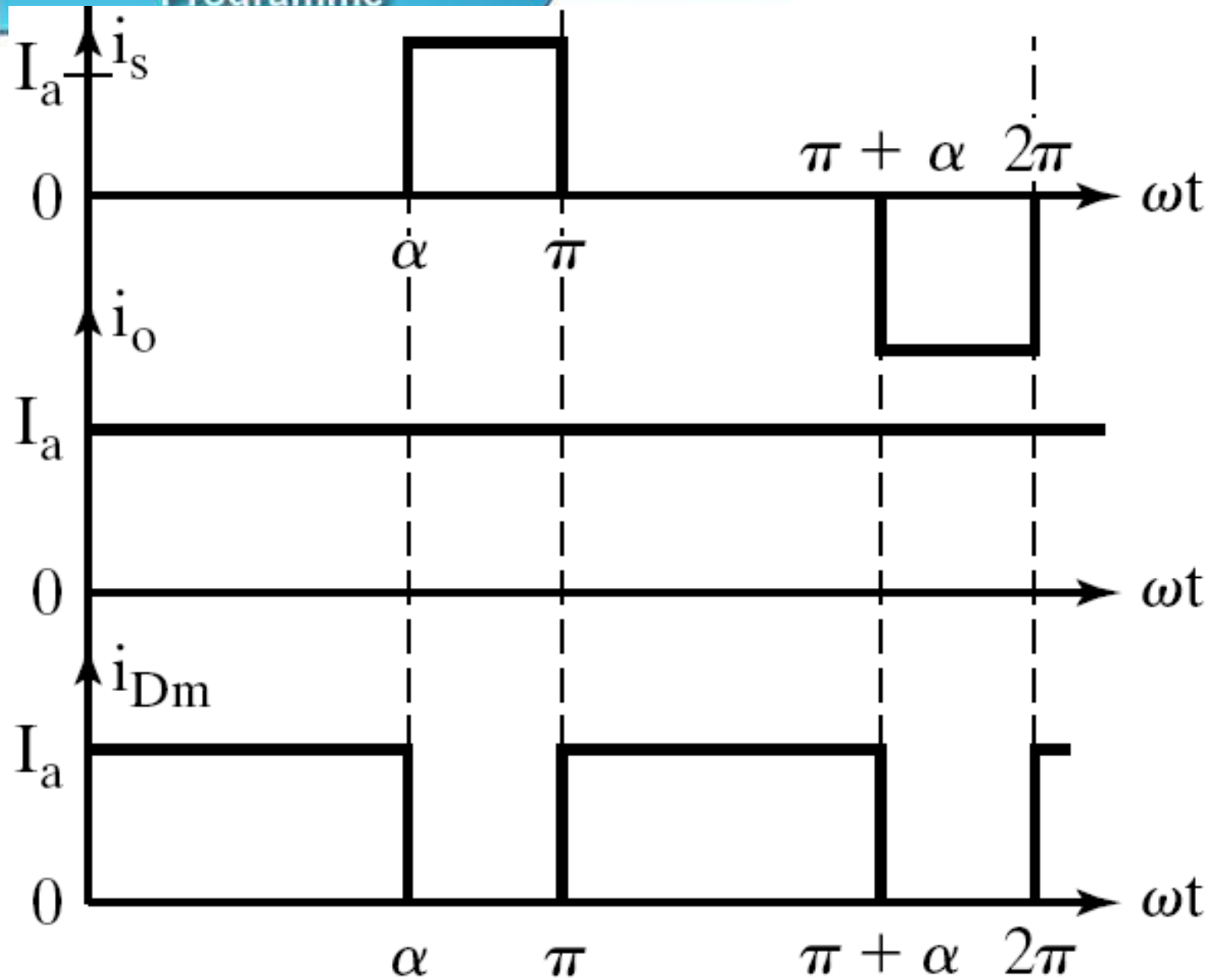



Thyristor  $T_1$  &  $D_1$  conduct

from  $\omega t = \alpha$  to  $\pi$

Thyristor  $T_2$  &  $D_2$  conduct

from  $\omega t = (\pi + \alpha)$  to  $2\pi$


FWD conducts during

$\omega t = 0$  to  $\alpha$ ,  $\pi$  to  $(\pi + \alpha)$ , ...



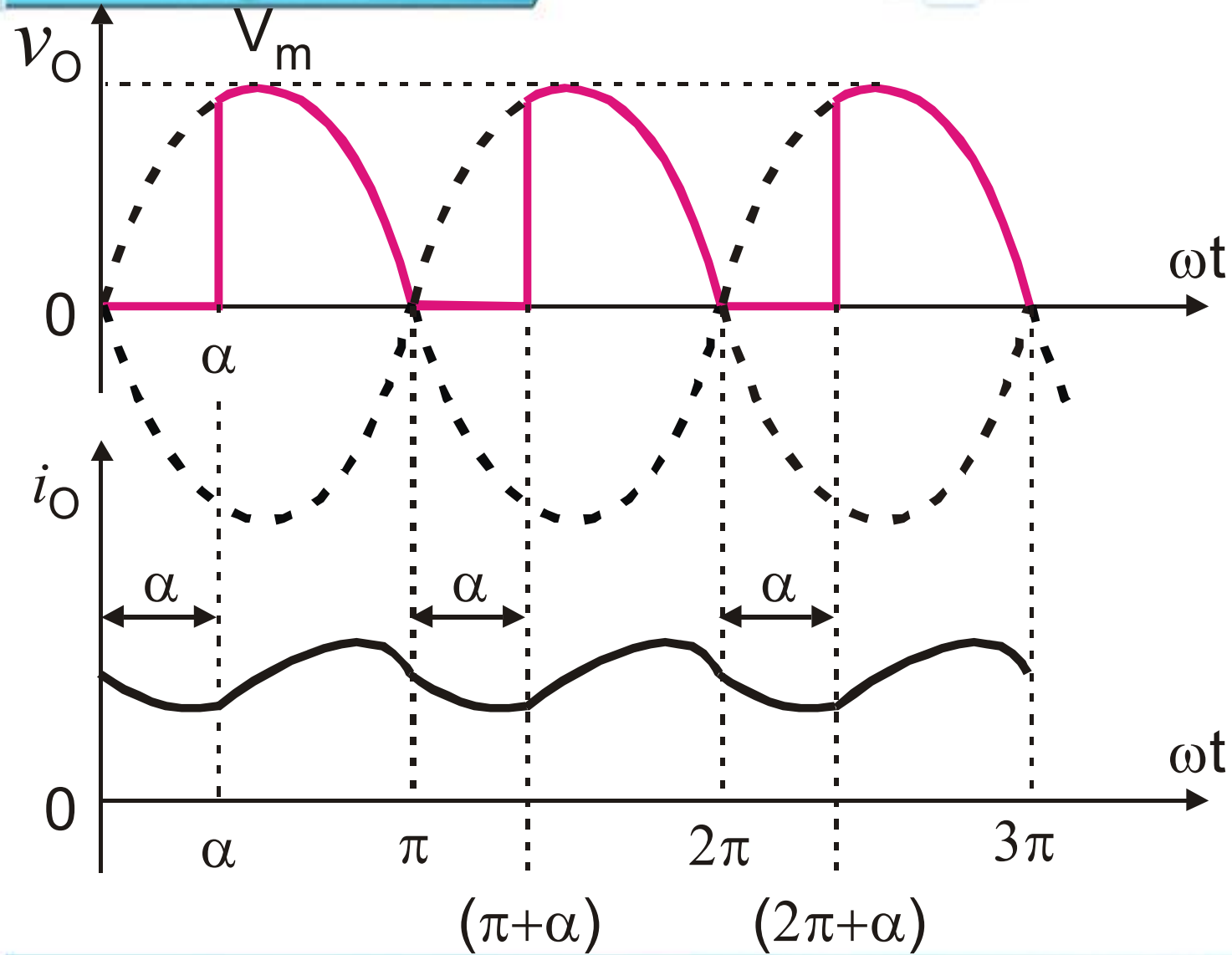Load Voltage & Load Current  
Waveform of Single Phase Semi  
Converter for  
 $\alpha < 90^0$   
& Continuous load current operation







To Derive an Expression  
For The  
DC Output Voltage of  
A  
Single Phase Semi-Converter With  
R,L, & E Load & FWD  
For Continuous, Ripple Free Load  
Current Operation



$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t=0}^{\pi} v_o \cdot d(\omega t)$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ -\cos \omega t \Big|_{\alpha}^{\pi} \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ -\cos \pi + \cos \alpha \right] \quad ; \quad \cos \pi = -1$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} (1 + \cos \alpha)$$



$V_{dc}$  can be varied from a max.

value of  $\frac{2V_m}{\pi}$  to 0 by varying  $\alpha$  from 0 to  $\pi$ .

For  $\alpha = 0$ , The max. dc o/p voltage obtained is

$$V_{dc(\max)} = V_{dm} = \frac{2V_m}{\pi}$$

Normalized dc o/p voltage is

$$V_{dcn} = V_n = \frac{V_{dc}}{V_{dn}} = \frac{V_m (1 + \cos \alpha)}{\pi \left( \frac{2V_m}{\pi} \right)} = \frac{1}{2} (1 + \cos \alpha)$$



## RMS O/P Voltage $V_{O(RMS)}$


$$V_{O(RMS)} = \left[ \frac{2}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \left[ \frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) \cdot d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}} \left[ \frac{1}{\pi} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{\frac{1}{2}}$$



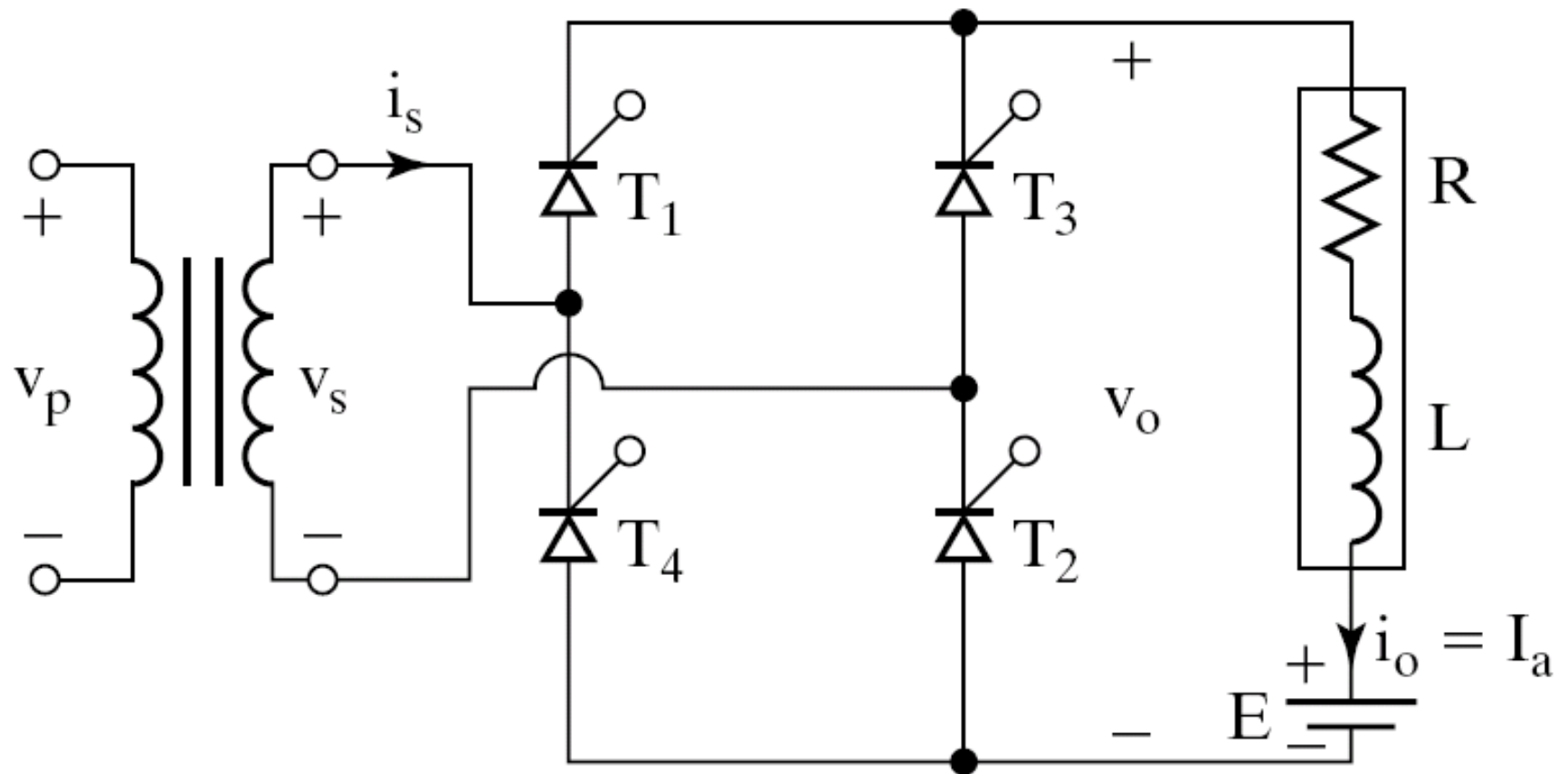
# Single Phase Full Wave Full Converter (Fully Controlled Bridge Converter) With R,L, & E Load






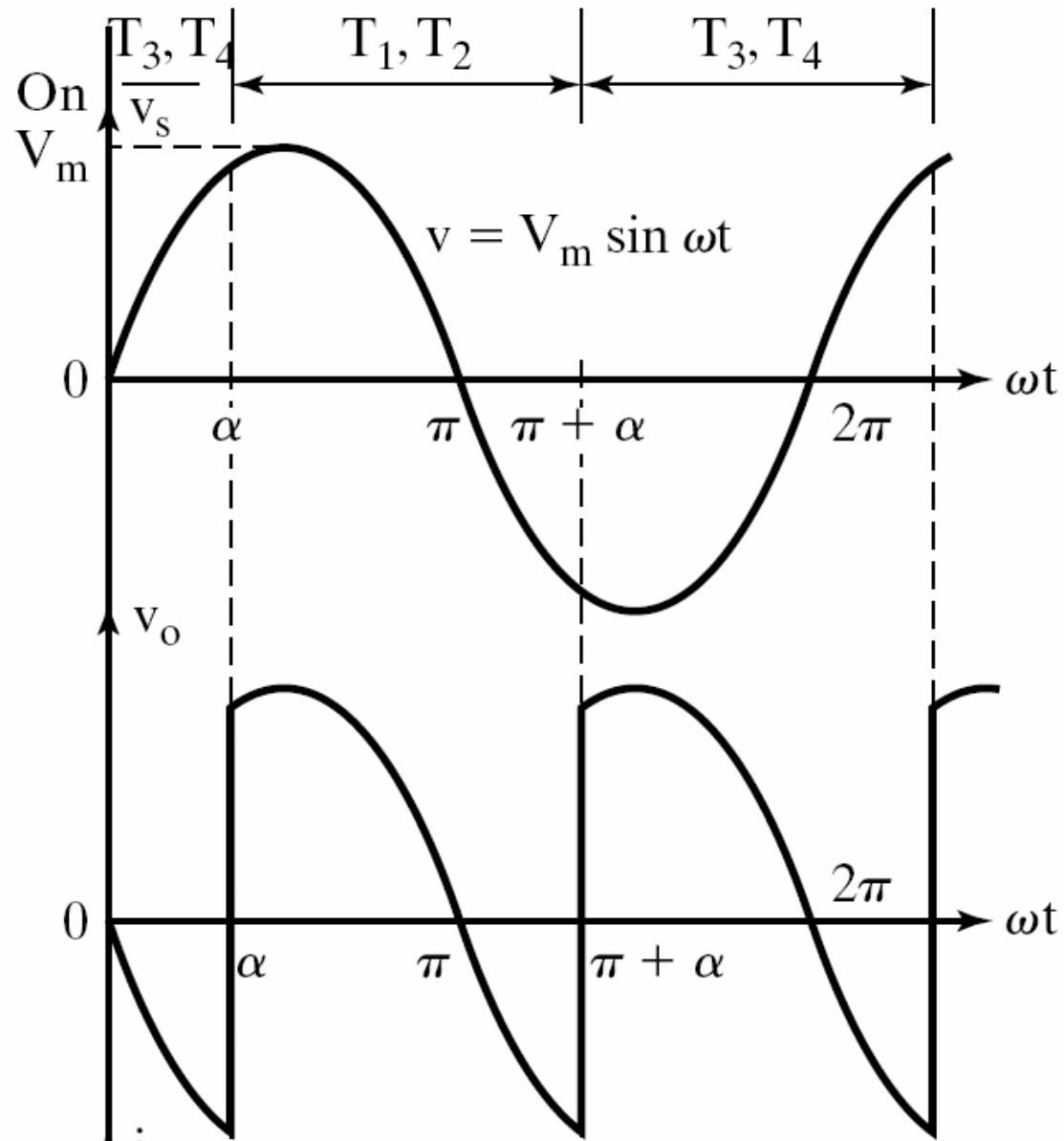
# Waveforms of Single Phase Full Converter Assuming Continuous (Constant Load Current) & Ripple Free Load Current





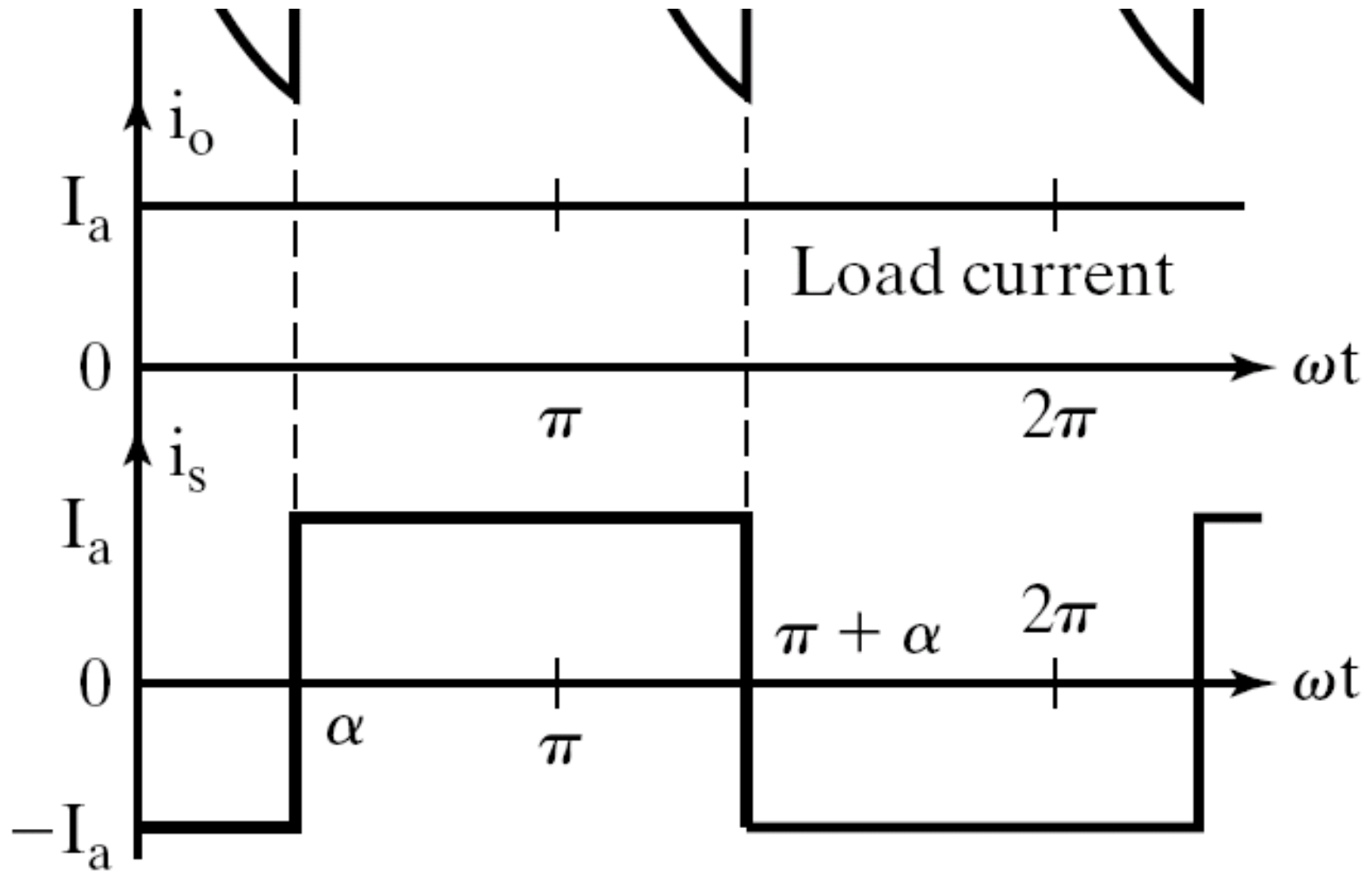

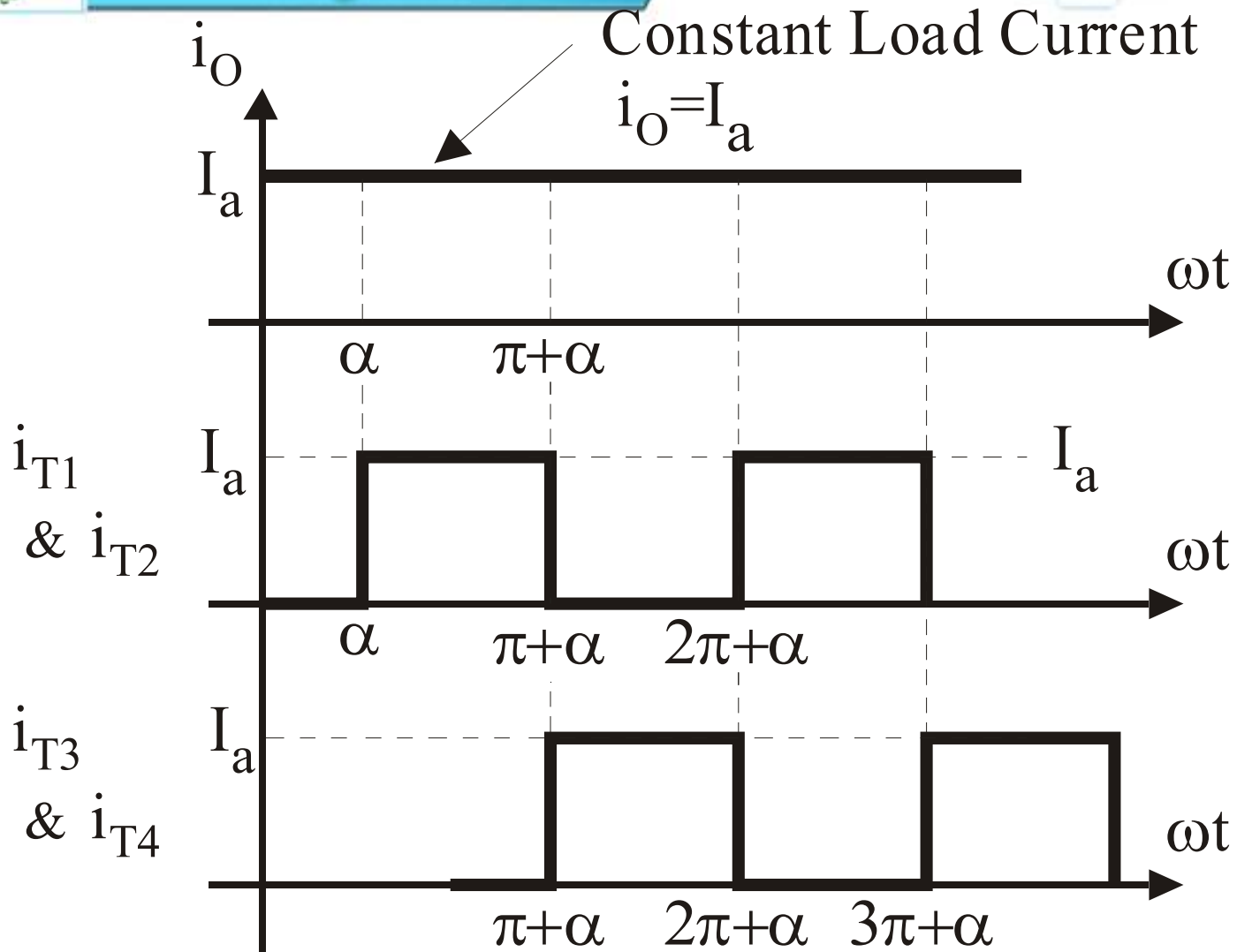



To Derive  
An Expression For  
The Average DC Output Voltage of a  
Single Phase Full Converter  
assuming  
Continuous & Constant Load Current



The average dc output voltage can be determined by using the expression

$$V_{O(dc)} = V_{dc} = \frac{1}{2\pi} \left[ \int_0^{2\pi} v_o \cdot d(\omega t) \right];$$

The o/p voltage waveform consists of two o/p pulses during the input supply time period of 0 to  $2\pi$  radians. Hence the Average or dc o/p voltage can be calculated as



$$V_{O(dc)} = V_{dc} = \frac{2}{2\pi} \left[ \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \cdot d(\omega t) \right]$$

$$V_{O(dc)} = V_{dc} = \frac{2V_m}{2\pi} \left[ -\cos \omega t \right]_{\alpha}^{\pi+\alpha}$$

$$V_{O(dc)} = V_{dc} = \frac{2V_m}{\pi} \cos \alpha$$



Maximum average dc output voltage is calculated for a trigger angle  $\alpha = 0^0$  and is obtained as

$$V_{dc(\max)} = V_{dm} = \frac{2V_m}{\pi} \times \cos(0) = \frac{2V_m}{\pi}$$

$$\therefore V_{dc(\max)} = V_{dm} = \frac{2V_m}{\pi}$$



The normalized average output voltage is given by

$$V_{dcn} = V_n = \frac{V_{O(dc)}}{V_{dc(max)}} = \frac{V_{dc}}{V_{dm}}$$
$$\therefore V_{dcn} = V_n = \frac{\frac{2V_m}{\pi} \cos \alpha}{\frac{2V_m}{\pi}} = \cos \alpha$$





By plotting  $V_{O(dc)}$  versus  $\alpha$ ,  
we obtain the control characteristic of a  
single phase full wave fully controlled  
bridge converter  
(single phase full converter)  
for constant & continuous  
load current operation.




To plot the control characteristic of a Single Phase Full Converter for constant & continuous load current operation.

We use the equation for the average/ dc output voltage

$$V_{O(dc)} = V_{dc} = \frac{2V_m}{\pi} \cos \alpha$$



Trigger angle $\alpha$ in degrees	$V_{O(dc)}$	Remarks
0	$V_{dm} = \left( \frac{2V_m}{\pi} \right)$	Maximum dc output voltage $V_{dc(max)} = V_{dm} = \left( \frac{2V_m}{\pi} \right)$
$30^\circ$	$0.866 V_{dm}$	
$60^\circ$	$0.5 V_{dm}$	
$90^\circ$	$0 V_{dm}$	
$120^\circ$	$-0.5 V_{dm}$	
$150^\circ$	$-0.866 V_{dm}$	
$180^\circ$	$-V_{dm} = -\left( \frac{2V_m}{\pi} \right)$	

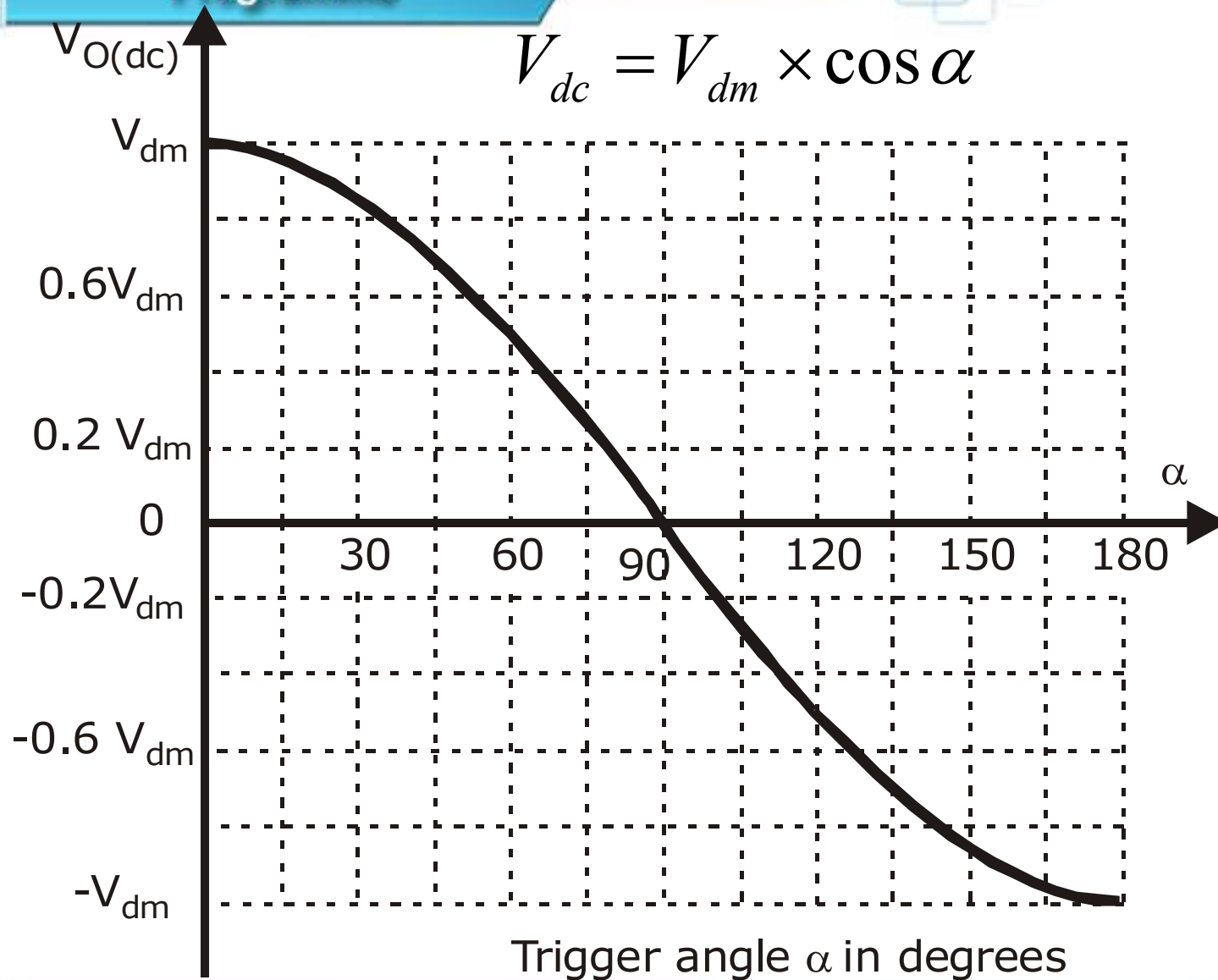



- During the period from  $\omega t = \alpha$  to  $\pi$  the input voltage  $v_s$  and the input current  $i_s$  are both positive and the power flows from the supply to the load.
- The converter is said to be operated in the rectification mode

## Controlled Rectifier Operation

for  $0 < \alpha < 90^\circ$



- During the period from  $\omega t = \pi$  to  $(\pi + \alpha)$ , the input voltage  $v_s$  is negative and the input current  $i_s$  is positive and the output power becomes negative and there will be reverse power flow from the load circuit to the supply.
- The converter is said to be operated in the inversion mode.

## Line Commutated Inverter Operation


for  $90^\circ < \alpha < 180^\circ$



## Two Quadrant Operation of a Single Phase Full Converter

$$0 < \alpha < 90^\circ$$

Controlled Rectifier  
Operation

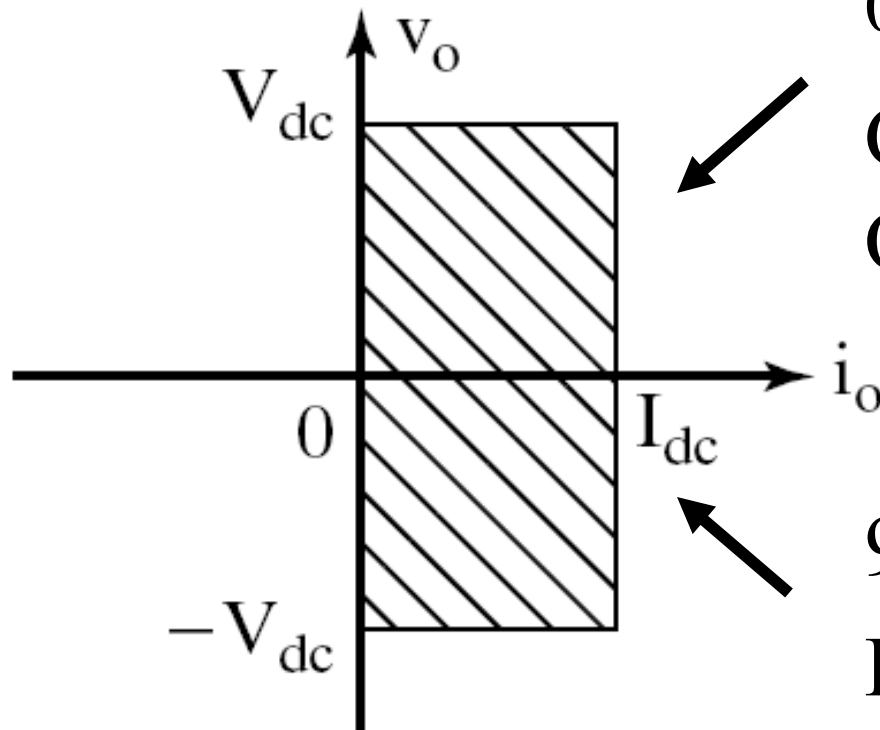

$$90^\circ < \alpha < 180^\circ$$

Line Commutated  
Inverter Operation



## To Derive An Expression For The RMS Value Of The Output Voltage

The rms value of the output voltage  
is calculated as

$$V_{O(RMS)} = \sqrt{\frac{1}{2\pi} \left[ \int_0^{2\pi} v_o^2 \cdot d(\omega t) \right]}$$





The single phase full converter gives two output voltage pulses during the input supply time period and hence the single phase full converter is referred to as a two pulse converter. The rms output voltage can be calculated as

$$V_{O(RMS)} = \sqrt{\frac{2}{2\pi} \left[ \int_{\alpha}^{\pi+\alpha} v_o^2 \cdot d(\omega t) \right]}$$



$$V_{O(RMS)} = \sqrt{\frac{1}{\pi} \left[ \int_{\alpha}^{\pi+\alpha} V_m^2 \sin^2 \omega t . d(\omega t) \right]}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{\pi} \left[ \int_{\alpha}^{\pi+\alpha} \sin^2 \omega t . d(\omega t) \right]}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{\pi} \left[ \int_{\alpha}^{\pi+\alpha} \frac{(1 - \cos 2\omega t)}{2} . d(\omega t) \right]}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{2\pi} \left[ \int_{\alpha}^{\pi+\alpha} d(\omega t) - \int_{\alpha}^{\pi+\alpha} \cos 2\omega t . d(\omega t) \right]}$$



$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{2\pi} \left[ \frac{(\omega t)}{\alpha} \Big|_{\pi+\alpha}^{\pi+\alpha} - \left( \frac{\sin 2\omega t}{2} \right) \Big|_{\alpha}^{\pi+\alpha} \right]}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{2\pi} \left[ (\pi + \alpha - \alpha) - \left( \frac{\sin 2(\pi + \alpha) - \sin 2\alpha}{2} \right) \right]}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{2\pi} \left[ (\pi) - \left( \frac{\sin (2\pi + 2\alpha) - \sin 2\alpha}{2} \right) \right]};$$

$$\sin (2\pi + 2\alpha) = \sin 2\alpha$$



$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{2\pi} \left[ (\pi) - \left( \frac{\sin 2\alpha - \sin 2\alpha}{2} \right) \right]}$$


$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{2\pi} (\pi) - 0} = \sqrt{\frac{V_m^2}{2}} = \frac{V_m}{\sqrt{2}}$$

$$\therefore V_{O(RMS)} = \frac{V_m}{\sqrt{2}} = V_s$$

Hence the rms output voltage is same as the rms input supply voltage



# Thyristor Current Waveforms

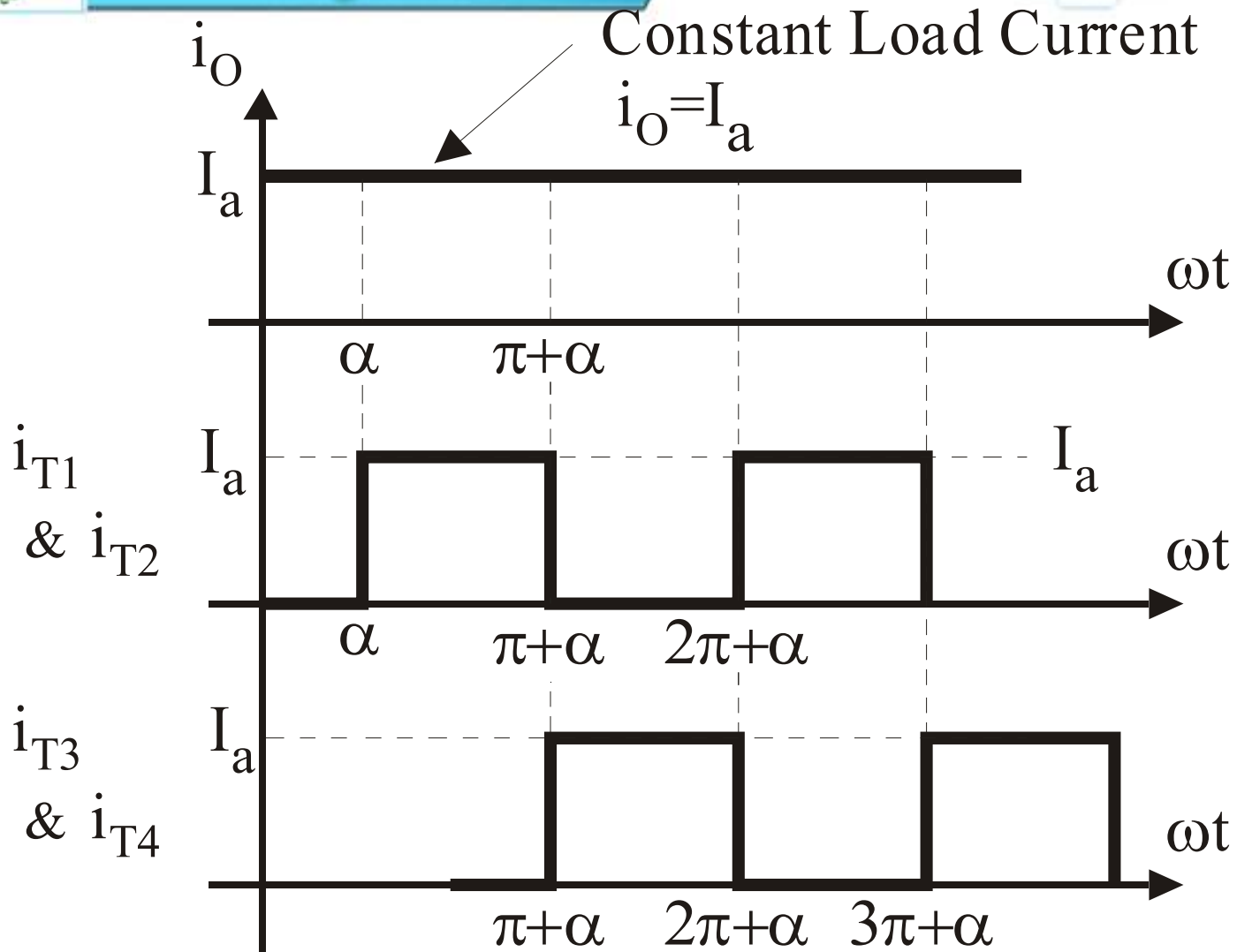



The rms thyristor current can be calculated as


$$I_{T(RMS)} = \frac{I_{O(RMS)}}{\sqrt{2}}$$

The average thyristor current can be calculated as


$$I_{T(Avg)} = \frac{I_{O(dc)}}{2}$$





# Single Phase Dual Converter

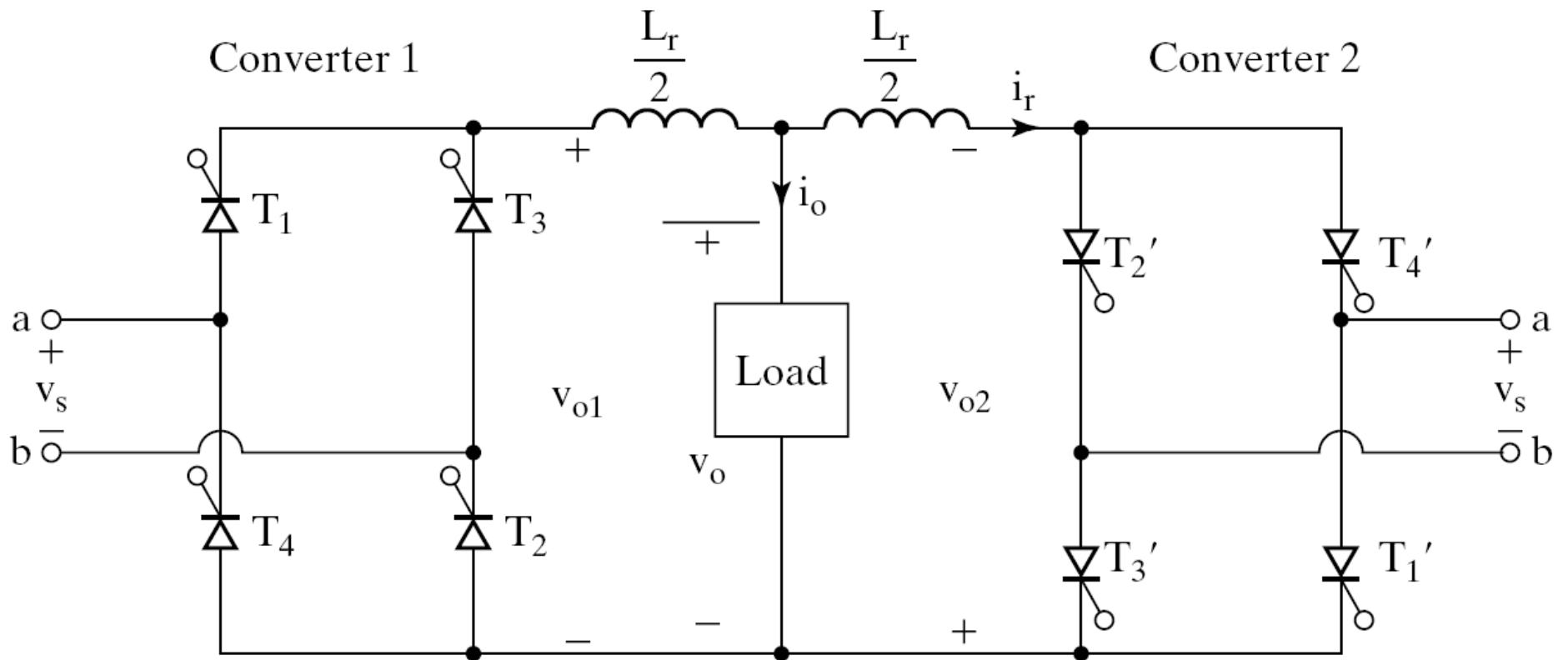



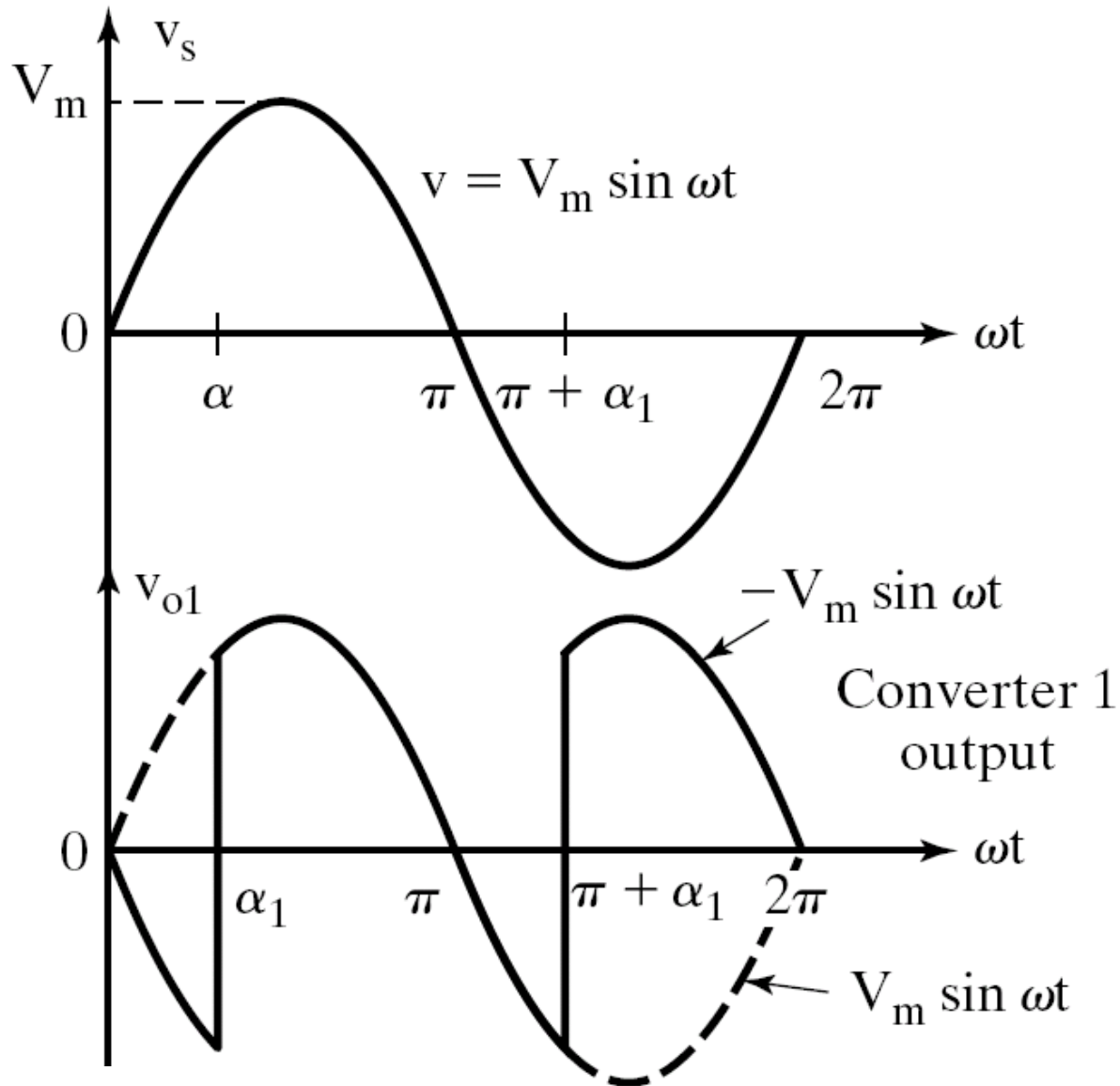

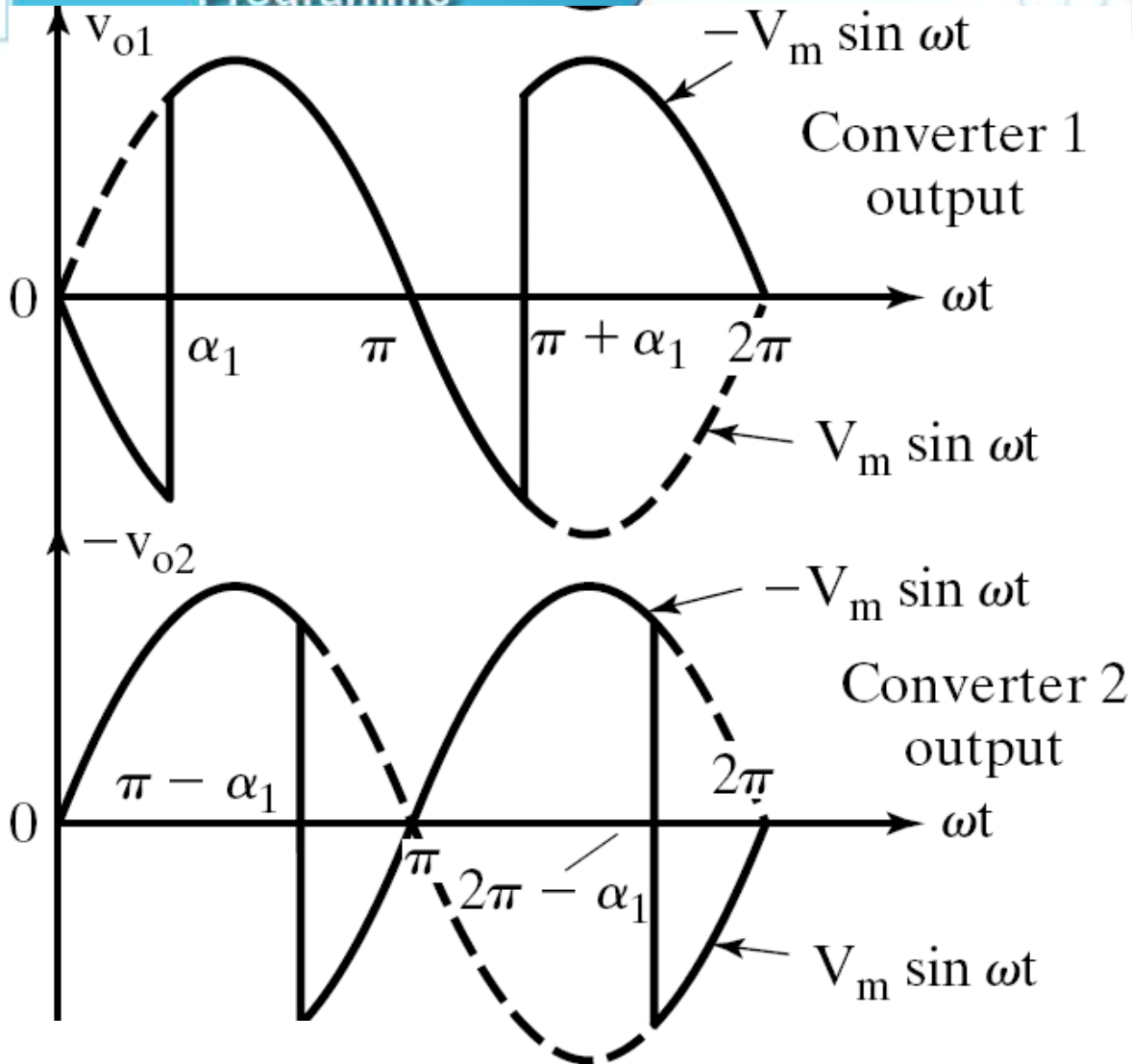

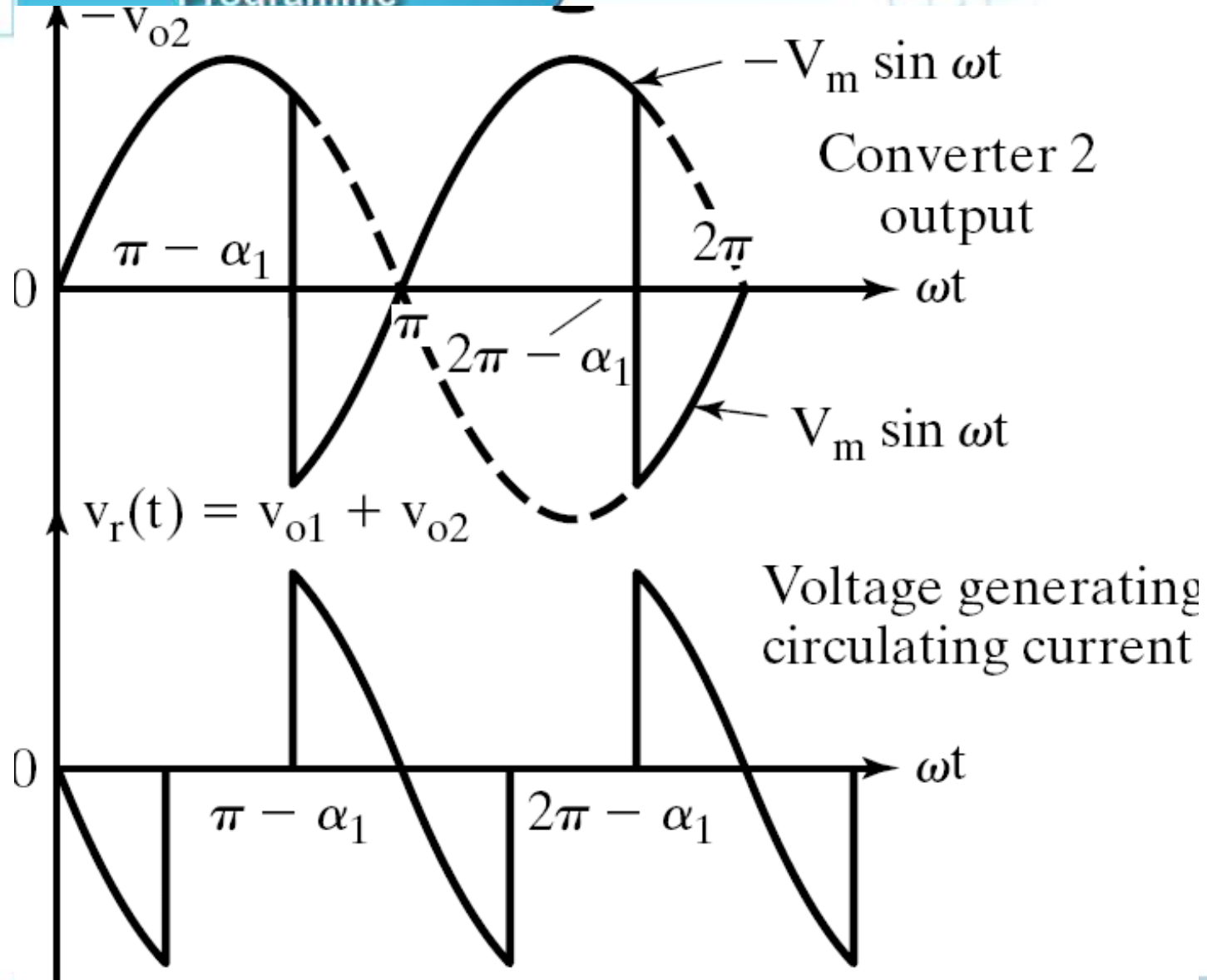



The average dc output voltage of converter 1 is

$$V_{dc1} = \frac{2V_m}{\pi} \cos \alpha_1$$

The average dc output voltage of converter 2 is

$$V_{dc2} = \frac{2V_m}{\pi} \cos \alpha_2$$



In the dual converter operation one converter is operated as a controlled rectifier with  $\alpha < 90^\circ$  & the second converter is operated as a line commutated inverter in the inversion mode with  $\alpha > 90^\circ$

$$\therefore V_{dc1} = -V_{dc2}$$



$$\frac{2V_m}{\pi} \cos \alpha_1 = \frac{-2V_m}{\pi} \cos \alpha_2 = \frac{2V_m}{\pi} (-\cos \alpha_2)$$

$$\therefore \cos \alpha_1 = -\cos \alpha_2$$

or

$$\cos \alpha_2 = -\cos \alpha_1 = \cos(\pi - \alpha_1)$$

$$\therefore \alpha_2 = (\pi - \alpha_1) \text{ or}$$

$$(\alpha_1 + \alpha_2) = \pi \text{ radians}$$

Which gives

$$\alpha_2 = (\pi - \alpha_1)$$



# To Obtain an Expression for the Instantaneous Circulating Current



- $v_{O1}$  = Instantaneous o/p voltage of converter 1.
- $v_{O2}$  = Instantaneous o/p voltage of converter 2.
- The circulating current  $i_r$  can be determined by integrating the instantaneous voltage difference (which is the voltage drop across the circulating current reactor  $L_r$ ), starting from  $\omega t = (2\pi - \alpha_1)$ .
- As the two average output voltages during the interval  $\omega t = (\pi + \alpha_1)$  to  $(2\pi - \alpha_1)$  are equal and opposite their contribution to the instantaneous circulating current  $i_r$  is zero.





$$i_r = \frac{1}{\omega L_r} \left[ \int_{(2\pi - \alpha_1)}^{\omega t} v_r \cdot d(\omega t) \right]; \quad v_r = (v_{O1} - v_{O2})$$

As the o/p voltage  $v_{O2}$  is negative

$$v_r = (v_{O1} + v_{O2})$$

$$\therefore i_r = \frac{1}{\omega L_r} \left[ \int_{(2\pi - \alpha_1)}^{\omega t} (v_{O1} + v_{O2}) \cdot d(\omega t) \right];$$

$$v_{O1} = -V_m \sin \omega t \text{ for } (2\pi - \alpha_1) \text{ to } \omega t$$



$$i_r = \frac{V_m}{\omega L_r} \left[ \int_{(2\pi - \alpha_1)}^{\omega t} -\sin \omega t . d(\omega t) - \int_{(2\pi - \alpha_1)}^{\omega t} \sin \omega t . d(\omega t) \right]$$

$$i_r = \frac{2V_m}{\omega L_r} (\cos \omega t - \cos \alpha_1)$$

The instantaneous value of the circulating current depends on the delay angle.



For trigger angle (delay angle)  $\alpha_1 = 0$ ,  
the magnitude of circulating current becomes min.  
when  $\omega t = n\pi$ ,  $n = 0, 2, 4, \dots$  & magnitude becomes  
max. when  $\omega t = n\pi$ ,  $n = 1, 3, 5, \dots$

If the peak load current is  $I_p$ , one of the  
converters that controls the power flow  
may carry a peak current of

$$\left( I_p + \frac{4V_m}{\omega L_r} \right),$$



where

$$I_p = I_{L(\max)} = \frac{V_m}{R_L},$$

&

$$i_{r(\max)} = \frac{4V_m}{\omega L_r} = \text{max. circulating current}$$



# The Dual Converter Can Be Operated In Two Different Modes Of Operation

- Non-circulating current (circulating current free) mode of operation.
- Circulating current mode of operation.



## Non-Circulating Current Mode of Operation

- In this mode only one converter is operated at a time.
- When converter 1 is ON,  $0 < \alpha_1 < 90^\circ$
- $V_{dc}$  is positive and  $I_{dc}$  is positive.
- When converter 2 is ON,  $0 < \alpha_2 < 90^\circ$
- $V_{dc}$  is negative and  $I_{dc}$  is negative.



## Circulating Current Mode Of Operation

- In this mode, both the converters are switched ON and operated at the same time.
- The trigger angles  $\alpha_1$  and  $\alpha_2$  are adjusted such that  $(\alpha_1 + \alpha_2) = 180^\circ$  ;  $\alpha_2 = (180^\circ - \alpha_1)$ .



- When  $0 < \alpha_1 < 90^\circ$ , converter 1 operates as a controlled rectifier and converter 2 operates as an inverter with  $90^\circ < \alpha_2 < 180^\circ$ .
- In this case  $V_{dc}$  and  $I_{dc}$ , both are positive.
- When  $90^\circ < \alpha_1 < 180^\circ$ , converter 1 operates as an Inverter and converter 2 operated as a controlled rectifier by adjusting its trigger angle  $\alpha_2$  such that  $0 < \alpha_2 < 90^\circ$ .
- In this case  $V_{dc}$  and  $I_{dc}$ , both are negative.






# Four Quadrant Operation

Conv. 2  
Inverting  
 $\alpha_2 > 90^\circ$

Conv. 2  
Rectifying  
 $\alpha_2 < 90^\circ$

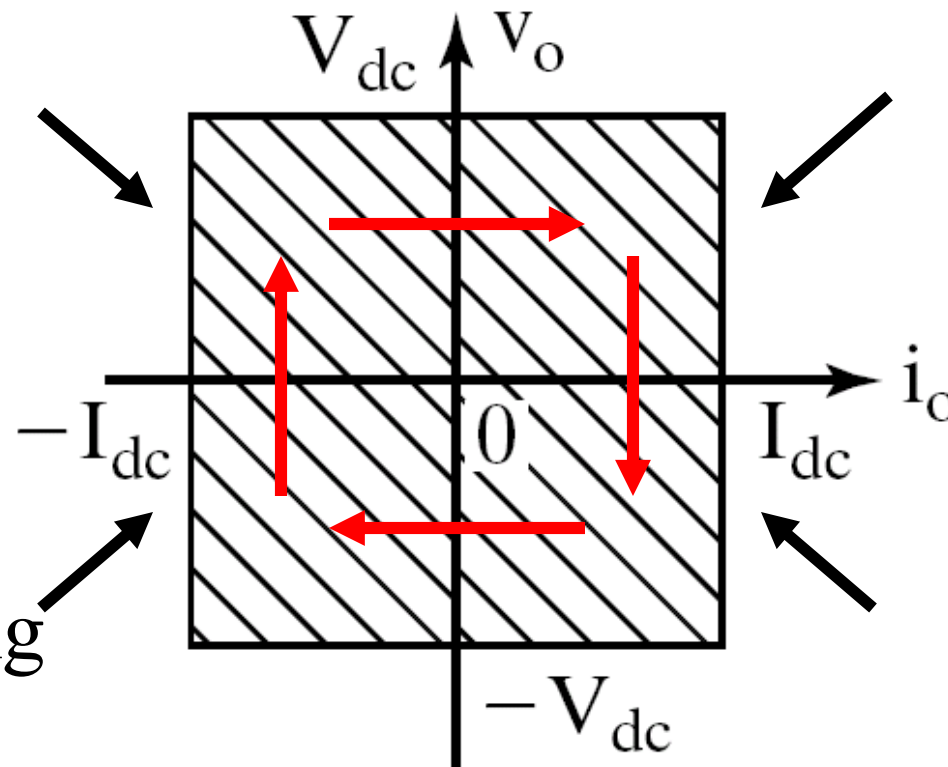

Conv. 1  
Rectifying  
 $\alpha_1 < 90^\circ$

Conv. 1  
Inverting  
 $\alpha_1 > 90^\circ$



## Advantages of Circulating Current Mode Of Operation

- The circulating current maintains continuous conduction of both the converters over the complete control range, independent of the load.
- One converter always operates as a rectifier and the other converter operates as an inverter, the power flow in either direction at any time is possible.



- As both the converters are in continuous conduction we obtain faster dynamic response. i.e., the time response for changing from one quadrant operation to another is faster.



## Disadvantages of Circulating Current Mode Of Operation

- There is always a circulating current flowing between the converters.
- When the load current falls to zero, there will be a circulating current flowing between the converters so we need to connect circulating current reactors in order to limit the peak circulating current to safe level.
- The converter thyristors should be rated to carry a peak current much greater than the peak load current.