

Programmable Logic Controllers (PLC):

PLC is the single most widely used industrial controller.

Acc. to the standards, "A Prog. controller is a digitally operated electronic apparatus that uses a programmable memory for the internal storage of instructions that implement specific functions such as logic, sequence, timing, counting and arithmetic to control machines and processes"

Relays can easily handle high currents needed to operate actuators and work conveniently on the 230 V ac. However, the relays are

- (i) subject to mechanical fatigue
- (ii) failure rates in relay systems were higher
- (iii) trouble shooting is difficult
- (iv) it is most discouraging when we must scrap the entire relay based system at the end of every year to accommodate new models.

PLCs have evolved now into a computer system with a wide assortment of capabilities such as arithmetic operations, D/A converters, data comparisons and equations solving. Two additional functions include communications with the operator and communications with a distributed control system.



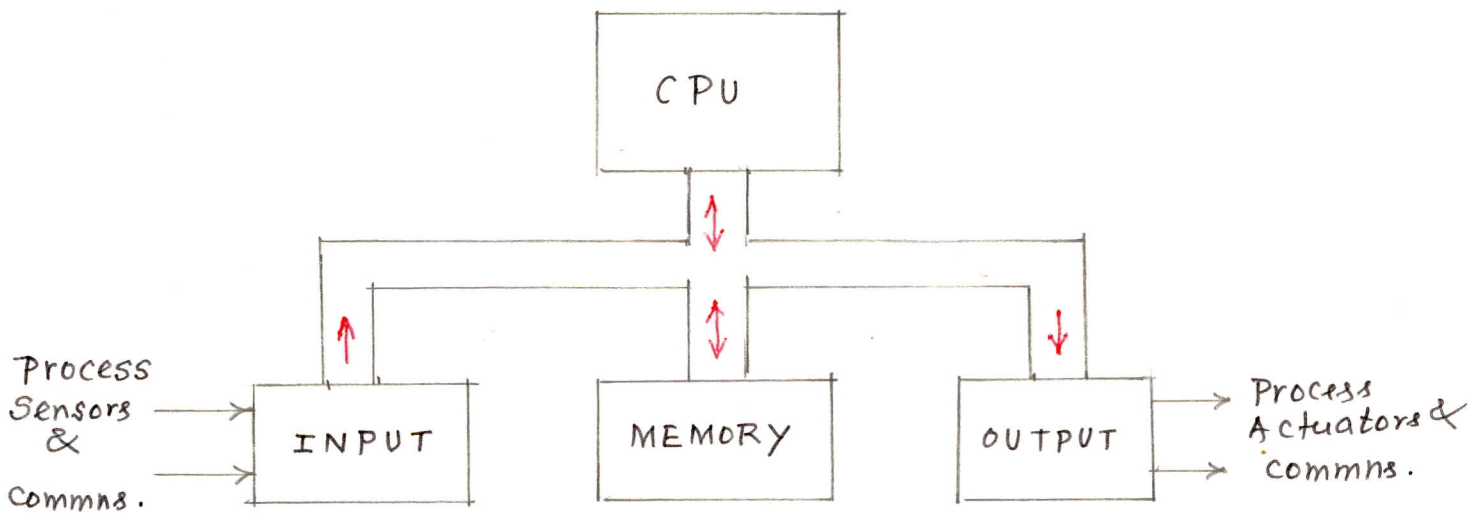


Fig.1 BLOCK DIAGRAM OF PLC

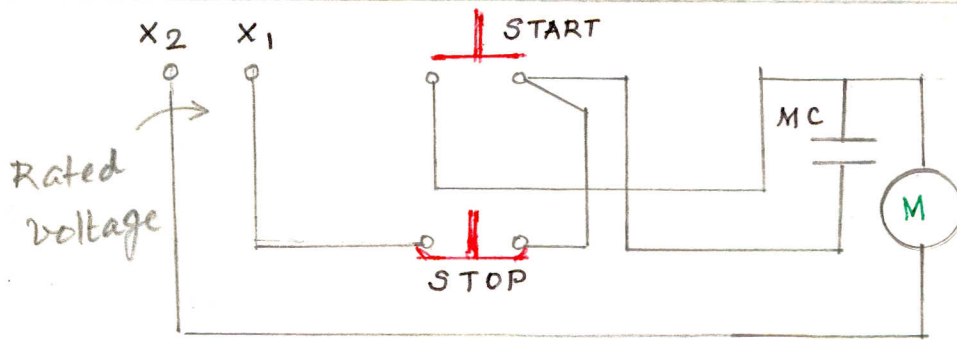

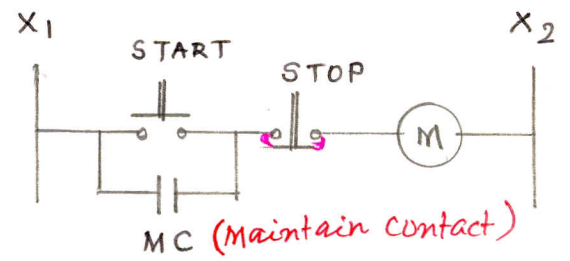
(a) Electrical Schematic

Whenever the power is applied, the MC contacts are closed; this places a closed parallel path around the start button.



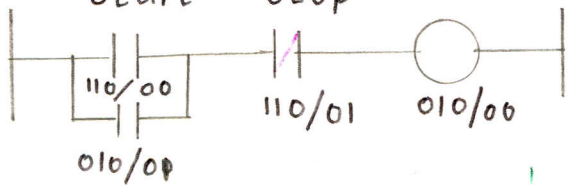(b) Relay Ladder Logic diagram

Parallel Connection: Logic OR
Series Connection: Logic AND



(c) PLC Programming

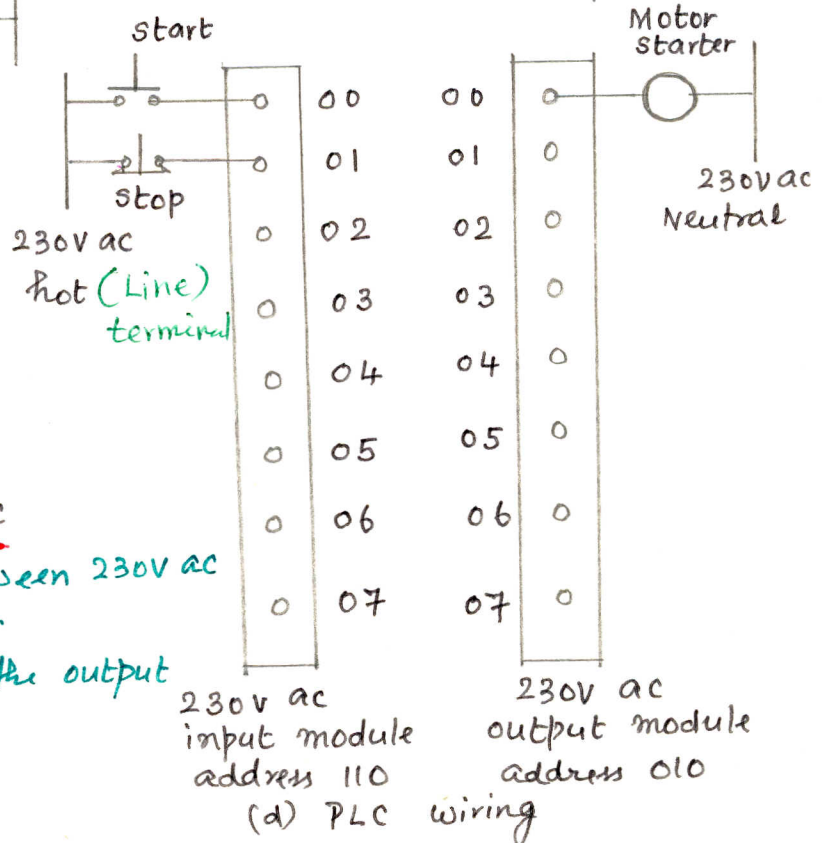


Fig.2

MOTOR STARTER LOGIC

The contacts are connected between 230V ac hot line and PLC's input module.

Loads are connected between the output module & the 230V ac neutral.

(d) PLC wiring

Operational Procedure and Ladder Logic diagram

To program a PLC to accomplish the following task:

A Relay coil is to actuate when two switches are actuated.


Step 1: Assign PLC identification numbers to the inputs and outputs, as follows:

Switch 1 = IN 01


Switch 2 = IN 02

Relay output = O 01

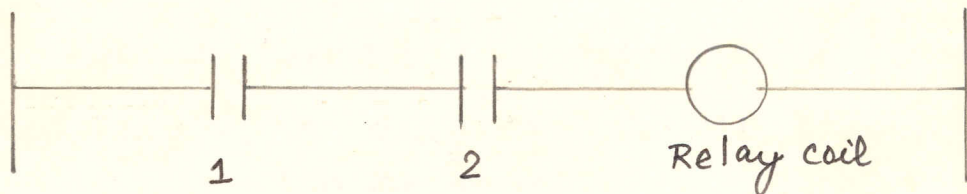
Step 2: Sketch a ladder logic diagram to represent the circuit



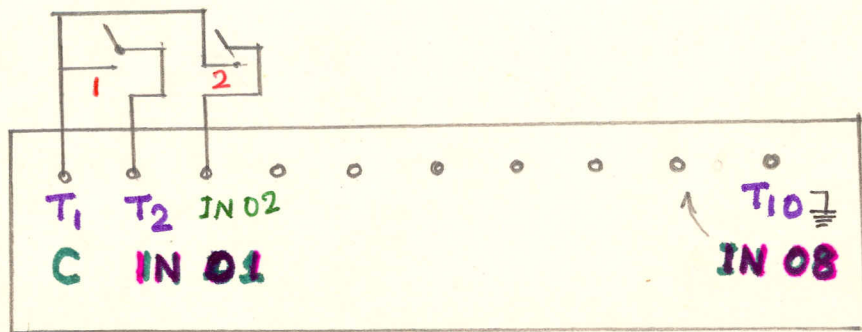Step 3: Make the connections from inputs and outputs.
(No external interconnections are made)



Input module

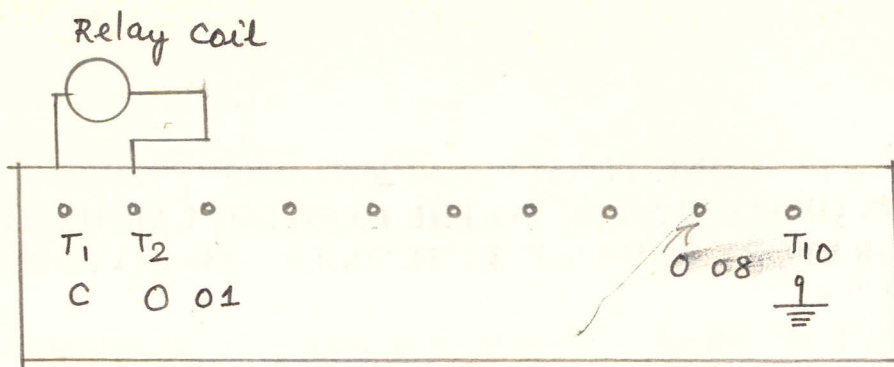

OUTPUT MODULE

Step 4 : Finally the ladder diagram must be entered in the CPU by means of the key board

(i) CLEAR (ii) EDIT MODE (iii) Push the INPUT key first

(iv) type 01 (v) ENTER : Now the contact will appear in the monitor


(vi) Move the cursor one space to the right

(vii) Push INPUT key (viii) Type 02 (ix) ENTER & Now

the second contact will appear on the screen &

the resulting PLC diagram is as shown below :
(on the screen)

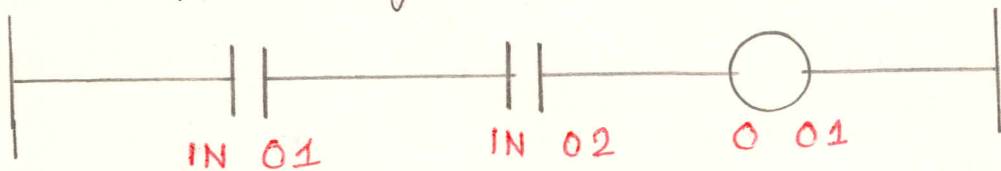(ix) one space to right; output key; type 01; ENTER




Step 5 : PLC is set in the RUN Mode.

Ladder Logic diagram :

Battery o/p directly connected to X001
 X001: Jo sense
 $V_B > 10V$.

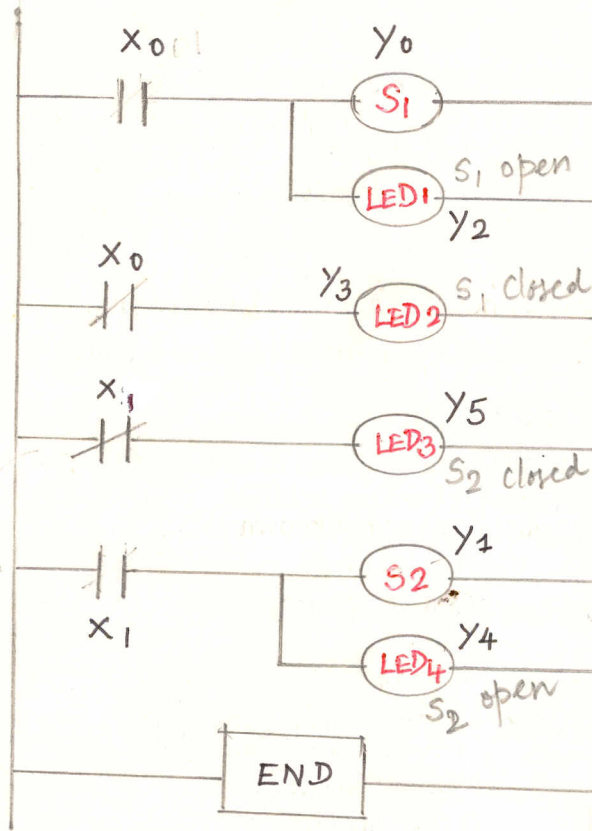Battery o/p thro Pot to : X000
 X000: Jo sense
 $V_B > 14V$



(i) X0 is connected to the output of solar panel

\therefore when the voltage at X0 is $< 14V$; (it gets closed) it closes Y0

The battery is connected to the output terminal Y0

Hence when X0 is High, both Y0 & Y2 are closed;

Y0 connects the battery to solar panel & Y2 lights an LED to indicate closure of Y0 (S1)

When X0 is Low ($> 14V$), battery should be isolated from the solar panel (thru S1, i.e., S1 is open thru Y3)

(ii) Why X1 is connected to output of the battery & when the

battery voltage falls below 10V, X1 goes High; on sensing this the load which is connected to the output of the battery is disconnected thru a switch S2 (which is connected to output port Y5).

When S2 is open, it is in

Hardware connections :

(i) The battery voltage is connected directly to input port X001. This is used to check whether the battery voltage has fallen below 10V or not.

(ii) The input to channel (port) X000 is given from the battery after passing it thro' the potentiometer.

The pot is set in such a way that when the battery voltage exceeds 14V, the input X000 goes high.

Program :

Position	Mnemonics	device	Remarks
0	LDI (NC)	X000	Signal for activating S_1 (High)
1	OUT	Y000	To open S_1
2	OUT	Y002	To indicate S_1 open (LED)
3	LD (NO)	X000	signal for activating S_1 (Low)
4	OUT	Y003	To close S_1
5	LDI	X001	Signal for activating S_2 (High)
6	OUT	Y005	To open S_2
7	LD	X001	Low signal for activating S_2
8	OUT	Y001	To close S_2
9	OUT	Y004	To indicate S_2 is closed
10	END		

(iii) When the battery voltage exceeds 10V, X_1 goes High; on sensing this signal, the load is connected to the output of the battery thro' S_2 closing which is done by output port Y_1 . The closing of S_2 is indicated by an LED lighted by a signal from Y_4 .