

## Some Applications

Several applications of power electronics are listed in Art 1.2. Study of all these applications will be a voluminous task. Even then, some of these applications described in this chapter will be of interest to the reader.

### 11.1. SWITCHED MODE POWER SUPPLY (SMPS)

With advances in electronics, need for dc power supplies for use in integrated circuits (ICs) and digital circuits has increased manifold. For such electronic circuits, NASA was the first to develop a light-weight and compact switched mode power supply in the 1960s for use in its space vehicles. Subsequently, this power supply became popular and presently, annual production of SMPSs may be as high as 70 to 80% of the total number power supplies produced.

At this juncture, a question may arise that controlled dc supply can also be obtained from phase-controlled rectifiers. Then why go in for SMPS? An ac to dc rectifier operates at supply frequency of 50 (or 60) Hz. In order to obtain almost negligible ripple in the dc output voltage, physical size of filter circuits required is quite large. This makes the dc power supply inefficient, bulky and weighty. On the other hand, SMPS works like a dc chopper. By operating the on/off switch very rapidly, ac ripple frequency rises which can be easily filtered by  $L$  and  $C$  filter circuits which are small in size and less weighty. It may therefore be inferred that it is the requirement of small physical size and weight that has led to the wide spread use of SMPSs.

As stated above, SMPS is based on the chopper principle. The output dc voltage is controlled by varying the duty cycle of chopper by PWM or FM techniques. The circuit configurations used for SMPS can be classified into four broad categories; namely flyback, pushfull, half bridge and full-bridge.

In SMPS circuits discussed here, PWM technique is used for the inverter. The output of the inverter is then converted to dc by a diode rectifier. As the inverter is made to operate at very high frequency, the ripples on the dc output voltage can be filtered out easily by using small filter components. If the switching devices are power transistors, the chopping frequency is limited to 40 kHz. For power MOSFETs, the chopping frequency is of the order of 200 kHz; as a result, size of the filter circuit and transformer decreases leading to considerable savings. At such high frequency, ferrite core is used in transformers.

The four categories of SMPSs listed above are now discussed briefly.

#### 11.1.1. Flyback Converter

The circuit configuration for flyback converter is shown in Fig. 11.1. It consists of a power MOSFET  $M_1$ , transformer for isolation purposes, diode  $D$ , capacitor  $C$  and load. An

uncontrolled rectifier converts ac to dc output which is fed to flyback SMPS as shown in Fig. 11.1.

When power MOSFET is turned on, supply voltage  $V_s$  is applied to the transformer primary, i.e.  $v_1 = V_s$ . A corresponding voltage  $v_2$ , with the polarity as shown in Fig. 11.2(a), is induced in the transformer secondary, i.e.  $v_2 = \frac{V_s}{N_1} N_2$ . As  $v_2$  reverse biases diode  $D$ , equivalent circuit of Fig. 11.2(a) is obtained. Filter capacitance  $C$  is assumed large enough so that capacitor voltage  $v_c(t) =$  load or output voltage  $V_0$  is taken as almost constant. When M1 is turned off, a voltage of opposite polarity is induced in primary and secondary windings as shown in Fig. 11.2(b). Voltage across transformer secondary is  $v_2 = -V_0 = -\frac{V_s}{N_1} N_2$ . Diode  $D$  is forward biased and starts conducting a current  $i_D$ . As a result, energy stored in the transformer core is delivered partly to load and partly to charge the capacitor  $C$ .

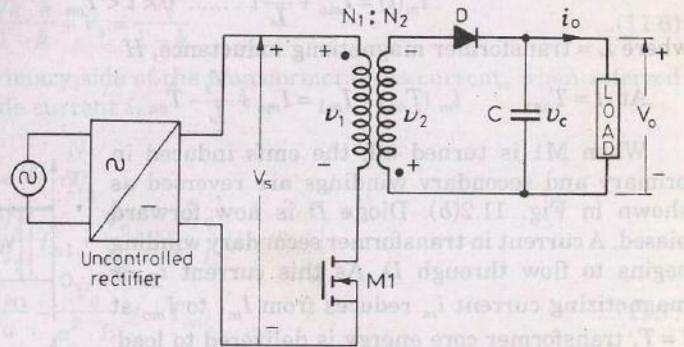


Fig. 11.1. Flyback SMPS.

When M1 is turned on, supply voltage  $V_s$  is applied to the transformer primary, i.e.  $v_1 = V_s$ . A corresponding voltage  $v_2$ , with the polarity as shown in Fig. 11.2(a), is induced in the transformer secondary, i.e.  $v_2 = \frac{V_s}{N_1} N_2$ . As  $v_2$  reverse biases diode  $D$ , equivalent circuit of Fig. 11.2(a) is obtained. Filter capacitance  $C$  is assumed large enough so that capacitor voltage  $v_c(t) =$  load or output voltage  $V_0$  is taken as almost constant. When M1 is turned off, a voltage of opposite polarity is induced in primary and secondary windings as shown in Fig. 11.2(b). Voltage across transformer secondary is  $v_2 = -V_0 = -\frac{V_s}{N_1} N_2$ . Diode  $D$  is forward biased and starts conducting a current  $i_D$ . As a result, energy stored in the transformer core is delivered partly to load and partly to charge the capacitor  $C$ .

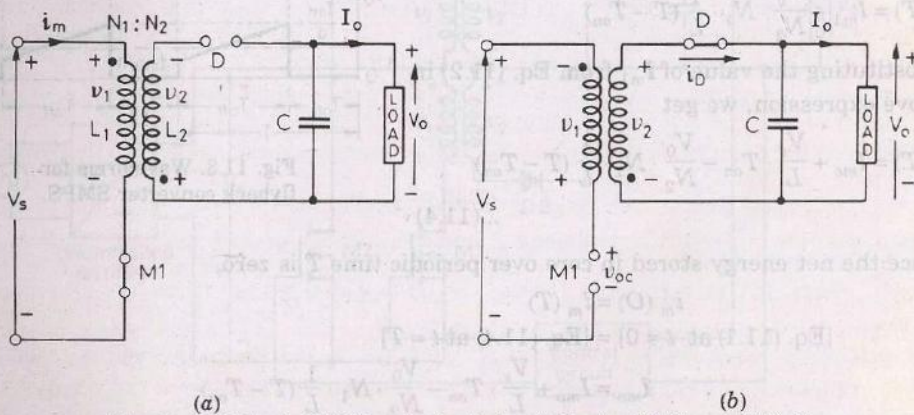


Fig. 11.2. Flyback SMPS equivalent circuit during (a)  $T_{on}$  and (b)  $T_{off}$

Waveforms for  $v_1$ ,  $v_2$ , transformer magnetizing current  $i_m$  and diode current  $i_D$  are shown in Fig. 11.3. During the time M1 is on,  $v_1 = V_s$ ,  $v_2 = \frac{V_s}{N_1} N_2$ . For magnetizing current, it is assumed that transformer core is not demagnetized completely at the end of periodic time  $T = T_{on} + T_{off}$ . In other words, it means that transformer magnetizing current at  $t = 0$  is not zero but has some positive value  $I_{m0}$ . Therefore, during  $T_{on}$ , magnetizing current rises linearly from its initial value  $I_{m0}$  to  $I_{m1}$  at  $t = T_{on}$ . With the rise of  $i_m$  during  $T_{on}$ , magnetic energy gets

stored in the transformer core. The variation of  $i_m$  as shown in Fig. 11.3 can be expressed as under :

$$i_m(t) = I_{m0} + \frac{V_s}{L} t \dots\dots 0 < t < T_{on} \dots\dots(11.1)$$

where  $L$  = transformer magnetizing inductance,  $H$

At  $t = T_{on}$ ,  $i_m(T_{on}) = I_{m1} = I_{m0} + \frac{V_s}{L} \cdot T_{on} \dots\dots(11.2)$

When M1 is turned off, the emfs induced in primary and secondary windings are reversed as shown in Fig. 11.2(b). Diode  $D$  is now forward biased. A current in transformer secondary winding begins to flow through  $D$ . As this current  $i_D$  or magnetizing current  $i_m$  reduces from  $I_{m1}$  to  $I_{m0}$  at  $t = T$ , transformer core energy is delivered to load. During  $T_{off}$ , M1 is off and  $v_2 = -V_0$ . This voltage when referred to primary is  $v_1 = -\frac{V_0}{N_2} N_1$ . The fall of current  $i_m$  during  $T_{off}$  can be expressed as under:

$$i_m(t) = I_{m1} - \frac{V_0}{N_2} N_1 \cdot \frac{1}{L} (t - T_{on}) \dots\dots T_{on} < t < T \dots\dots(11.3)$$

At  $t = T$ ,

$$i_m(T) = I_{m1} - \frac{V_0}{N_2} \cdot N_1 \cdot \frac{1}{L} (T - T_{on})$$

Substituting the value of  $I_{m1}$  from Eq. (11.2) in the above expression, we get

$$i_m(T) = I_{m0} + \frac{V_s}{L} \cdot T_{on} - \frac{V_0}{N_2} \cdot N_1 \cdot \frac{1}{L} (T - T_{on}) \dots\dots(11.4)$$

Since the net energy stored in core over periodic time  $T$  is zero,

$$i_m(0) = i_m(T)$$

or [Eq. (11.1) at  $t = 0$ ] = [Eq. (11.4) at  $t = T$ ]

$$I_{m0} = I_{m0} + \frac{V_s}{L} \cdot T_{on} - \frac{V_0}{N_2} \cdot N_1 \cdot \frac{1}{L} (T - T_{on})$$

or  $V_s \cdot T_{on} = \frac{V_0}{a} (T - T_{on})$

$\therefore$  Load voltage,  $V_0 = \frac{a \cdot V_s \cdot T_{on}}{T - T_{on}} = \frac{a \cdot V_s \cdot k}{1 - k} \dots\dots(11.5)$

where  $a = \frac{N_2}{N_1}$ , transformer turns ratio from secondary to primary

and  $k = \frac{T_{on}}{T}$ , duty cycle of flyback converter.

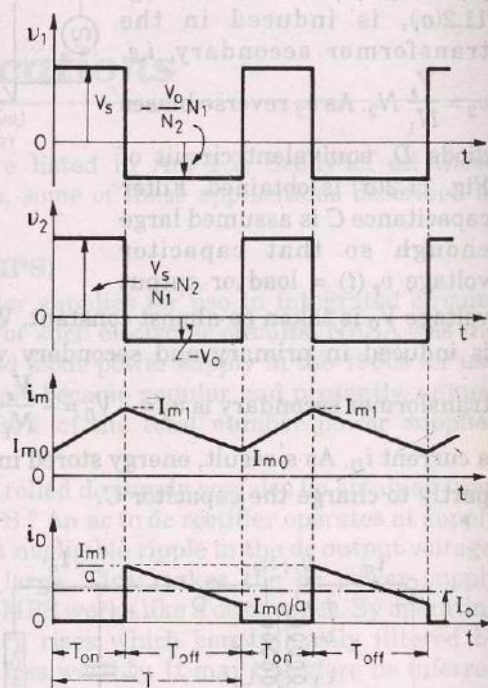


Fig. 11.3. Waveforms for flyback converter SMPS.

It is seen from Fig. 11.2 (b) that open circuit voltage across M1 is

$$V_{oc} = v_1 + V_s = \frac{V_0}{N_2} \cdot N_1 + V_s = \frac{V_0}{a} + V_s$$

From Eq. (11.5), 
$$V_{oc} = \frac{V_s \cdot k}{1-k} + V_s = \frac{V_s}{1-k} \dots(11.6)$$

Eq. (11.3) gives current on primary side of the transformer. This current, when referred to secondary side, is equal to diode current  $i_D$ .

$$\begin{aligned} \therefore i_D(t) &= i_m(t) \cdot \frac{N_1}{N_2} \\ &= \frac{N_1}{N_2} \left[ I_{m1} - \frac{V_0}{N_2} \cdot N_1 \cdot \frac{1}{L} (t - T_{on}) \right] \\ &= \frac{I_{m1}}{a} - \frac{V_0}{a^2 \cdot L} (t - T_{on}) \dots(11.7) \end{aligned}$$

Flyback converter offers simple SMPS and is useful for applications below about 500 W.

**11.1.2. Push-pull Converter**

SMPS with push-pull configuration is shown in Fig. 11.4. It uses two power MOSFETs M1 and M2 and a transformer with mid-taps on both primary and secondary sides. As in flyback converter, an uncontrolled rectifier feeds push-pull SMPS. Inductor  $L$  and capacitor  $C$  are the filter components.

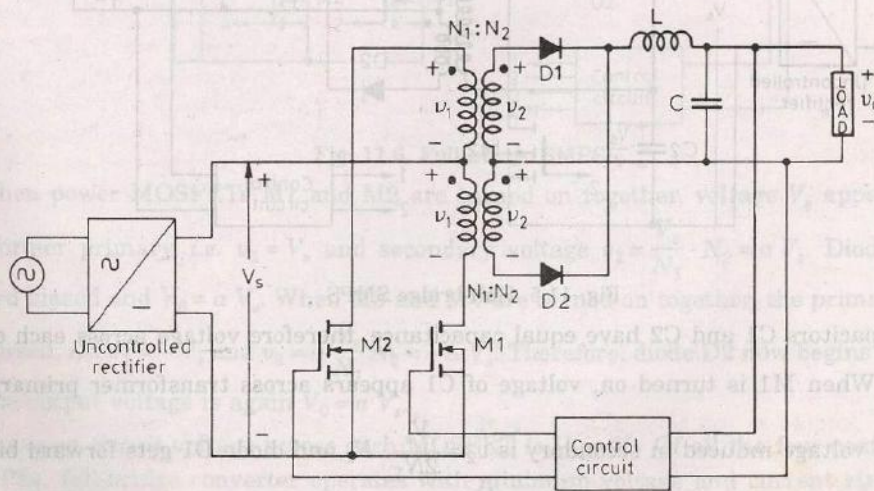


Fig. 11.4. Push-pull SMPS.

When M1 is turned on,  $V_s$  is applied to lower half of transformer primary, i.e.  $v_1 = V_s$ . As a result, voltage  $v_2 = \frac{V_s}{N_1} N_2$  is induced in both the secondary windings. Voltage  $v_2$  in the upper half secondary forward biases diode D1, therefore load voltage  $V_0$  is given by

$$V_0 = \frac{V_s}{N_1} N_2 = aV_s.$$

When M2 is turned on,  $v_1 = -V_s$  is applied to upper half of primary winding. Consequently,  $v_2 = -\frac{V_s}{N_1} N_2$  is induced in both the transformer secondaries. As  $v_2$  is negative, diode D2 gets forward biased and  $V_0 = a V_s$  as before.

This shows that voltage on primary swings from  $+V_s$  with M1 on to  $-V_s$  with M2 on. Power MOSFETs M1 and M2 operate with duty cycle of 0.5. When M1 is off, the voltage across M1 terminals is  $V_{oc} = 2V_s$ . As both M1 and M2 are subjected to open-circuit voltage of  $2V_s$ , this configuration is suitable for low-voltage applications only.

### 11.1.3. Half-bridge Converter

The circuit for half-bridge SMPS configuration is shown in Fig. 11.5. It consists of an uncontrolled rectifier, two capacitors C1 and C2, two power MOSFETs M1 and M2, one transformer with mid-tap on the secondary side, two diodes D1 and D2 and filter components L and C.

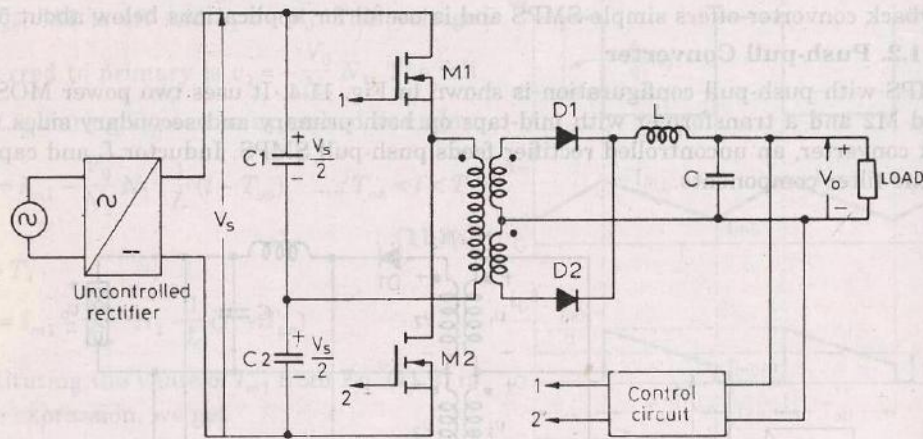


Fig. 11.5. Half-bridge SMPS.

Two capacitors C1 and C2 have equal capacitance, therefore voltage across each of the two is  $\frac{V_s}{2}$ . When M1 is turned on, voltage of C1 appears across transformer primary, *i.e.*  $v_1 = \frac{V_s}{2}$  and voltage induced in secondary is  $v_2 = \frac{V_s}{2N_1} \cdot N_2$  and diode D1 gets forward biased. When M2 is turned on, a reverse voltage of  $\frac{V_s}{2}$  appears across transformer primary from C2, *i.e.*  $v_1 = -\frac{V_s}{2}$  and voltage induced in secondary winding is  $v_2 = -\frac{V_s}{2N_1} N_2$ , therefore diode D2 gets forward biased. This means that transformer primary voltage swings from  $-\frac{V_s}{2}$  to  $+\frac{V_s}{2}$ . Average output voltage, however, is

$$V_0 = \frac{V_s}{2N_1} \cdot N_2 = 0.5 a V_s$$

When M1 is off, open circuit voltage across M1 terminals is  $V_{oc} = V_s$ . When M2 is off, as before  $V_{oc} = V_s$ . For *h.v. dc* applications, half-bridge converter is, therefore, preferred over push-pull converters. For *l.v. dc* applications, push-pull SMPS is preferred due to low MOSFET currents.

#### 11.1.4. Full-bridge Converter

The circuit arrangement for a full-bridge SMPS is shown in Fig. 11.6. It consists of an uncontrolled rectifier, four power MOSFETs, transformer with mid-tap secondary, two diodes and LC filter circuit. As in all the previous circuits, the function of control circuit is to sense the output load voltage and to decide about the duty ratio of MOSFETs.

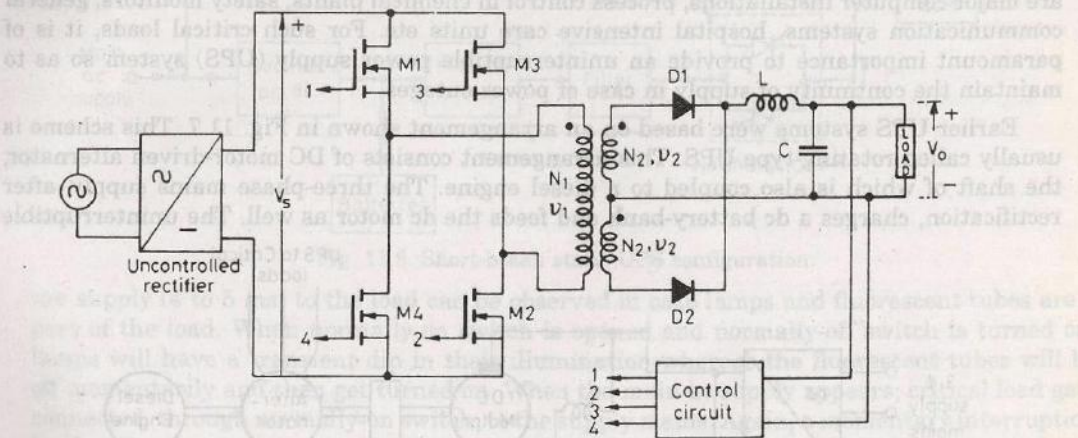


Fig. 11.6. Full bridge SMPS.

When power MOSFETs M1 and M2 are turned on together, voltage  $V_s$  appears across transformer primary, i.e.  $v_1 = V_s$  and secondary voltage  $v_2 = \frac{V_s}{N_1} \cdot N_2 = a V_s$ . Diode D1 gets forward biased and  $V_0 = a V_s$ . When M3 and M4 are turned on together, the primary voltage is reversed, i.e.  $v_1 = -V_s$  and  $v_2 = -\frac{V_s}{N_1} N_2 = -a V_s$ . Therefore, diode D2 now begins to conduct and the output voltage is again  $V_0 = a V_s$ .

The open circuit voltage across each MOSFET is  $V_{oc} = V_s$ . Of all the four configurations of SMPSs, full-bridge converter operates with minimum voltage and current stress on the power MOSFET. It is therefore very popular for high power applications above 750 W.

The overall size of SMPSs is dependent on its operating frequency. Use of power transistors is limited to approximately 40 to 50 kHz. Above this operating frequency, power MOSFETs are used up to about 200 kHz.

The main advantages of SMPSs over conventional linear power supplies are as under :

- (i) For the same power rating, SMPS is of smaller size, lighter in weight and possesses higher efficiency because of its high-frequency operation.
- (ii) SMPS is less sensitive to input voltage variations.

The disadvantages of SMPS are as under :

- (i) SMPS has higher output ripple and its regulation is worse
- (ii) SMPS is a source of both electromagnetic and radio interference due to high frequency switching.
- (iii) Control of radio frequency noise requires the use of filters on both input and output of SMPS.

The advantages possessed by SMPSs far outweigh their shortcomings. This is the reason for their wide-spread popularity and growth.

### 11.2. UNINTERRUPTIBLE POWER SUPPLIES

There are several applications where even a temporary power failure can cause a great deal of public inconvenience leading to large economic losses. Examples of such applications are major computer installations, process control in chemical plants, safety monitors, general communication systems, hospital intensive care units etc. For such critical loads, it is of paramount importance to provide an uninterruptible power supply (UPS) system so as to maintain the continuity of supply in case of power outages.

Earlier UPS systems were based on an arrangement shown in Fig. 11.7. This scheme is usually called rotating-type UPS. This arrangement consists of DC motor-driven alternator, the shaft of which is also coupled to a diesel engine. The three-phase mains supply, after rectification, charges a dc battery-bank and feeds the dc motor as well. The uninterruptible

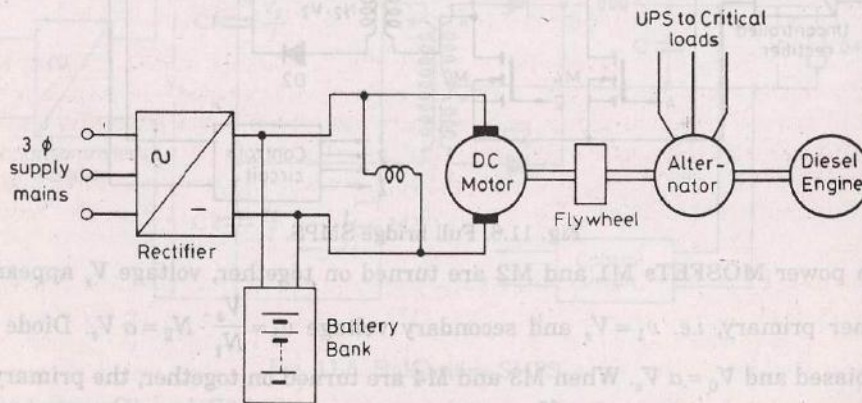


Fig. 11.7. Rotating-type UPS system based on dc motor/alternator set.

power supply needed is taken from the alternator output terminals. When mains supply fails, the diesel engine is run to take over the load. Starting of the diesel engine takes 10 to 15 seconds. During this period, the battery-bank is able to maintain the alternator speed through the dc motor and the flywheel, thus giving a no-break supply to the critical load. At present, however, static UPS systems are becoming popular up to a few kVA ratings.

Static UPS systems are of two types ; namely short-break UPS and no-break UPS. In short-break UPS, the load gets disconnected from the power source for a short duration of the order of 4 to 5 ms. In no-break UPS, load gets continuous uninterrupted supply from the power source. These are now discussed briefly.

**Short-break UPS.** In situations where short interruption (4 to 5 ms) in supply can be tolerated, the short-break UPS shown in Fig. 11.8 is used. In this system, main ac supply is rectified to dc. This dc output from the rectifier charges the batteries and is also converted

to ac by an inverter, Fig. 11.8. After passing through the filter, ac can be delivered to load in case normally-off contacts are closed. Under normal circumstances, normally-on contacts are closed and normally-off contacts are open and the main supply delivers ac power to the load. At the same time, the rectifier supplies continuous trickle charge to batteries to keep them fully charged. In the event of power outage, normally-off switch is turned-on and the batteries deliver ac power to critical load through the inverter and filter. A momentary interruption in

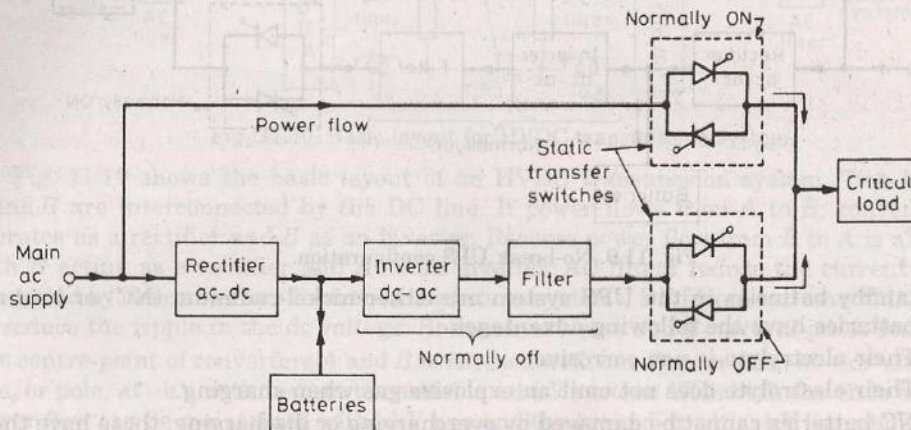


Fig. 11.8. Short-break static UPS configuration.

the supply (4 to 5 ms) to the load can be observed in case lamps and fluorescent tubes are a part of the load. When normally-on switch is opened and normally-off switch is turned on, lamps will have a transient dip in their illumination whereas the fluorescent tubes will be off momentarily and then get turned on. When the main ac supply appears, critical load gets connected, through normally-on switch, to the supply mains. Again, a momentary interruption in the illumination is noticed. The arrangement shown in Fig. 11.8 is also referred to as *stand-by power supply*.

**No-break UPS.** When a no-break supply is required, the static UPS system shown in Fig. 11.9 is used. In this system, main ac supply is rectified and the rectifier delivers power to maintain required charge on the batteries. Rectifier also supplies power to inverter continuously which is then given to ac-type load through filter and normally-on switch. In case of main-supply failure, batteries at once take over with no-break of supply to the critical load. No dip or discontinuity in the illumination is observed in case of no-break UPS. This configuration of Fig. 11.9 has the following additional advantages :

- (i) The inverter can be used to condition the supply delivered to load.
- (ii) Load gets protected from transients in the main ac supply.
- (iii) Inverter output frequency can be maintained at the desired value.

In case inverter failure is detected, the load is switched on to the main ac supply directly by turning on the normally-off static switch and opening the normally-on static switch. The transfer of load from inverter to main ac supply takes 4 to 5 ms by static transfer switch as compared to 40 to 50 ms for a mechanical contactor. After inverter fault is cleared, uninterruptible power supply is again restored to the load through the normally on switch. The batteries are now recharged from the main supply by adjusting the charger at maximum charge rate so that batteries are charged to their full capacity in the shortest possible time.



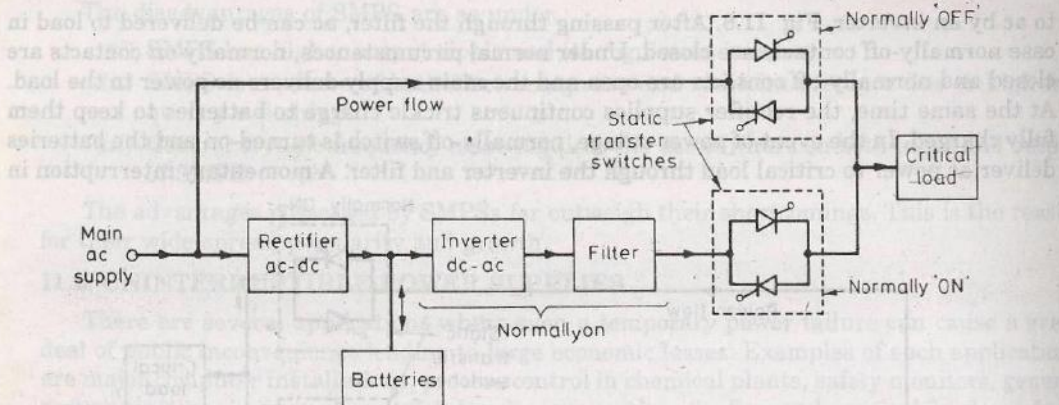


Fig. 11.9. No-break UPS configuration.

The standby batteries in the UPS system are either nickel-cadmium (NC) or lead-acid type. NC batteries have the following advantages :

- (a) Their electrolyte is non-corrosive.
- (b) Their electrolyte does not emit an explosive gas when charging.
- (c) NC batteries cannot be damaged by overcharging or discharging, these have therefore longer life.

Cost of NC batteries is, however, two or three times that of lead-acid batteries.

The time period for which a battery or a battery-bank can deliver power to load through inverter at the required voltage level depends upon (i) the size of the batteries and (ii) nature of the load.

## 11.5. STATIC CIRCUIT BREAKERS

Static circuit breakers are semiconductor-based circuits capable of providing a fast and reliable interruption to a continuous current. Static circuit breakers are of two types; static ac circuit breakers and static dc circuit breakers. High-current circuit breakers employing thyristors are now discussed briefly.

### 11.5.1. Static AC Circuit Breakers

Static ac switch can be made to operate as a static ac circuit breaker. In Fig. 11.19 (a) is shown a simplified circuit configuration for static ac circuit breaker and Fig. 11.19 (b) gives relevant voltage and current waveforms. As in static switches, thyristors 1 and 2 in Fig. 11.19(a) are turned on at the instant load current is passing through zero. For breaking the circuit, the triggering pulse is withdrawn. For example, at  $\omega t = 4\pi + \phi$ , if triggering pulse  $i_{g1}$  is not applied to T1, it will not get turned on. T2 is already off just before  $\omega t = 4\pi + \phi$ . Therefore, the continuity of the circuit is broken. So when turn-off command is received by the control circuit due to some system fault, the gating pulse is withdrawn from T1 or T2 and eventually

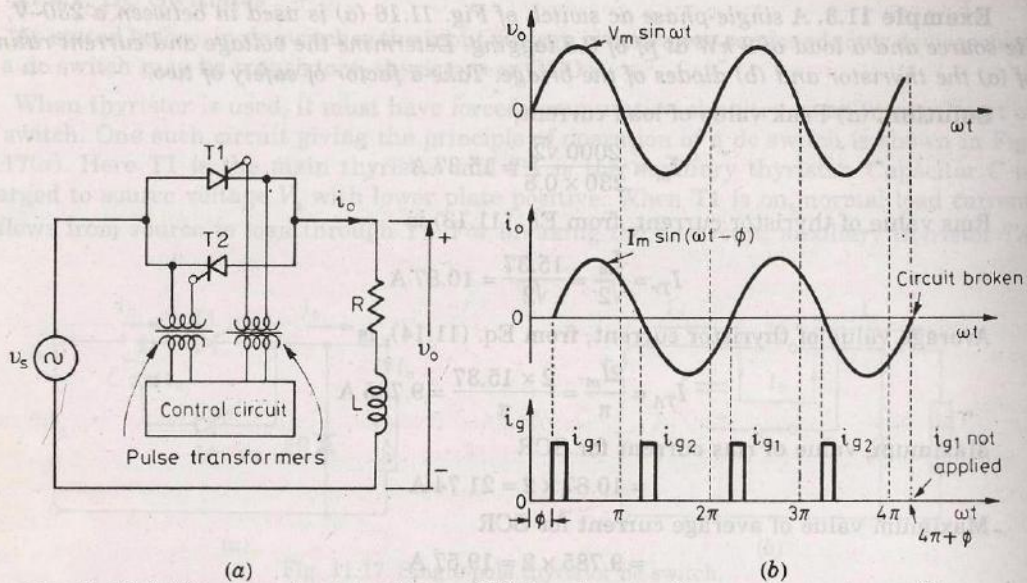


Fig. 11.19. (a) Static ac circuit breaker and (b) its relevant voltage and current waveforms.

the circuit is broken. In case turn-off command is received just after  $3\pi + \phi$ , load current will be broken only at  $4\pi + \phi$ , i.e. a delay of  $\pi$  radians or half-cycle is a must. If turn-off command is received at the instant  $(3\pi + \phi) < \omega t < (4\pi + \phi)$ , even then the circuit is broken at the instant  $\omega t = 4\pi + \phi$  only. This shows that maximum time delay for breaking the circuit is one half-cycle i.e.  $\frac{\pi}{\omega}$  seconds after turn-off command is accepted by the control circuit due to some exigencies in the system.

**11.5.2. Static DC Circuit Breakers**

A simple arrangement of static dc circuit breaker is shown in Fig. 11.20. This circuit is similar to that shown in Fig. 5.4(a), pertaining to class-C commutation. As stated before, when input voltage to a circuit consisting of thyristors is dc, forced commutation is essential for turning off a thyristor. For complete analysis, refer to section 5.3. Here only brief discussion is given.

When main thyristor T1 is turned on, load voltage becomes equal to source voltage  $V_s$  and capacitor C begins to charge through the circuit  $V_s, R_2, C$  and T1. Eventually capacitor C gets charged with right hand plate positive. For breaking the circuit, auxiliary thyristor T2 is turned on. Capacitor voltage  $v_c$  at once applies a reverse voltage  $V_s$  across SCR T1 and turns it off. After T1 is force commutated, capacitor will charge from  $+V_s$  to  $-V_s$  through the circuit  $V_s, \text{load}, C$  and T2. When C is fully charged to  $-V_s$  (left hand plate positive), current through load will be zero and at the same time current through  $R_2$  will be less than the holding current of SCR T2. As a result, T2 will get turned off naturally. From this, the value of  $R_2$  can be determined.

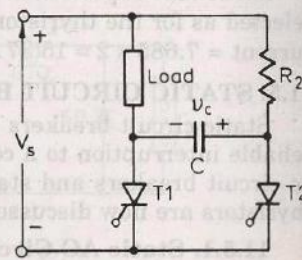


Fig. 11.20. Static dc circuit breaker.

## 11.6. SOLID STATE RELAYS

AC and dc static switches can be used as solid state relays (SSRs) in ac and dc circuits respectively. In ac circuits, thyristors or triacs are used whereas in dc circuits transistors are preferred. Solid state relays have no contacts or moving parts. These are now being used extensively and are replacing the conventional contact-type electromagnetic relays in applications like control of motor drives, resistance heating etc. SSRs need electrical isolation between control circuit and the load circuit by means of optocouplers or pulse transformers.

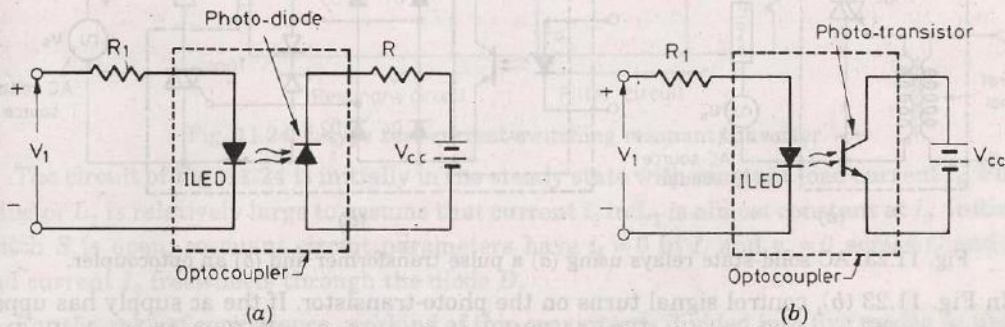


Fig. 11.21. Optocouplers using (a) a photo-diode and (b) a photo-transistor.

An optocoupler consists of infra-red light emitting diode (ILED) and a photo-diode or a photo-transistor. An optocoupler having ILED and photo-diode is shown in Fig. 11.21 (a). A short pulse  $V_1$  applied to ILED will cause it to emit light on to photo-diode which will then begin to conduct in the reverse direction as shown. An optocoupler using photo-transistor is shown in Fig. 11.21 (b). As before, a short pulse  $V_1$  applied to ILED will throw light on the base of photo-transistor and turn it on. As photo-transistor is more sensitive than a photo-diode, optocouplers based on opto-transistors are more common.

### 11.6.1. DC Solid State Relays

A dc solid state relay using opto-coupler for isolation purposes is shown in Fig. 11.22. When control pulse  $V_C$  is applied to ILED, it emits light and turns on the photo-transistor. The current output from the photo-transistor acts as the base current for transistor  $TR$ . Consequently  $TR$  is turned on and source voltage  $V_s$  is applied to load.

When control pulse  $V_C$  is absent,  $TR$  gets turned off and load voltage is zero.

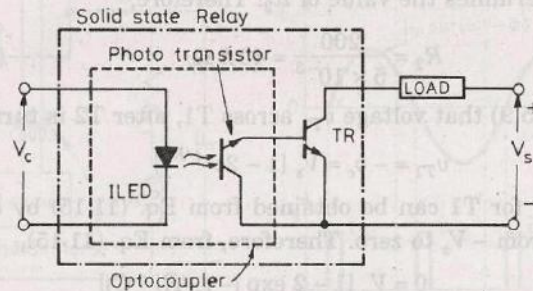


Fig. 11.22. DC solid-state relay using an optocoupler.

### 11.6.2. AC Solid State Relays

Fig. 11.23 shows two basic circuits for ac solid-state relays. Fig. 11.23 (a) uses a pulse transformer for isolation purposes and in Fig. 11.23 (b), isolation is provided by an optocoupler. When control signal appears across the primary of pulse transformer, its secondary applies a triggering pulse to turn on the triac. As a result, circuit is completed through  $v_s$ , load and triac and therefore, source voltage is applied to the load.

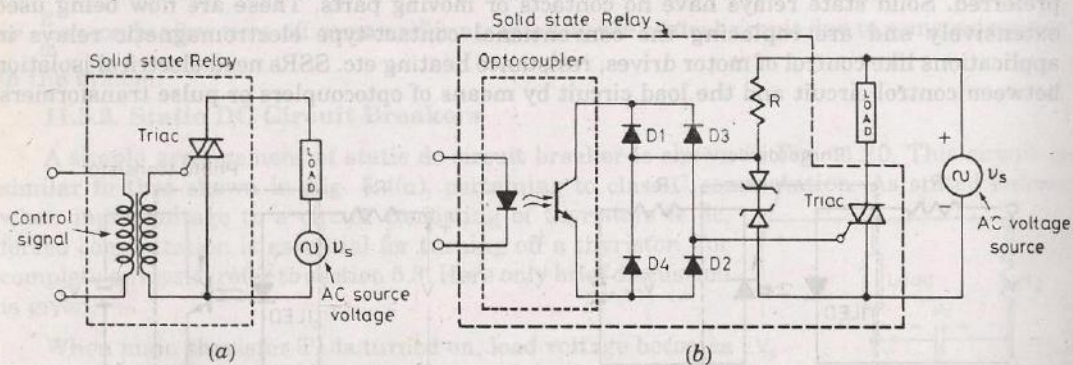


Fig. 11.23. AC solid-state relays using (a) a pulse transformer and (b) an optocoupler.

In Fig. 11.23 (b), control signal turns on the photo-transistor. If the ac supply has upper terminal positive as shown in Fig. 11.23(b), the current will flow through  $R$ ,  $D1$ , photo-transistor,  $D2$ , triac gate and source. This current will turn on the triac and load gets energised by source voltage  $v_s$ . The function of  $R$  is to limit the flow of gate current of triac. If lower terminal of ac supply is positive, the current will flow through triac gate,  $D3$ , photo-transistor,  $D4$ ,  $R$  and source  $v_s$ . Triac gets turned on and source voltage is applied to load.

## 11.7. RESONANT CONVERTERS

In SMPSs discussed in Art. 11.1 and in the PWM inverters described in Chapter 8, the switching devices are made to turn-on and turn-off the entire load current at high  $di/dt$ . The

devices handling high  $di/dt$  also experience high-voltage stresses across them; due to these two effects, there are increased power losses in the switching devices. In case size and weight of the converter components is to be reduced, switching frequencies are increased. At these high frequencies, switching losses and high-voltage stresses are further aggravated. Another major drawback of high  $di/dt$  and high  $dv/dt$  caused by rapid on and off of the switching devices is the electromagnetic interference.

The shortcomings enunciated above can be minimised if each switch in a converter is turned on and off when the voltage across it and/or current through it is zero at the instant of switching. The converter circuits which employ zero-voltage and/or zero-current switching are called *resonant converters*. In most of these converters, some form of  $L$ - $C$  resonance is used, that is why these are known as resonant converters.

In this section, resonant converters employing zero-current switching (ZCS) and zero-voltage switching (ZVS) are described.

### 11.7.1. Zero-Current Switching Resonant Converters

There are two types of ZCS resonant converters,  $L$ -type and  $M$ -type. Both of these circuit topologies use  $L$  and  $C$  as a series resonant circuit; in addition  $L$  also limits  $di/dt$  of the switching current. Here first  $L$ -type and then  $M$ -type ZCS resonant converters are presented.

**11.7.1.1.  $L$ -type ZCS Resonant Converters.** An  $L$ -type ZCS resonant converter is shown in Fig. 11.24. The switching device  $S$  in the figure can be a GTO, thyristor, BJT, power MOSFET or IGBT. At low kilohertz range; GTO, thyristor, transistor or IGBT is used whereas for megahertz range, power MOSFETs are preferred. Inductor  $L$  and capacitor  $C$  near the dc source  $V_s$  form a resonant circuit whereas  $L_1, C_1$  near the load constitute a filter circuit. Direction of currents and polarities of voltages as marked in Fig. 11.24 are treated as positive.

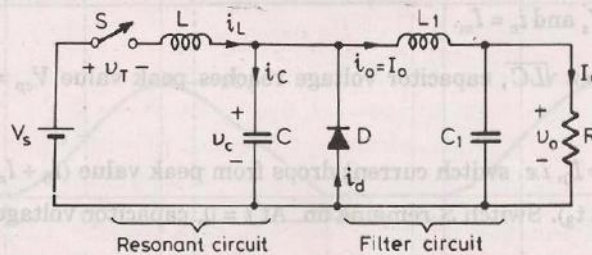


Fig. 11.24.  $L$ -type zero-current-switching resonant converter.

The circuit of Fig. 11.24 is initially in the steady state with constant load current  $I_0$ . Filter inductor  $L_1$  is relatively large to assume that current  $i_o$  in  $L_1$  is almost constant at  $I_0$ . Initially, switch  $S$  is open; resonant circuit parameters have  $i_L = 0$  in  $L$  and  $v_c = 0$  across  $C$  and the load current  $I_0$  freewheels through the diode  $D$ .

For the sake of convenience, working of this converter is divided into five modes as under. For all these modes, time  $t$  is taken as zero at the beginning of each mode.

**Mode I. ( $0 \leq t \leq t_1$ ).** At  $t = 0$ , switch  $S$  is turned on. As  $I_0$  is freewheeling through diode  $D$ , voltage across ideal diode  $v_D = 0$  and also  $v_c = 0$ , Fig. 11.25(a). It implies that source voltage  $V_s$  gets applied across  $L$  and the switch current  $i_L$  begins to flow through  $V_s$ , switch  $S$ ,  $L$  and diode  $D$ , Fig. 11.25(a). Therefore,  $V_s = L di/dt$ . It gives  $i_L = \frac{V_s}{L} t$ . It shows that inductor or switch current  $i_L$  rises linearly from its zero initial value. The diode current  $i_D$  is given by

$$i_D = I_0 - i_L = I_0 - \frac{V_s}{L} t \quad \dots(11.15)$$

At  $t = t_1$ ,

$$i_L = \frac{V_s}{L} \cdot t_1 = I_0. \text{ This gives}$$

$$t_1 = \frac{I_0 \cdot L}{V_s}$$

Also, at  $t = t_1$ ,  $i_D = I_0 - I_0 = 0$ . Soon after  $t_1$ , as  $i_D$  tends to reverse, diode  $D$  gets turned off. As a result of this, short circuit across  $C$  is removed.

**Mode II ( $0 \leq t \leq t_2$ ).** Switch  $S$  remains on. As  $D$  turns off at  $t = 0$ , current  $I_0$  flows through  $V_s, L, L_1$  and  $R$ . In Figs. 11.25(a) and (b), constant current through  $L_1$  and  $R$  is represented by current source  $I_0$ . Also, a current  $i_C$  begins to build up through resonant circuit consisting of  $V_s, L$  and  $C$  in series. The inductor current  $i_L$  is, therefore, given by

$$i_L = I_0 + i_C = I_0 + I_m \sin \omega_0 t \quad \dots(11.16)$$

where  $I_m = V_s \sqrt{\frac{C}{L}} = \frac{V_s}{Z_0}$  and  $\omega_0 = \frac{1}{\sqrt{LC}}$ . Here  $Z_0 = \sqrt{\frac{L}{C}}$  is the characteristic impedance of the resonant circuit.

The capacitor current is  $i_c = I_m \sin \omega_0 t$  and capacitor voltage  $v_c$  is given by

$$v_c(t) = V_s (1 - \cos \omega_0 t) \quad \dots(11.17)$$

The peak value of current  $i_L$  is  $I_p = I_0 + I_m$  and it occurs at  $t = \frac{\pi}{2\omega_0} = \frac{\pi}{2} \sqrt{LC}$ . At this instant,  $v_c = V_s [1 - \cos \pi] = 2V_s$  and  $i_c = I_m$ .

When  $t = t_2 = \frac{\pi}{\omega_0} = \pi \sqrt{LC}$ , capacitor voltage reaches peak value  $V_{cp} = V_s [1 - \cos \pi] = 2V_s$  and  $i_c = 0$ .

Also, at  $t = t_2$ ,  $i_L = I_0$ , i.e. switch current drops from peak value  $(I_0 + I_m)$  to  $I_0$ .

**Mode III ( $0 \leq t \leq t_3$ ).** Switch  $S$  remains on. At  $t = 0$ , capacitor voltage is  $2V_s$ . As  $i_c$  tends to reverse at  $t = 0$ , capacitor begins to discharge and force a current  $i_c = V_s \sqrt{\frac{C}{L}} \sin \omega_0 t$  opposite to  $i_L$ , Fig. 11.25(c), so that inductor or device current  $i_L$  is given by

$$i_L = I_0 - i_c = I_0 - I_m \sin \omega_0 t \quad \dots(11.18)$$

and capacitor voltage  $v_c = 2V_s \cos \omega_0 t$ . Current  $i_L$  falls to zero when  $t = t_3$ ,

$$i_L = 0 = I_0 - I_m \sin \omega_0 t_3$$

or  $t_3 = \sqrt{LC} \sin^{-1} (I_0/I_m)$

$$\text{At } t = t_3, \quad v_c = 2V_s \cos \omega_0 t_3 = 2V_s \left[ \frac{\sqrt{I_m^2 - I_0^2}}{I_m} \right] = V_{c3}$$

During this mode,  $i_c = I_m \sin \omega_0 t$  and as  $i_L$  falls to zero at  $t_3$ , switching device  $S$  gets turned off. Note that current  $i_c$  in this mode flows opposite to its positive direction, it is therefore shown negative in Fig. 11.25(c) and in Fig. 11.26. At  $t = t_3$ , the value of  $i_c = -I_0$ .

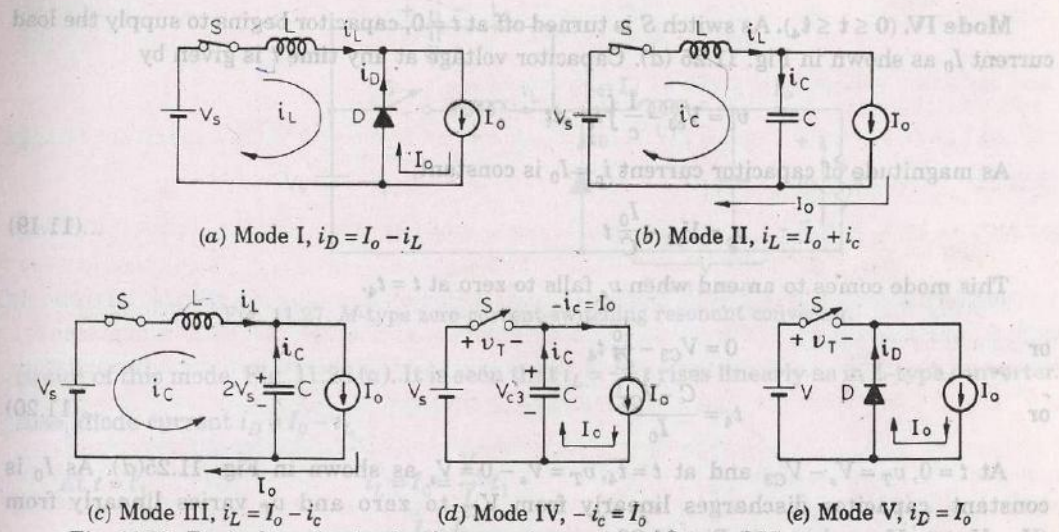


Fig. 11.25. Equivalent circuits for the operating modes of *L*-type ZCS resonant converter.

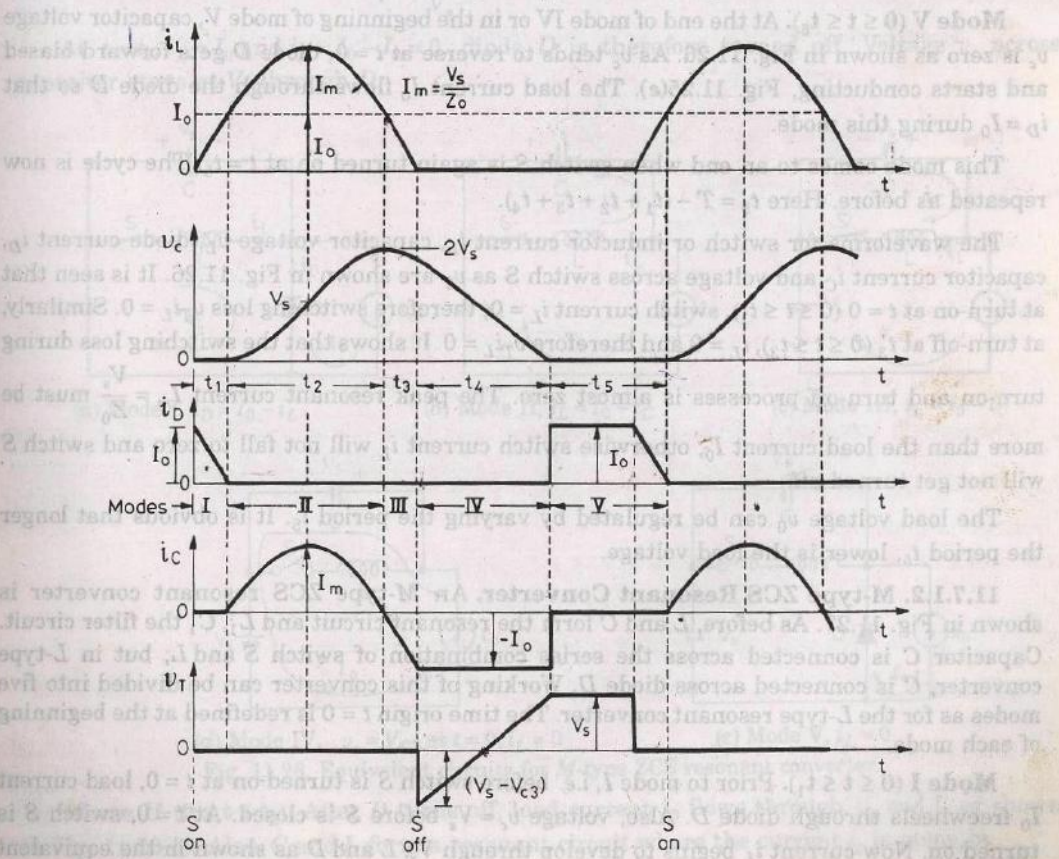


Fig. 11.26. Waveforms for *L*-type ZCS resonant converter.

**Mode IV.** ( $0 \leq t \leq t_4$ ). As switch  $S$  is turned off at  $t = 0$ , capacitor begins to supply the load current  $I_0$  as shown in Fig. 11.25 (d). Capacitor voltage at any time  $t$  is given by

$$v_c = V_{C3} - \frac{1}{C} \int i_c \cdot dt$$

As magnitude of capacitor current  $i_c = I_0$  is constant,

$$v_c = V_{C3} - \frac{I_0}{C} t \quad \dots(11.19)$$

This mode comes to an end when  $v_c$  falls to zero at  $t = t_4$ .

$$\begin{aligned} \text{or} \quad 0 &= V_{C3} - \frac{I_0}{C} t_4 \\ \text{or} \quad t_4 &= \frac{C \cdot V_{C3}}{I_0} \quad \dots(11.20) \end{aligned}$$

At  $t = 0$ ,  $v_T = V_s - V_{C3}$  and at  $t = t_4$ ,  $v_T = V_s - 0 = V_s$  as shown in Fig. 11.25(d). As  $I_0$  is constant, capacitor discharges linearly from  $V_{C3}$  to zero and  $v_T$  varies linearly from  $(V_s - V_{C3})$  to  $V_s$  as shown in Fig. 11.26.

**Mode V** ( $0 \leq t \leq t_5$ ). At the end of mode IV or in the beginning of mode V, capacitor voltage  $v_c$  is zero as shown in Fig. 11.26. As  $v_c$  tends to reverse at  $t = 0$ , diode  $D$  gets forward biased and starts conducting, Fig. 11.25(e). The load current  $I_0$  flows through the diode  $D$  so that  $i_D = I_0$  during this mode.

This mode comes to an end when switch  $S$  is again turned on at  $t = t_5$ . The cycle is now repeated as before. Here  $t_5 = T - (t_1 + t_2 + t_3 + t_4)$ .

The waveforms for switch or inductor current  $i_L$ , capacitor voltage  $v_L$ , diode current  $i_D$ , capacitor current  $i_C$  and voltage across switch  $S$  as  $v_T$  are shown in Fig. 11.26. It is seen that at turn-on at  $t = 0$  ( $0 \leq t \leq t_1$ ), switch current  $i_L = 0$ , therefore switching loss  $v_T i_L = 0$ . Similarly, at turn-off at  $t_3$  ( $0 \leq t \leq t_3$ ),  $i_L = 0$  and therefore  $v_T i_L = 0$ . It shows that the switching loss during turn-on and turn-off processes is almost zero. The peak resonant current  $I_m = \frac{V_s}{Z_0}$  must be more than the load current  $I_0$ , otherwise switch current  $i_L$  will not fall to zero and switch  $S$  will not get turned off.

The load voltage  $v_0$  can be regulated by varying the period  $t_5$ . It is obvious that longer the period  $t_5$ , lower is the load voltage.

**11.7.1.2. M-type ZCS Resonant Converter.** An  $M$ -type ZCS resonant converter is shown in Fig. 11.27. As before,  $L$  and  $C$  form the resonant circuit and  $L_1, C_1$  the filter circuit. Capacitor  $C$  is connected across the series combination of switch  $S$  and  $L$ ; but in  $L$ -type converter,  $C$  is connected across diode  $D$ . Working of this converter can be divided into five modes as for the  $L$ -type resonant converter. The time origin  $t = 0$  is redefined at the beginning of each mode.

**Mode I** ( $0 \leq t \leq t_1$ ). Prior to mode I, i.e. before switch  $S$  is turned on at  $t = 0$ , load current  $I_0$  freewheels through diode  $D$ . Also, voltage  $v_c = V_s$  before  $S$  is closed. At  $t = 0$ , switch  $S$  is turned on. Now current  $i_L$  begins to develop through  $V_s, L$  and  $D$  as shown in the equivalent



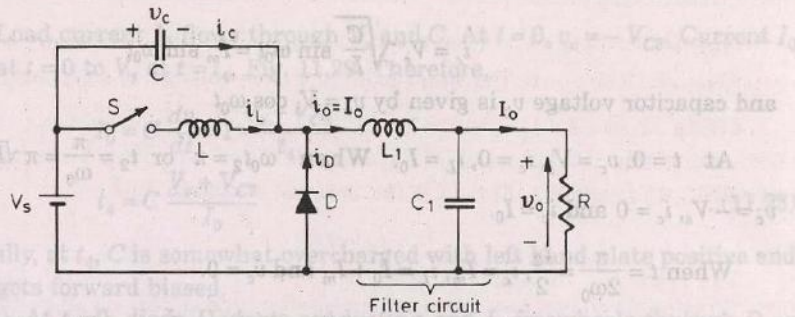


Fig. 11.27. *M*-type zero-current-switching resonant converter.

circuit of this mode, Fig. 11.28 (a). It is seen that  $i_L = \frac{V_s}{L} t$  rises linearly as in *L*-type converter.

Also, diode current  $i_D = I_0 - i_L$

At  $t = t_1$ , 
$$i_L = I_0 = \frac{V_s}{L} t_1$$

or 
$$t_1 = \frac{I_0 \cdot L}{V_s} \quad \dots(11.21)$$

At  $t = t_1$ ,  $i_L = I_0$  and  $i_D = I_0 - I_0 = 0$ , diode *D* is therefore turned off. Voltage  $v_c$  across capacitor stays at  $V_s$  through *D*.

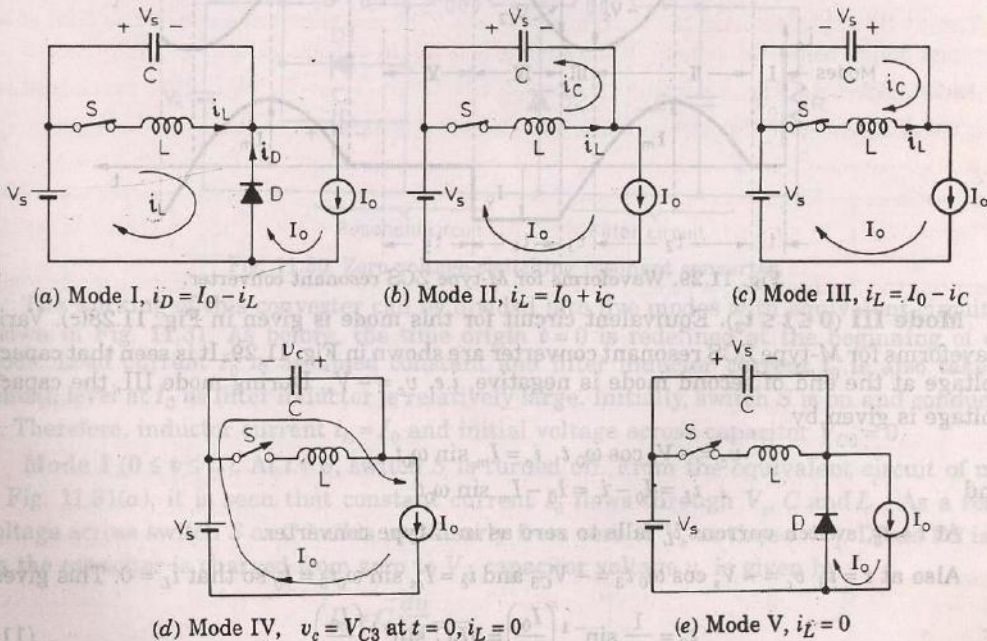


Fig. 11.28. Equivalent circuits for *M*-type ZCS resonant converter.

**Mode II** ( $0 \leq t \leq t_2$ ). After *D* turns off, load current  $I_0$  flows through  $V_s$  and *L* as shown in Fig. 11.28(b). Also, *C* and *L* form a resonant circuit where the current  $i_c$  is given by

$$i_c = V_s \sqrt{\frac{C}{L}} \sin \omega_0 t = I_m \sin \omega_0 t$$

and capacitor voltage  $v_c$  is given by  $v_c = V_s \cos \omega_0 t$

At  $t = 0$ ,  $v_c = V_s$ ,  $i_c = 0$ ,  $i_L = I_0$ . When  $\omega_0 t_2 = \pi$  or  $t_2 = \frac{\pi}{\omega_0} = \pi \sqrt{LC}$ , capacitor voltage  $v_c = -V_s$ ,  $i_c = 0$  and  $i_L = I_0$ .

When  $t = \frac{\pi}{2\omega_0} = \frac{t_2}{2}$ ,  $i_c = I_m$ ,  $i_L = I_0 + I_m$  and  $v_c = 0$ .

During this mode,  $i_L = I_0 + I_c = I_0 + I_m \sin \omega_0 t$  and capacitor gets charged from  $V_s$  to  $-V_s$  as shown in Fig. 11.29.

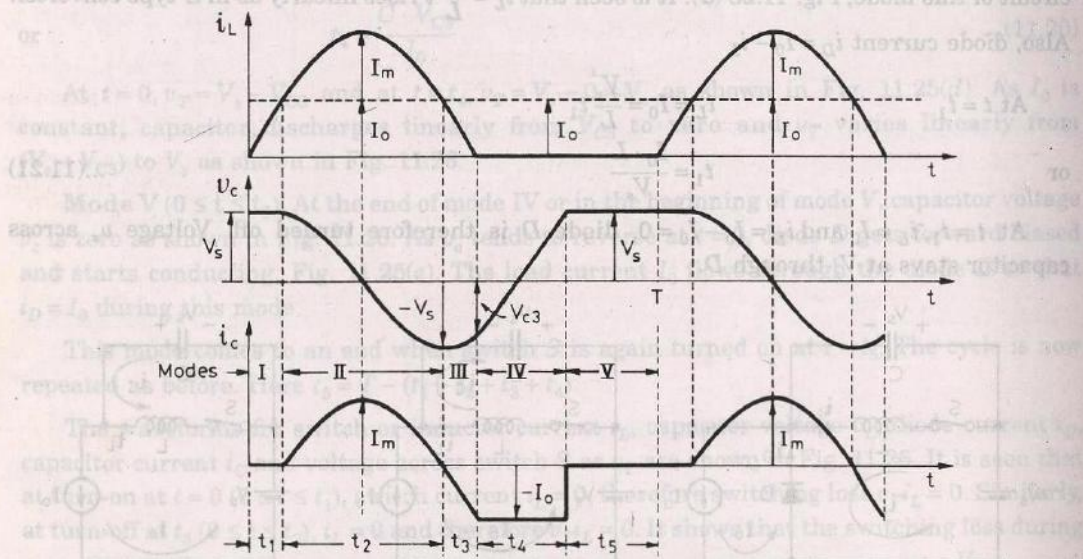


Fig. 11.29. Waveforms for  $M$ -type ZCS resonant converter.

**Mode III ( $0 \leq t \leq t_3$ ).** Equivalent circuit for this mode is given in Fig. 11.28(c). Various waveforms for  $M$ -type ZCS resonant converter are shown in Fig. 11.29. It is seen that capacitor voltage at the end of second mode is negative, i.e.  $v_c = -V_s$ . During mode III, the capacitor voltage is given by

$$v_c = -V_s \cos \omega_0 t, \quad i_c = I_m \sin \omega_0 t$$

and

$$i_L = I_0 - i_c = I_0 - I_m \sin \omega_0 t$$

At  $t = t_3$ , switch current  $i_L$  falls to zero as in  $L$ -type converter.

Also at  $t = t_3$ ,  $v_c = -V_s \cos \omega_0 t_3 = -V_{C3}$  and  $i_c = I_m \sin \omega_0 t_3 = I_0$  so that  $i_L = 0$ . This gives

$$t_3 = \frac{1}{\omega_0} \sin^{-1} \left( \frac{I_0}{I_m} \right) = \sqrt{LC} \sin^{-1} \left( \frac{I_0}{I_m} \right) \quad \dots(11.22)$$

**Mode IV ( $0 \leq t \leq t_4$ ).** In the previous mode, as  $i_L$  falls to zero and tends to reverse, switch  $S$  is naturally turned off. In this mode, therefore,  $S$  remains off and the equivalent circuit of

Fig. 11.28(d) applies. Load current  $I_0$  flows through  $V_s$  and  $C$ . At  $t=0$ ,  $v_c = -V_{C3}$ . Current  $I_0$  charges  $C$  from  $-V_{C3}$  at  $t=0$  to  $V_s$  at  $t=t_4$ , Fig. 11.29. Therefore,

$$I_0 = C \frac{dv}{dt} = I \frac{V_s + V_{C3}}{t_4}$$

$$\text{or } t_4 = C \frac{V_s + V_{C3}}{I_0} \dots(11.23)$$

At  $t_4$ ,  $v_c = V_s$ . Actually, at  $t_4$ ,  $C$  is somewhat overcharged with left hand plate positive and consequently diode  $D$  gets forward biased.

**Mode V ( $0 \leq t \leq t_5$ ).** At  $t=0$ , diode  $D$  starts conducting and  $I_0$  freewheels through  $D$  as shown in Fig. 11.28 (e). Switch  $S$  is open and voltage  $v_c$  stays at  $V_s$  through  $D$ . Switch current  $i_L$  remains zero as  $S$  is open. At time  $t=T$ , switch  $S$  is again turned on and the cycle repeats.

**11.7.2. Zero-Voltage-Switching Resonant Converters**

A zero-voltage-switching (ZVS) resonant converter is shown in Fig. 11.30. It consists of diode  $D1$  and capacitor  $C$  connected across the switch  $S$ . As in ZCS converter, ZVS resonant converter has  $L, C$  as the resonant circuit components and  $L_1, C_1$  as the filter circuit components. The function of the resonant capacitor  $C$  is to produce zero voltage across the switch  $S$ . Diode  $D2$  provides a free wheeling path to load current  $I_0$ . As the name suggests, the switch  $S$  in ZVS resonant converter is turned on and off at zero-voltage across the switch.

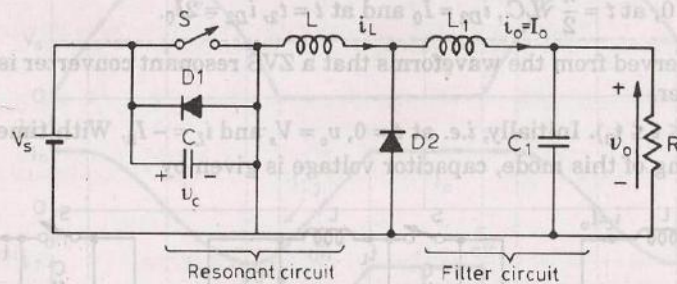


Fig. 11.30. Zero-voltage-switching resonant converter.

The working of this converter can be divided into five modes with equivalent circuits as shown in Fig. 11.31. As before, the time origin  $t=0$  is redefined at the beginning of each mode. Load current  $I_0$  is assumed constant and filter inductor current  $i_0$  is also taken to remain level at  $I_0$  as filter inductor is relatively large. Initially, switch  $S$  is on and conducting  $I_0$ . Therefore, inductor current  $i_L = I_0$  and initial voltage across capacitor  $V_{C0} = 0$ .

**Mode I ( $0 \leq t \leq t_1$ ).** At  $t=0$ , switch  $S$  is turned off. From the equivalent circuit of mode I, Fig. 11.31(a), it is seen that constant current  $I_0$  flows through  $V_s, C$  and  $L$ . As a result, voltage across switch  $S$  or  $C$  builds up linearly from zero to  $V_s$  at time  $t=t_1$ . Diode  $D2$  is off. As the capacitor is charged from zero to  $V_s$ , capacitor voltage  $v_c$  is given by

$$I_0 = C \frac{dv}{dt}$$

$$\text{or } v_c = \frac{I_0}{C} t$$

$$\text{At time } t=t_1, v_c = \frac{I_0}{C} t_1 = V_s \text{ or } t_1 = \frac{CV_s}{I_0} \dots(11.24)$$

Note that voltage across diode D2 is  $v_{D2} = V_s$  at  $t = 0$  and  $v_{D2} = 0$  at  $t = t_1$ .

Also, at  $t = 0$ ,  $v_c = 0$ ; therefore switch  $S$  is turned off at zero voltage as required.

**Mode II** ( $0 \leq t \leq t_2$ ). At  $t = 0$ , actually capacitor is somewhat overcharged, i.e.  $v_c > V_s$ ; therefore diode D2 becomes forward biased. Now a resonant current  $i_L$  is set up in series circuit  $V_s, C, L$  and D2, Fig. 11.31(b), where  $i_L$  is given by

$$i_L = I_0 \cos \omega_0 t$$

The capacitor voltage  $v_c$  is given by

$$v_c = V_s + V_m \sin \omega_0 t \tag{11.25}$$

where  $V_m = I_0 \sqrt{\frac{L}{C}} = I_0 Z_0$  and  $Z_0 = \sqrt{\frac{L}{C}}$  is the characteristic impedance of the circuit in

ohms. The peak switch or capacitor voltage  $V_{pk}$  occurs when  $\omega_0 t = \pi/2$  or  $t = \frac{\pi}{2} \sqrt{LC}$  and its value is

$$V_{pk} = V_s + V_m = V_s + I_0 Z_0$$

At  $t = t_2$ ,  $i_L = -I_0$  where  $\omega_0 t_2 = \pi$  or  $t_2 = \pi \sqrt{LC}$  and capacitor voltage is  $v_c = V_s$ .

Diode D2 current is given by  $i_{D2} = I_0 - I_0 \cos \omega_0 t$ .

At  $t = 0$ ,  $i_{D2} = 0$ , at  $t = \frac{\pi}{2} \sqrt{LC}$ ,  $i_{D2} = I_0$  and at  $t = t_2$ ,  $i_{D2} = 2I_0$ .

It may be observed from the waveforms that a ZVS resonant converter is the dual of ZCS resonant converter.

**Mode III** ( $0 \leq t \leq t_3$ ). Initially, i.e. at  $t = 0$ ,  $v_c = V_s$  and  $i_L = -I_0$ . With time  $t$  reckoned zero from the beginning of this mode, capacitor voltage is given by

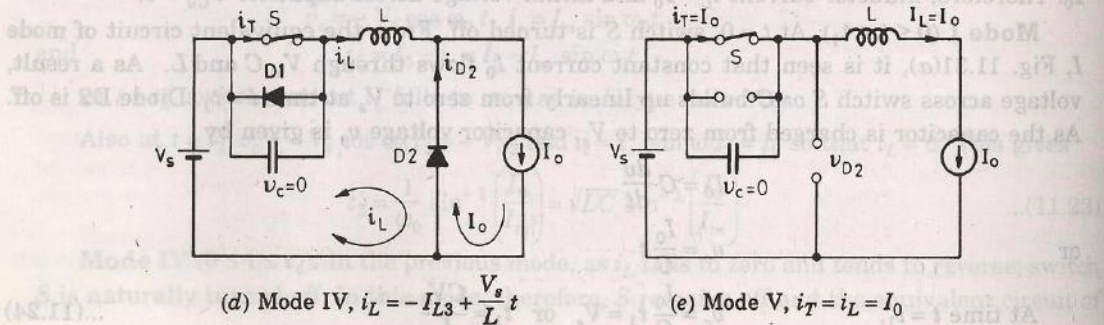
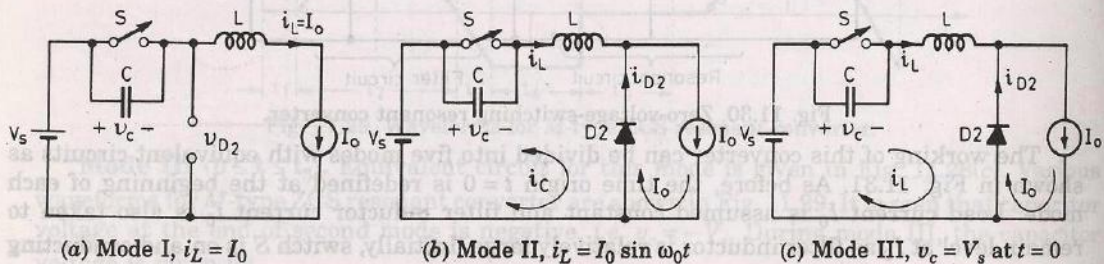


Fig. 11.31. Equivalent circuit for ZVS resonant converter.

and  
so that

$$v_c = V_s - V_m \sin \omega_0 t$$

$$i_L = -I_0 \cos \omega_0 t$$

$$i_{D2} = I_0 - I_0 \cos \omega_0 t$$

At time  $t = t_3$ ,  $v_c = 0$ ,  $i_L = I_{L3}$  and  $i_{D2} = I_0 - I_{L3}$ . This gives

$$0 = V_s - V_m \sin \omega_0 t_3$$

or

$$t_3 = \sqrt{LC} \sin^{-1} \left( \frac{V_s}{I_0} \right) \sqrt{\frac{C}{L}} \quad \dots(11.26)$$

At the end of this mode, i.e. at  $t = t_3$ ,  $v_c = 0$ ; as a result reverse bias across D1 vanishes and  $i_L$  begins to flow through D1.

**Mode IV ( $0 \leq t \leq t_4$ ).** During this mode, capacitor voltage is clamped to zero by diode D1 conducting negative current  $i_L$ . As soon as antiparallel diode D1 begins to conduct at  $t = 0$ , gate drive is applied to switch  $S$ . The inductor current  $i_L$  rises linearly from  $-I_{L3}$  to zero. At this instant, reverse bias of D1 vanishes and already gated switch  $S$  turns on. This shows that switch  $S$  turns on at zero voltage and zero current. After this, current rises linearly to  $I_0$  in the circuit formed by  $V_s$ ,  $S$ ,  $L$  and D2. The linear variation of current from  $I_{L3}$  is given by

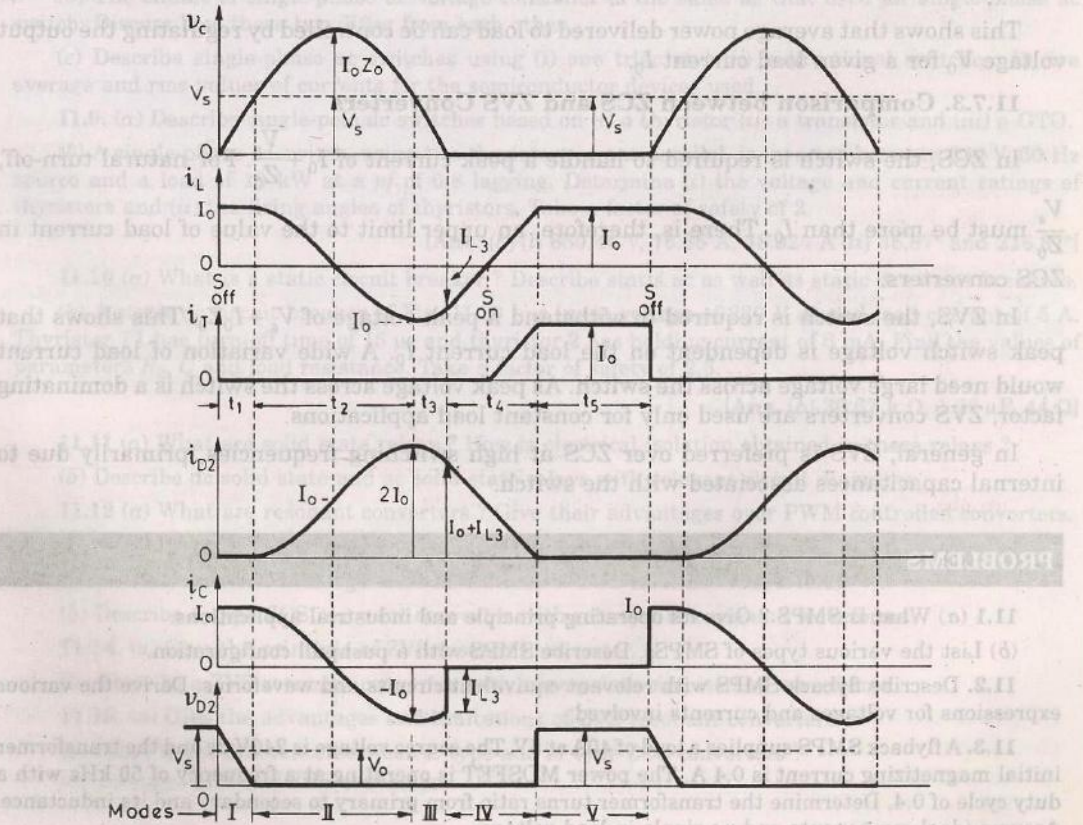


Fig. 11.32. Waveforms for ZVS resonant converter.

$$i_L = -I_{L3} + \frac{V_s}{L} t$$

At  $t = t_4$ ,  $i_L = I_0 = -I_{L3} + \frac{V_s}{L} t_4$ . This gives

$$t_4 = (I_0 + I_{L3}) \left( \frac{L}{V_s} \right) \quad \dots(11.27)$$

Diode current  $i_{D2} = I_0 + i_L$ . At  $t = 0$ ,  $i_{D2} = I_0 + I_{L3}$  and time  $t = t_4$ ,  $i_{D2} = 0$ . During modes II, III and IV, diode D2 is in conduction, therefore  $v_{D2} = 0$ , as shown in the waveforms of Fig. 11.32.

**Mode V ( $0 \leq t \leq t_5$ ).** At the end of mode IV, or in the beginning of mode V at  $t = 0$ ,  $i_L$  reaches  $I_0$  and therefore diode D2 turns off. Switch S continues conducting  $I_0$  as shown in Fig. 11.31(e). Note that voltage  $v_{D2} = V_s$  during this mode. Mode V ends at  $t = t_5$  when switch S is turned off again at zero voltage. The cycle now repeats as before.

The various waveforms for these five modes are now sketched in Fig. 11.32. It is seen from these waveforms that for a ZVS resonant converter :

- (i) switch, or inductor, current is limited to  $I_0$
- (ii) average value of output voltage  $V_0$  can be controlled by controlling the interval  $t_5$ .

This shows that average power delivered to load can be controlled by regulating the output voltage  $V_0$  for a given load current  $I_0$ .

### 11.7.3. Comparison between ZCS and ZVS Converters

In ZCS, the switch is required to handle a peak current of  $I_0 + \frac{V_s}{Z_0}$ . For natural turn-off,  $\frac{V_s}{Z_0}$  must be more than  $I_0$ . There is, therefore, an upper limit to the value of load current in ZCS converters.

In ZVS, the switch is required to withstand a peak voltage of  $V_s + I_0 Z_0$ . This shows that peak switch voltage is dependent on the load current  $I_0$ . A wide variation of load current would need large voltage across the switch. As peak voltage across the switch is a dominating factor, ZVS converters are used only for constant load applications.

In general, ZVS is preferred over ZCS at high switching frequencies, primarily due to internal capacitances associated with the switch.

## PROBLEMS

11.1 (a) What is SMPS ? Give its operating principle and industrial applications.

(b) List the various types of SMPSs. Describe SMPS with a pushpull configuration.

11.2. Describe flyback SMPS with relevant equivalent circuits and waveforms. Derive the various expressions for voltages and currents involved.

11.3. A flyback SMPS supplies a load of 40A at 5V. The source voltage is 240V dc and the transformer initial magnetizing current is 0.4 A. The power MOSFET is operating at a frequency of 50 kHz with a duty cycle of 0.4. Determine the transformer turns ratio from primary to secondary and its inductance. Assume ideal components and no ripple in load voltage.