

## SYNTHESIS OF NETWORKS

\* There are three types of passive elements

Viz. Inductor (L), capacitor (C) and Resistor (R).

\* Two methods are available to synthesis

1. Foster form and

2. Cauer form.

\* By using these two methods we can synthesize

1. LC Network

2. RL Network

3. RC Network

### 1. LC Network:

i) Properties of LC function:

1. Poles and Zeros must be simple. They must also lie on the imaginary axis ( $j\omega$  axis)

2. Poles and Zeros must be interlacing

3. There must be a pole or zero at the origin ( $\omega=0$ )

4. There must be a pole or zero at infinity ( $\omega \rightarrow \infty$ )

5. The slope of  $F(j\omega)$  versus  $\omega$  must be positive.

6. Residues of poles and Zeros on the imaginary axis must be real and positive


ii) Synthesize of LC network in Cauer form:

In Cauer method, there are two types of ladder network.

i<sup>st</sup> Cauer form: Series arm - Inductor  
Shunt arm - capacitor

ii<sup>nd</sup> Cauer form: Series arm - capacitor  
Shunt arm - Inductor

First Cauer form:

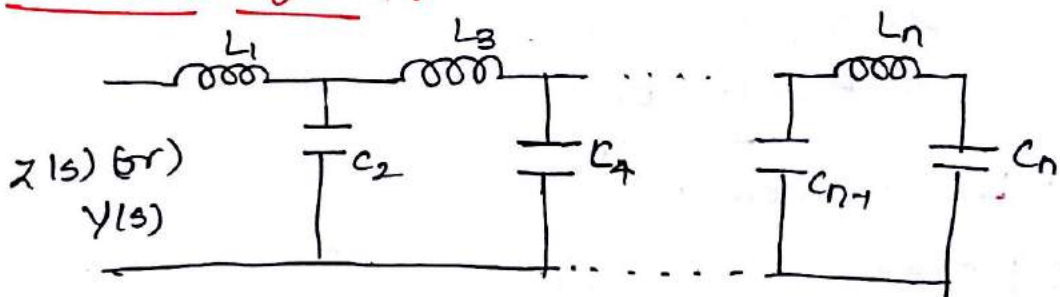

The continued fraction expansion is

$$Z(s) = L_1 s + \frac{1}{C_2 s + \frac{1}{L_3 s + \frac{1}{C_4 s + \dots}}}$$

\* polynomial having descending powers of  $s$

Condition for 1<sup>st</sup> Element and Last Element:

1<sup>st</sup> Element  $\Rightarrow$  At pole  $= \alpha$  ( $s = \alpha$ ) = series Inductor  
At Zero  $= \alpha$  ( $s = \alpha$ ) = shunt capacitor

Last Element  $\Rightarrow$  At pole  $= 0$  ( $s = 0$ ) = shunt capacitor  
At Zero  $= 0$  ( $s = 0$ ) = Series Inductor

1. find the cance I form of the network having

$$Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$$

Solution:

The given function has pole at  $s = \pm \sqrt{3}$  and zero at  $s = 0$ .  $\therefore$  Inductor is 1<sup>st</sup> & last element.

$$s^4 + 4s^2 + 3 \ ) \ 2s^5 + 12s^3 + 16s \quad (2s \rightarrow L_1 s)$$

$$\underline{2s^5 + 8s^3 + 6s}$$

$$4s^3 + 10s \ ) \ s^4 + 4s^2 + 3 \quad \left(\frac{s}{4} \rightarrow C_2 s\right)$$

$$\underline{s^4 + \frac{5}{2}s^2}$$

$$\frac{3}{2}s^2 + 3 \ ) \ 4s^3 + 10s \quad \left(\frac{8s}{3} \rightarrow L_3 s\right)$$

$$\underline{4s^3 + 8s}$$

$$2s \ ) \ \frac{3}{2}s^2 + 3 \quad \left(\frac{3s}{4} \rightarrow C_4 s\right)$$

$$\underline{\frac{3}{2}s^2}$$


$$3 \ ) \ 2s \quad \left(\frac{2s}{3} \rightarrow L_5 s\right)$$

$$\underline{2s}$$


$$\underline{0}$$
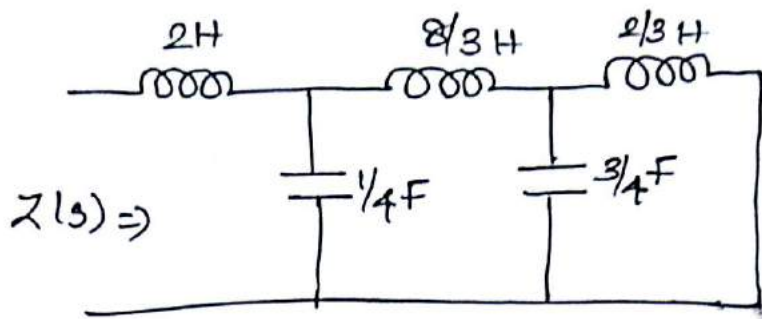
$$\therefore Z(s) = 2s + \frac{1}{\frac{s}{4} + \frac{1}{\frac{8s}{3} + \frac{1}{\frac{3s}{4} + \frac{1}{\frac{2s}{3}}}}}$$





Second Cause form:

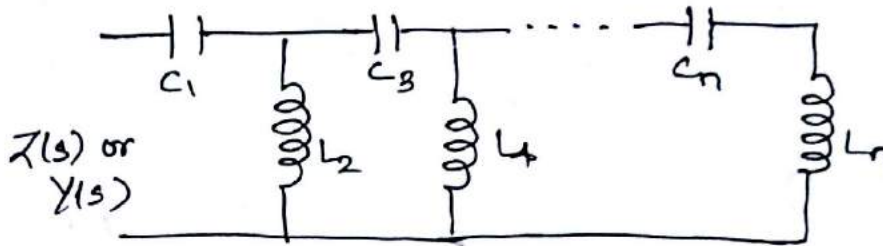

The continued fraction expansion is

$$Z(s) = \frac{1}{C_1 s} + \frac{1}{\frac{1}{L_2 s} + \frac{1}{\frac{1}{C_3 s} + \frac{1}{\frac{1}{L_4 s} + \dots}}}$$

\* polynomial having ascending powers of  $s$

Condition for 1<sup>st</sup> and Last Element:

1<sup>st</sup> Element  $\Rightarrow$  At pole  $= 0$  ( $s=0$ )  $\Rightarrow$  Series Capacitor  
 At zero  $= 0$  ( $s=0$ )  $\Rightarrow$  Shunt Inductance

Last Element  $\Rightarrow$  At pole  $= \infty$  ( $s=\infty$ )  $\Rightarrow$  Inductor  
 At zero  $= \infty$  ( $s=\infty$ )  $\Rightarrow$  Capacitor

\* Numerator power should be greater than the denominator power if not inverse  $Z(s)$ .

$$\therefore Y(s) = \frac{1}{Z(s)}$$

1. find the second cause form of the network

$$Z(s) = \frac{s^4 + 4s^2 + 3}{s^3 + 2s}$$

Solution:

$$Z(s) = \frac{3 + 4s^2 + s^4}{2s + s^3}$$

$$2s + s^3 \overline{) 3 + 4s^2 + s^4} \left( \frac{3}{2s} \rightarrow \frac{1}{C_1 s} \right)$$

$$3 + \frac{3}{2}s^2$$

$$\frac{5s^2 + s^4}{2} \overline{) 2s + s^3} \left( \frac{4}{5s} \rightarrow \frac{1}{L_2 s} \right)$$

$$2s + \frac{4s^3}{5}$$

$$\frac{3s^3}{5} \overline{) \frac{5}{2}s^2 + s^4} \left( \frac{25}{2s} \rightarrow \frac{1}{C_3 s} \right)$$

$$\frac{5}{2}s^2$$


$$s^4 \overline{) \frac{s^3}{5}} \left( \frac{1}{5s} \rightarrow \frac{1}{L_4 s} \right)$$

$$\frac{s^3}{5}$$

$$\underline{\quad\quad\quad}$$

$$0$$
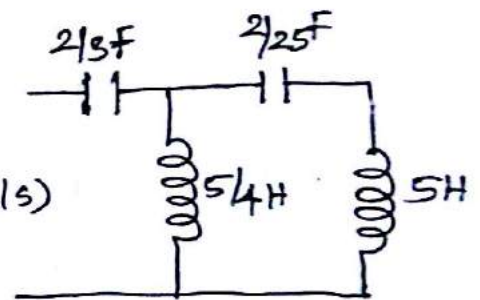
$$Z(s) = \frac{3}{2s} + \frac{1}{\frac{4}{5s} + \frac{1}{\frac{25}{2s} + \frac{1}{\frac{1}{5s}}}}$$




iii) Synthesize of LC network in Foster form:

Foster I Method:

The driving point impedance of a LC network is

$$Z(s) = Z_1(s) + Z_2(s) + \dots + Z_n(s)$$

The network is

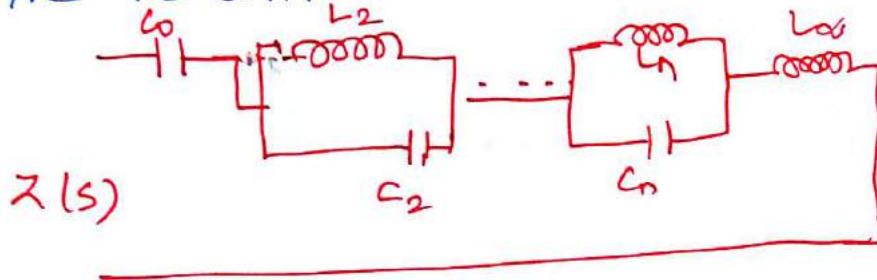

$$Z_1(s) = \frac{P_0}{sC_0} = \frac{P_0}{s} \text{ where } P_0 = \frac{1}{C_0}$$

$$Z_2(s) = L_2 s \parallel \frac{1}{C_2 s} = \frac{L_2 s \times \frac{1}{sC_2}}{L_2 s + \frac{1}{sC_2}}$$

$$= \frac{L_2 s}{s^2 C_2 L_2 + 1} = \frac{(L_2 s / C_2 L_2)}{s^2 + \frac{1}{C_2 L_2}}$$

$$Z_2(s) = \frac{(\frac{1}{C_2})s}{s^2 + \omega_n^2} = \frac{2P_n s}{s^2 + \omega_n^2}$$

where  $2P_n = \frac{1}{C_n}$  to  $\omega_n^2 = \frac{1}{C_n L_n}$  — ①

$$Z_n(s) = L_\infty = Hs$$

$$\therefore Z(s) = \frac{P_0}{s} + \frac{2P_n s}{s^2 + \omega_n^2} + Hs$$

from ①,

$$C_n = \frac{1}{2P_n}, \quad L_n = \frac{1}{C_n \omega_n^2}$$

$$C_0 = \frac{1}{P_0}, \quad L_\infty = H$$



\* If there is a pole at  $\omega=0$ , the first element  $C_0$  is present in the network.


\* If there is a pole at  $\omega=\alpha$ , the last element  $L_n$  is present in the network.

Foster II method:

The driving point admittance  $Y(s)$  of LC network is

$$Y(s) = Y_1(s) + Y_2(s) + \dots + Y_n(s)$$
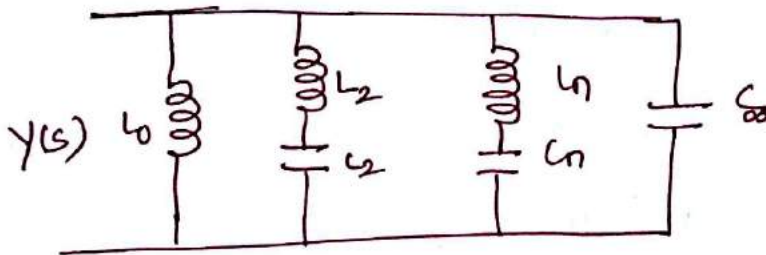
$$\therefore Y(s) = \frac{H}{s} \frac{(s^2 + \omega_1^2)(s^2 + \omega_3^2)}{(s^2 + \omega_2^2)(s^2 + \omega_4^2)}$$



$$Y_1(s) = \frac{1}{L_0 s} = \frac{P_0}{s} \text{ where } P_0 = \frac{1}{L_0}$$

$$Y_2(s) = \frac{1}{L_2 s + \frac{1}{s C_2}} = \frac{s C_2}{s^2 L_2 C_2 + 1}$$

$$Y_2(s) = \frac{(s/L_2)}{s^2 + \frac{1}{L_2 C_2}}$$

$$Y_n(s) = C_0 s = H s$$

$$Y(s) = \frac{P_0}{s} + \frac{2P_2s}{s^2 + \omega_2^2} + \frac{2P_4s}{s^2 + \omega_4^2} + \dots + Hs$$

$$Y(s) = \frac{P_0}{s} + \frac{2P_n s}{s^2 + \omega_n^2} + Hs$$

$$\therefore L_0 = \frac{1}{P_0}$$

$$C_\infty = H$$

$$P_n = \frac{1}{2L_n} \Rightarrow L_n = \frac{1}{2P_n}$$

$$C_n = \frac{2P_n}{\omega_n^2}$$

\* If there is a pole at  $\omega=0$ , the first element  $L_0$  is present in the network.

\* If there is a pole at  $\omega=\infty$ , the last element  $C_\infty$  is present in the network.



1. The driving point impedance of a LC network is given by

$$Z(s) = \frac{5(s^2+4)(s^2+25)}{s(s^2+16)}$$

obtain first and second Foster networks.

Solution:

numerator has higher power than the denominator.

First Foster form:

By partial fraction,

$$Z(s) = \frac{A}{s} + \frac{B}{(s+j4)} + \frac{B^*}{s-j4}$$

Apply Heaviside Method,

$$A = \left. \frac{5(s^2+4)(s^2+25)}{s(s^2+16)} \right|_{s=0} = \frac{500}{16} = \frac{125}{4}$$

$$B = \left. \frac{(s+j4) 5(s^2+4)(s^2+25)}{s(s+j4)(s-j4)} \right|_{s=-j4} = \frac{-20 \times 4 \times 25}{(-j4)(-8j)}$$

$$= \frac{20 \times 4 \times 25}{32} = \frac{135}{8}$$

$$B^* = \frac{135}{8}$$

$$\therefore Z(s) = \frac{(125/4)}{s} + \frac{2(135/8)s}{s^2+16} \quad \text{--- (1)}$$

By inspection,  $H=5$ .

$$Z(s) = \frac{P_0}{s} + \frac{2P_n s}{s^2 + \omega_n^2} + HS \quad \text{--- (2)}$$


By Comparing ① & ②

$$C_0 = \frac{1}{P_0} = \frac{1}{\left(\frac{125}{4}\right)} = \frac{4}{125} F$$

$$L_x = H = 5H$$

$$C_1 = \frac{1}{2P_1} = \frac{1}{2 \times \left(\frac{135}{8}\right)} = \frac{8}{2 \times 135} = \frac{8}{270} F$$
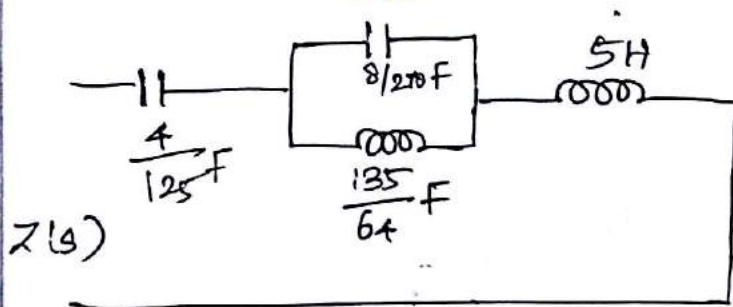
$$L_2 = \frac{1}{C_1 \omega_p^2} = \frac{1}{\frac{8}{270} \times 16} = \frac{270}{8 \times 16} = \frac{270}{128} = \frac{135}{64} H$$



Second Foster form:

$$Y(s) = \frac{3(s^2 + 16)}{5(s^2 + 4)(s^2 + 25)}$$

By partial fraction,

$$Y(s) = \frac{A}{s+2j} + \frac{A^*}{s-2j} + \frac{B}{s+5j} + \frac{B^*}{s-5j}$$

$$A = \frac{(s+2j) \cancel{3} (s^2 + 16)}{5 (s+2j) (s-2j) (s^2 + 25)} \Big|_{s=-2j}$$

$$= \frac{-\cancel{3} \times -10}{5 \times -1 \times -21} = \frac{6}{105} = \frac{2}{35}$$

$$B = \frac{(s+5j) \cancel{3} (s^2 + 16)}{5 (s^2 + 4) (s+5j) (s-5j)} \Big|_{s=-5j}$$

$$= \frac{-\cancel{3} \times -9}{5 \times -21 \times -10} = \frac{3}{70}$$

$$\therefore Y(s) = \frac{2\left(\frac{2}{35}\right)s}{s^2+4} + \frac{2\left(\frac{3}{70}\right)s}{s^2+25}$$

$$\therefore Y(s) = \frac{p_0}{s} + \frac{2p_2s}{s^2+\omega_2^2} + \dots + HS$$


$$C_0 = 0, \quad C_\infty = 0$$

$$L_1 = \frac{1}{2p_1} \Rightarrow \frac{1}{2 \times \frac{2}{35}} = \frac{35}{4} \text{ H}$$

$$C_1 = \frac{2p_1}{\omega_1^2} = \frac{2 \times 2}{35 \times 4} = \frac{1}{35} \text{ F}$$

$$L_2 = \frac{1}{2p_2} = \frac{70 \times 35}{2 \times 3} = \frac{35}{3} \text{ H}$$
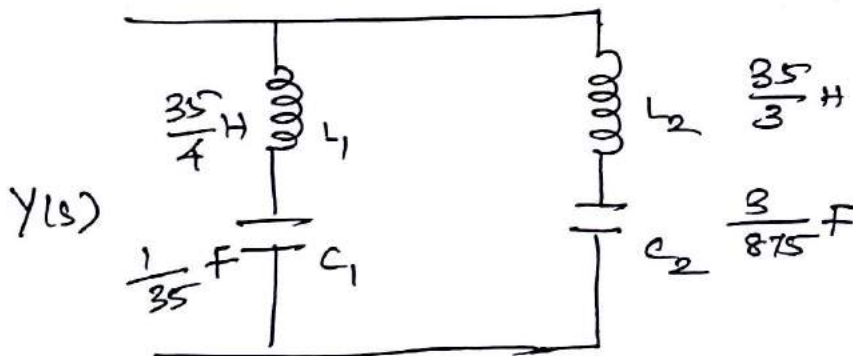
$$C_2 = \frac{2p_2}{\omega_2^2} = \frac{2 \times 3}{70 \times 25} = \frac{3}{875} \text{ F}$$





## RC Network:

i) Properties of RC function:

Impedance

1. poles and zeros are simple
2. poles and zeros are interlaced
3. There must a pole at the origin or near to the origin ( $s=0$ )
4. There must a zero at the origin infinity or near to the infinity ( $s=\infty$ )
5. The degree of the denominator can be equal to or greater than atmost by one than numerator
6. Residues of the poles of impedance function must be real and positive
7.  $Z_{RC}(0) > Z_{RC}(\infty)$

Admittance


- and lie on negative real axis of  $s$  plane
3. There must be a zero at the origin or near to the origin ( $s=0$ )
  4. There must be a pole at the infinity or near to the infinity ( $s=\infty$ )
  5. The degree of the numerator can be equal to or greater than atmost by one than the degree of the denominator.
  6. Residues of poles of admittance are real and negative.  $\frac{Y_{RC}(s)}{s}$  are real and positive
  7.  $Y_{RC}(0) \leq Y_{RC}(\infty)$

ii) Synthesize of RC network in canon form

First Canon form:

Series arm - Resistor

Shunt arm - capacitor

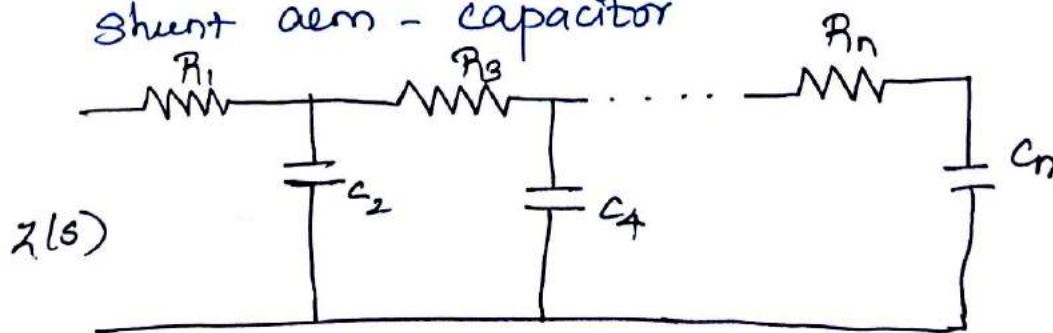



## Conditions for 1<sup>st</sup> and Last Element:

- \* If  $z(s)$  has a zero at  $s=\infty$ , 1<sup>st</sup> element is  $C_1$
- \* If  $z(s)$  is a constant at  $s=\infty$ , 1<sup>st</sup> element is  $R_1$
- \* If  $z(s)$  has a pole at  $s=0$ , last element is  $C_n$
- \* If  $z(s)$  is a constant at  $s=0$ , last element is  $R_n$

→ The continued fraction expansion for the first case form,

$$z(s) = R_1 + \frac{1}{C_2 s + 1} \frac{1}{R_3 + \frac{1}{C_4 s + \dots}}$$

1. find the first case form

$$z(s) = \frac{(s+2)(s+4)}{s(s+3)}$$

Solution:

$$z(0) = \frac{8}{0} = \infty$$

$$z(\infty) = \frac{s^2 \left(1 + \frac{2}{s}\right) \left(1 + \frac{4}{s}\right)}{s^2 \left(1 + \frac{3}{s}\right)} = 1$$

$$z(s) = \frac{s^2 + 6s + 8}{s^2 + 3s}$$

$$s^2 + 3s \Big) s^2 + 6s + 8 \quad (1)$$

$$\underline{s^2 + 3s}$$

$$3s + 8 \Big) s^2 + 3s \quad \left(\frac{s}{3}\right)$$

$$\underline{s^2 + \frac{8s}{3}}$$

$$\frac{s}{3} \Big) 3s + 8 \quad (9)$$


$$\underline{3s}$$

$$8 \Big) \frac{s}{3} \quad \left(\frac{s}{24}\right)$$

$$\underline{\frac{s}{3}}$$

$$0$$

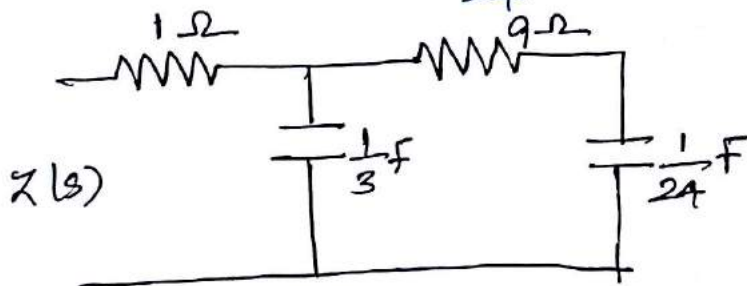
$$Z(s) = 1 + \frac{1}{\frac{s}{3} + \frac{1}{9 + \frac{1}{\frac{s}{24}}}}$$



### Second Cauer form:

series arm - capacitor

shunt arm - Resistor

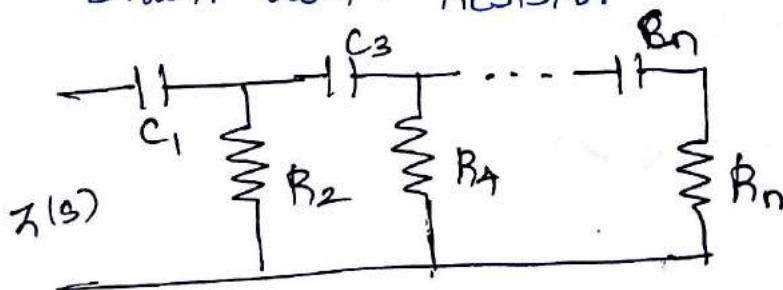

The continued fraction expansion is

$$z(s) = \frac{1}{C_1 s} + \frac{1}{R_2 + \frac{1}{\frac{1}{C_3 s} + \frac{1}{R_4 + \dots}}}$$

Condition for first and last Element:

- \* If  $z(s)$  has a pole at  $s=0$ , 1<sup>st</sup> element is  $C_1$ ,
- \* If  $z(s)$  has a constant at  $s=0$ , " "  $R_1$ ,
- \* If  $z(s)$  has a zero at  $s=\infty$ , last element is  $C_n$
- \* If  $z(s)$  has a constant at  $s=\infty$ , " "  $R_n$

1. find the second case form

$$z(s) = \frac{s^2 + 6s + 8}{s^2 + 3s}$$

Solution:

$$z(s) = \frac{8 + 6s + s^2}{3s + s^2}$$

$$z(0) = \frac{(s+2)(s+4)}{(s+0)(s+3)} = \frac{8}{0} = \infty$$

$$z(\infty) = \frac{s^2(1 + \frac{2}{s})(1 + \frac{4}{s})}{s^2(1 + \frac{0}{s})(1 + \frac{3}{s})} = 1$$

$$z(0) > z(\infty)$$

$$3s + s^2 \Big) 8 + 6s + 9^2 \left( \frac{8}{3s} \right)$$

$$8 + \frac{8s}{3}$$

$$\frac{10s}{3} + s^2 \Big) 3s + s^2 \left( \frac{9}{10} \right)$$

$$3s + \frac{9s^2}{10}$$

$$\frac{s^2}{10} \Big) \frac{10s}{3} + s^2 \left( \frac{100}{3s} \right)$$


$$\frac{10s}{3}$$

$$s^2 \Big) \frac{s^2}{10} \left( \frac{1}{10} \right)$$

$$\frac{s^2}{10}$$

$$\underline{\quad 0}$$
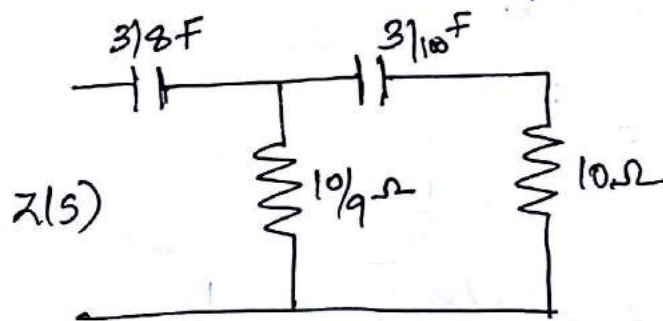
$$Z(s) = \frac{8}{3s} + \frac{1}{\frac{9}{10} + \frac{1}{\frac{100}{3s} + \frac{1}{10}}}$$





iii) Synthesize of RC Network By Foster Method:


Foster - 1 Form:

Properties of RL admittance is same for RC impedance also.

The driving point impedance of RC network is

$$Z(s) = \frac{H(s + \sigma_1)(s + \sigma_3) \dots}{S(s + \sigma_2)(s + \sigma_4) \dots}$$

The network is

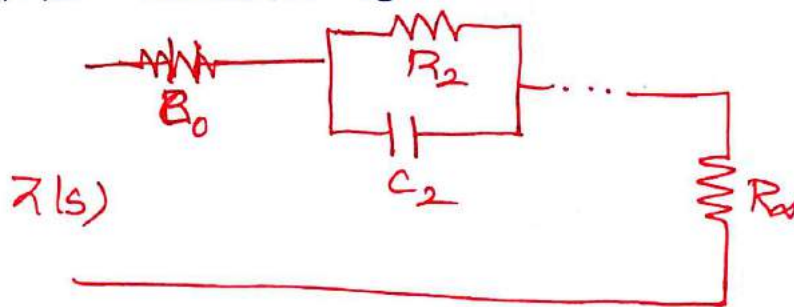

$$Z(s) = Z_1(s) + Z_2(s) + \dots + Z_n(s)$$

$$Z_1(s) = \frac{1}{sC_0} = \frac{P_0}{s} \quad \text{where } P_0 = \frac{1}{C_0}$$

$$\begin{aligned} Z_2(s) &= R_2 \parallel \frac{1}{sC_2} = \frac{R_2 \times \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{(R_2 \times \frac{1}{sC_2}) / sC_2}{R_2 sC_2 + 1} \\ &= \frac{R_2}{1 + sR_2C_2} = \frac{R_2/R_2C_2}{\frac{1}{R_2C_2} + s} = \frac{1/C_2}{s + \sigma_2} \end{aligned}$$

$$= \frac{P_n}{s + \sigma_n} \quad \text{where } P_n = \frac{1}{C_n} \quad \sigma_n = \frac{1}{R_n C_n}$$

$$Z_n(s) = H$$

$$Z(s) = \frac{P_0}{s} + \frac{P_n}{s + \sigma_n} + \dots + H$$

$$\therefore P_0 = \frac{1}{C_0} \Rightarrow C_0 = \frac{1}{P_0}$$

$$P_n = \frac{1}{C_n} \Rightarrow C_n = \frac{1}{P_n}$$

$$\sigma_n = \frac{1}{R_n C_n} \Rightarrow R_n = \frac{1}{\sigma_n C_n}$$

1. Find the first Foster form for the driving point function  $Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$

Solution:

By taking partial fraction,

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)} = \frac{s^2 + 4s + 3}{s^2 + 2s}$$

$$\begin{array}{r} s^2 + 2s \ ) \ s^2 + 4s + 3 \ (1 \\ \underline{s^2 + 2s} \phantom{+ 3} \\ 2s + 3 \end{array}$$

$$\therefore Z(s) = 1 + \frac{2s+3}{s^2+2s}$$

$$Z(s) = 1 + \frac{A}{s} + \frac{B}{s+2}$$

By Heavisides method,

$$A = s \cdot \frac{(2s+3)}{s(s+2)} \Big|_{s=0} = \frac{3}{2}$$

$$B = (s+2) \frac{(2s+3)}{s(s+2)} \Big|_{s=-2} = \frac{-1}{-2} = \frac{1}{2}$$


$$\therefore Z(s) = 1 + \frac{(3/2)}{s} + \frac{(1/2)}{s+2}$$

$$R_{\infty} = H = 1 \Omega$$

$$C_0 = \frac{1}{P_0} = \frac{1}{(3/2)} = \frac{2}{3} F$$

$$C_1 = \frac{1}{P_1} = \frac{1}{(1/2)} = 2 F$$
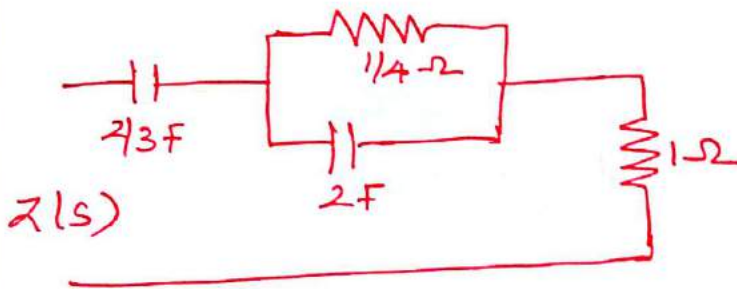
$$R_1 = \frac{1}{\sigma_1 C_1} \Rightarrow \frac{1}{2 \times 2} = \frac{1}{4} \Omega$$




Foster II form:

\* properties of RL impedance is same for RC admittance.

\* The driving point function of RC network  $Y(s)$  is given by

$$Y(s) = \frac{H (s + \sigma_1) (s + \sigma_3) \dots}{(s + \sigma_2) (s + \sigma_4) \dots}$$

The network is

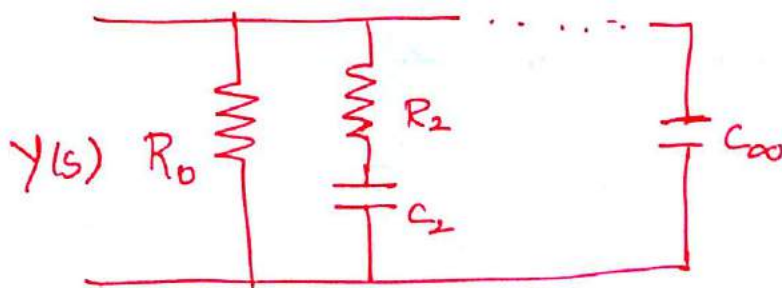

$$Y(s) = Y_1(s) + Y_2(s) + \dots + Y_n(s)$$

$$Y_1(s) = P_0 = \frac{1}{R_0}$$



$$Y_2(s) = \frac{1}{R_2 + \frac{1}{sC_2}} = \frac{sC_2}{sC_2R_2 + 1} = \frac{sC_2/R_2C_2}{s + \frac{1}{R_2C_2}}$$

$$= \frac{(\frac{1}{R_2})s}{s + \sigma_2} = \frac{P_n s}{s + \sigma_n}$$

where  $P_n = \frac{1}{R_n}$

$$\sigma_n = \frac{1}{R_n C_n}$$

$$Y_n(s) = C_\infty = Hs$$

$$Y(s) = P_0 + \frac{P_n s}{s + \sigma_n} + Hs$$

$$\therefore P_0 = \frac{1}{R_0} \Rightarrow R_0 = \frac{1}{P_0}$$

$$\therefore C_\infty = H$$

$$P_n = \frac{1}{R_n} \Rightarrow R_n = \frac{1}{P_n}$$

$$\sigma_n = \frac{1}{R_n C_n} \Rightarrow C_n = \frac{1}{\sigma_n R_n}$$

1. find the second foster form.

$$Y(s) = \frac{s(s+2)}{(s+1)(s+3)}$$

Solution:

$$Y(s) = \frac{s^2 + 2s}{s^2 + 4s + 3}$$

$$\begin{array}{r} s^2 + 4s + 3 \overline{) s^2 + 2s} \quad (1) \\ \underline{s^2 + 4s + 3} \\ -2s - 3 \end{array}$$

$$Y(s) = 1 + \frac{(-2s-3)}{s^2 + 4s + 3}$$



Taking partial fraction,

$$= 1 + \frac{A}{s+1} + \frac{B}{s+3}$$

Using Heavisides Method,

$$A = (s+1) \frac{\cancel{s+1}(-2s-3)}{(s+1)(s+3)} \Big|_{s=-1} = \frac{-1}{2}$$

$$B = (s+3) \frac{(-2s-3)}{(s+1)\cancel{(s+3)}} \Big|_{s=-3} = \frac{-3}{2}$$

$$Y(s) = 1 - \frac{(1/2)}{s+1} - \frac{(3/2)}{s+3}$$

Since residues are negative, we have to expand

$\frac{Y(s)}{s}$  as follows,

$$\frac{Y(s)}{s} = \frac{\cancel{s}(s+2)}{\cancel{s}(s+1)(s+3)} = \frac{s+2}{(s+1)(s+3)}$$

$$= \frac{A}{s+1} + \frac{B}{s+3}$$

using Heavisides Method,

$$A = (s+1) \frac{\cancel{(s+1)}(s+2)}{(s+1)(s+3)} \Big|_{s=-1} = \frac{1}{2}$$

$$B = (s+3) \frac{(s+2)}{(s+1)\cancel{(s+3)}} \Big|_{s=-3} = \frac{1}{2}$$

$$\frac{Y(s)}{s} = \frac{(1/2)}{s+1} + \frac{(1/2)}{s+3}$$

$$Y(s) = \frac{(1/2)s}{s+1} + \frac{(1/2)s}{s+3}$$

The element values are


$$P_0 = 0, \quad C_0 = 0$$

$$\frac{P_0 s}{s + \sigma_0} = \frac{(1/2)s}{s+1} \Rightarrow P_0 = 1/2 \Rightarrow R_0 = \frac{1}{P_0} = 2 \Omega$$

$$C_1 = \frac{1}{\sigma_1 R_1} = \frac{1}{1 \times 2} = \frac{1}{2} \text{ F}$$

$$\frac{P_2 s}{s + \sigma_2} = \frac{(1/2)s}{s+3} \Rightarrow P_2 = 1/2 \Rightarrow R_2 = \frac{1}{P_2} = 2 \Omega$$
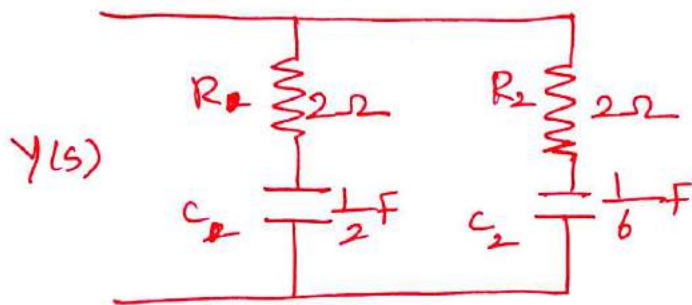
$$C_2 = \frac{1}{\sigma_2 R_2} = \frac{1}{3 \times 2} = \frac{1}{6} \text{ F}$$



### 3. RL Network:

i) Properties of RL function:

a) Properties of RL Impedance is same as the properties of RC Admittance


b) Properties of RL Admittance is same as the properties of RC Impedance.

ii) Synthesize of RL network in Cauer form:

First Cauer form:

Series arm - Inductor

Shunt arm - Resistor

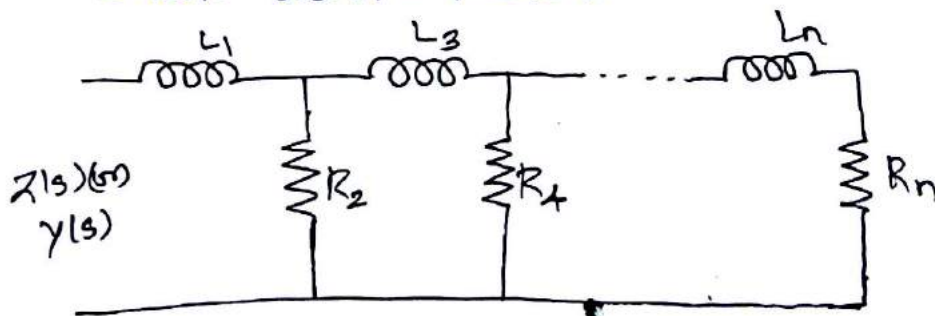



The continued fraction expansion is

$$z(s) = sL_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{sL_3 + \frac{1}{R_4 + \dots}}}$$

Condition for 1<sup>st</sup> and Last Element:

- \* If  $z(s)$  has a pole at  $s = \infty$ , 1<sup>st</sup> element is  $L_1$
- \* If  $z(s)$  is a constant at  $s = \infty$ , " "  $R_1$
- \* If  $z(s)$  has a zero at  $s = 0$ , last element is  $L_n$
- \* If  $z(s)$  is a constant at  $s = 0$ , " "  $R_n$

1) find first cause form

$$z(s) = \frac{(s+4)(s+8)}{(s+2)(s+6)}$$

Solution:

$$z(0) = \frac{32}{12} = 2.67$$

$$z(\infty) = \frac{s^2(1+\frac{4}{s})(1+\frac{8}{s})}{s^2(1+\frac{2}{s})(1+\frac{6}{s})} = 1$$

$$z(0) > z(\infty)$$

$$(s^2 + 8s + 12) \overline{s^2 + 12s + 32} \left( \frac{1}{s^2 + 8s + 12} \right)$$


$$4s + 20 \overline{s^2 + 8s + 12} \left( \frac{s}{4} \right)$$

$$3s + 12 \overline{4s + 20} \left( \frac{4}{3} \right)$$


$$4 \overline{3s + 12} \left( \frac{3s}{4} \right)$$

$$12 \overline{4} \left( \frac{1}{3} \right)$$
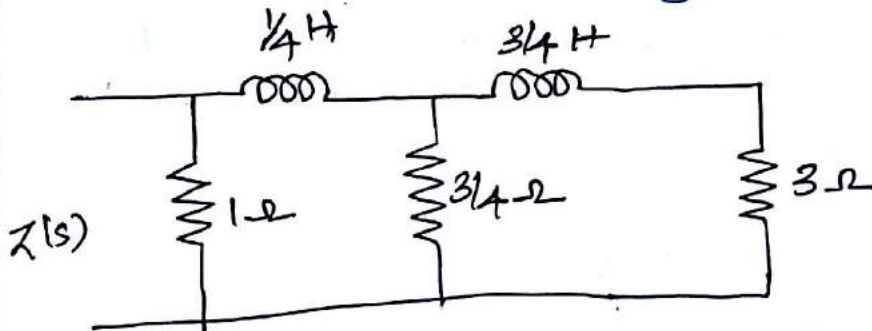
$$Z(s) = \frac{1}{1 + \frac{3}{4} + \frac{1}{\frac{4}{3} + \frac{1}{\frac{3s}{4} + \frac{1}{3}}}}$$



Second Canonical form:

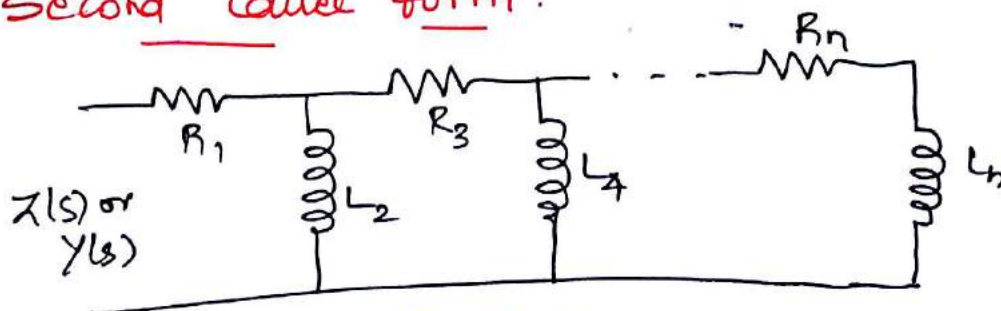

Series elem - Resistor  
Shunt elem - Inductor

The continued fraction expansion is

$$Z(s) = R_1 + \frac{1}{sL_2 + \frac{1}{R_3 + \frac{1}{sL_4 + \frac{1}{R_5 + \dots}}}}$$

Condition for 1<sup>st</sup> and last element:

\* If  $Z(s)$  has a zero at  $s=0$ , 1<sup>st</sup> element is  $L_1$

\* If  $Z(s)$  is a constant at  $s=0$ , " "  $R_1$

\* If  $Z(s)$  has a pole at  $s=\infty$ , last element is  $L_n$

\* If  $Z(s)$  is a constant at  $s=\infty$ , " "  $R_n$

1. Find the second canonical form

$$Z(s) = \frac{2s^2 + 8s + 6}{s^2 + 8s + 12}$$

Solution:

$$Z(0) = \frac{6}{12} = 0.5$$

$$Z(\infty) = \frac{(s+1)(s+3)}{(s+2)(s+6)} = \frac{s^2(1+\frac{1}{s})(1+\frac{3}{s})}{s^2(1+\frac{2}{s})(1+\frac{6}{s})} = 1$$

$$Z(0) < Z(\infty)$$



$$12 + 8s + s^2 \Big) \frac{6 + 8s + 2s^2}{2} \left( \frac{1}{2} \right)$$

$$\underline{6 + 4s + \frac{s^2}{2}}$$

$$4s + \frac{3s^2}{2} \Big) \frac{12 + 8s + s^2}{3} \left( \frac{3}{3} \right)$$

$$\underline{12 + \frac{9}{2}s}$$

$$\frac{7}{2}s + s^2 \Big) \frac{4s + \frac{3s^2}{2}}{7} \left( \frac{8}{7} \right)$$

$$\underline{4s + \frac{8s^2}{7}}$$

$$\frac{5}{14}s^2 \Big) \frac{\frac{7}{2}s + s^2}{53} \left( \frac{49}{53} \right)$$


$$\underline{\frac{7}{2}s}$$

$$s^2 \Big) \frac{\frac{5}{14}s^2}{14} \left( \frac{5}{14} \right)$$

$$\underline{\frac{5}{14}s^2}$$

$$\underline{\quad 0}$$
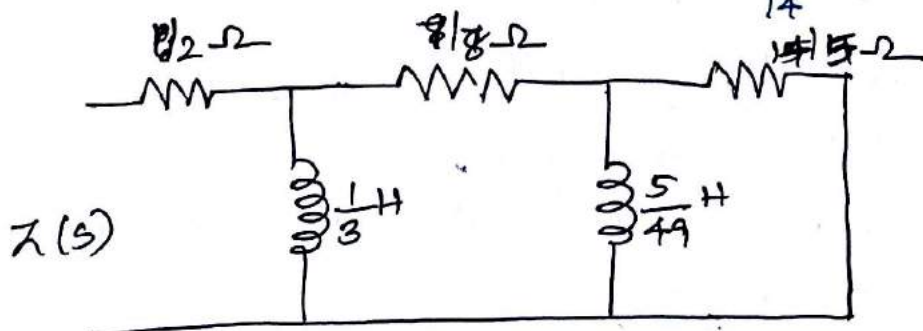
$$Z(s) = \frac{1}{2} + \frac{1}{\frac{3}{3} + \frac{1}{\frac{8}{7} + \frac{1}{\frac{49}{53} + \frac{1}{\frac{5}{14}}}}}$$




iii) Synthesize of RL network by the Foster form:

Foster -1 form:

The driving point impedance function of RL network is given by
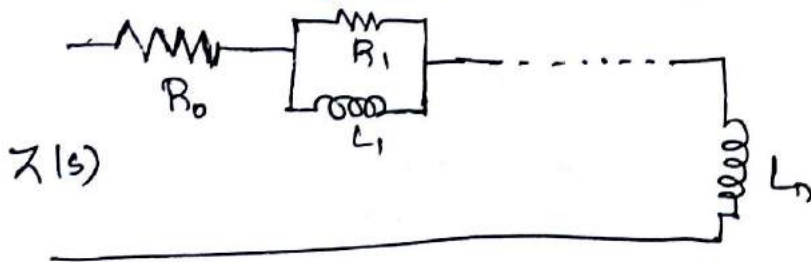
$$Z(s) = \frac{H (s + \sigma_1) (s + \sigma_3) \dots}{(s + \sigma_2) (s + \sigma_4) \dots}$$



Expression for parallel combination of \$R\_1\$ & \$L\_1\$,

$$Z_2(s) = R_1 \parallel L_1 s = \frac{R_1 \times s L_1}{R_1 + s L_1}$$

$$\div \text{ by } L_1 \Rightarrow Z_1(s) = \frac{R_1 s}{\frac{R_1}{L_1} + s} = \frac{R_1 s}{s + \sigma_1} \quad \text{--- (1)}$$

$$\text{where } \sigma_1 = \frac{R_1}{L_1}$$

$$\frac{Z_1(s)}{s} = \frac{R_1}{s + \sigma_1}$$

\$Z(s)\$ can be expressed as

$$Z(s) = \frac{a_0 s^n + a_1 s^{n-1} + \dots + a_n}{b_0 s^m + b_1 s^{m-1} + \dots + b_m} \quad \text{where } n > m \quad \text{--- (2)}$$

The degree of numerator is greater than that of the denominator by one.

By separating the constant term and linear terms in eq (2), the RL impedance function can be written as

$$Z(s) = P_0 + \frac{P_i s}{s + \sigma_i} + \dots + Hs \quad \text{--- (3)}$$

If we divide the total impedance into a series of impedance  $Z_1(s), Z_2(s), \dots, Z_n(s)$

$$Z(s) = Z_1(s) + Z_2(s) + \dots + Z_n(s) \quad \text{--- (4)}$$

Comparing eq (3) to (4)

$Z_1(s) = P_0$ , a constant represents resistor

$Z_n(s) = Hs$  represents inductor  $L_\alpha$

The remaining terms represent parallel combination of an inductor and a resistor

$$\begin{aligned} P_n &= R_n \\ \sigma_n &= \frac{R_n}{L_n} \\ R_0 &= P_0 \\ L_\alpha &= Hs \end{aligned}$$

1. find first foster form for the function

$$Z(s) = \frac{5(s+1)(s+4)}{(s+3)(s+5)}$$

Solution:

$Z(s)$  represents RL impedance because it satisfies all the properties.

By partial fraction expansion,

$$\begin{aligned} \frac{5(s+1)(s+4)}{(s+3)(s+5)} &= \frac{5s^2 + 25s + 20}{s^2 + 8s + 15} \\ &= 5 + \frac{(-15s - 55)}{s^2 + 8s + 15} \end{aligned}$$

$$\begin{array}{r} (s^2 + 8s + 15) \frac{5s^2 + 25s + 20}{s^2 + 8s + 15} \\ \hline 5s^2 + 40s + 75 \\ \hline -15s - 55 \end{array}$$



$$\frac{-15s - 55}{s^2 + 8s + 15} = \frac{A}{s+3} + \frac{B}{s+5}$$

$$A = \frac{(s+5)(-15s-55)}{(s+3)(s+5)} \Big|_{s=-3} = \frac{45-55}{2}$$

$$\boxed{A = -5}$$

$$B = \frac{(s+3)(-15s-55)}{(s+3)(s+5)} \Big|_{s=-5} = \frac{75-55}{-2}$$

$$\boxed{B = -10}$$

$$\therefore Z(s) = 5 - \frac{5}{s+3} - \frac{10}{s+5}$$

$Z(s)$  has negative residues, so  $\frac{Z(s)}{s}$

$$\frac{Z(s)}{s} = \frac{5(s+1)(s+4)}{s(s+3)(s+5)}$$

$$= \frac{A}{s} + \frac{B}{s+3} + \frac{C}{s+5}$$

Apply Heavisides method,

$$A = \frac{5(s+1)(s+4)}{s(s+3)(s+5)} \Big|_{s=0} = \frac{20}{15} = \frac{4}{3}$$

$$B = \frac{(s+5)5(s+1)(s+4)}{s(s+3)(s+5)} \Big|_{s=-3} = \frac{-20}{-6} = \frac{5}{3}$$

$$C = \frac{(s+3)5(s+1)(s+4)}{s(s+3)(s+5)} \Big|_{s=-5} = \frac{-20}{-10} = 2$$

$$\therefore \frac{Z(s)}{s} = \frac{4}{3s} + \frac{5}{3(s+3)} + \frac{2}{s+5}$$

$$Z(s) = \frac{4}{3} + \frac{5s}{3(s+3)} + \frac{2s}{s+5}$$

$$Z(s) = p_0 + \frac{p_1 s}{s+\sigma_1} + \frac{p_2 s}{s+\sigma_2}$$


$$P_0 = \frac{4}{3} \Omega = R_0$$

$$P_1 = \frac{5}{3} \Omega = R_1$$

$$\sigma_1 = 3 \Rightarrow L_1 = \frac{R_1}{\sigma_1} = \frac{5}{3 \times 3} = \frac{5}{9} \text{ H}$$

$$P_2 = 2 \Omega = R_2$$
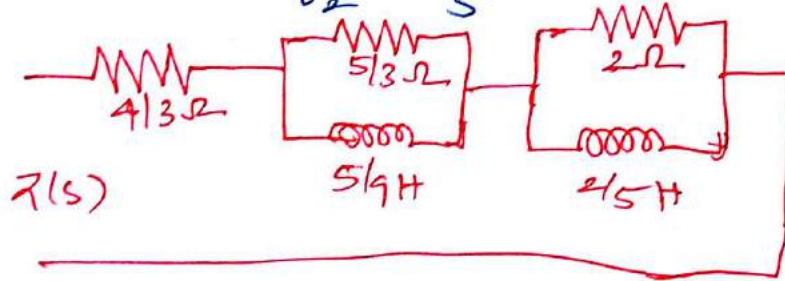
$$\sigma_2 = 5 \Rightarrow L_2 = \frac{R_2}{\sigma_2} = \frac{2}{5} \text{ H}$$




Foster II Form:

The driving point admittance function of the RL network  $Y(s)$  is given by

$$Y(s) = \frac{b_0 s^m + b_1 s^{m-1} + \dots + b_m}{a_0 s^n + a_1 s^{n-1} + \dots + a_n}$$
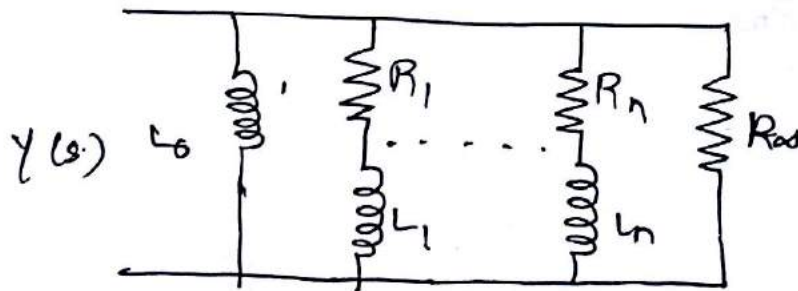
$$= \frac{H (s + \sigma_1) (s + \sigma_2) \dots}{s (s + \sigma_3) (s + \sigma_4) \dots} \quad \text{--- (1)}$$



The RL admittance function can be written as,

$$Y(s) = \frac{P_0}{s} + \frac{P_i}{s + \sigma_i} + \dots + H \quad \text{--- (2)}$$

Series combination of RL Network is

$$Y_1(s) = \cancel{R_1 + \frac{1}{sL_1}} \frac{1}{R_1 + sL_1} \quad - (3)$$

Compare (2) & (3)

$$R_n = \frac{\sigma_n}{P_n}$$

$$L_n = \frac{1}{P_n}$$

$$Y(s) = Y_1(s) + Y_2(s) + \dots + Y_n(s)$$

$$Y_1(s) = \frac{P_0}{s} \text{ represents inductor } L_0, L_0 = \frac{1}{P_0}$$

$$Y_n(s) = H \text{ represents resistor } R_n, R_n = H$$

$$\begin{aligned} L_0 &= \frac{1}{P_0} \\ R_n &= H \\ R_n &= \frac{\sigma_n}{P_n} \\ L_n &= \frac{1}{P_n} \end{aligned}$$

1. Find the second foster form of admittance function.  $Y(s) = \frac{2s^2 + 16s + 30}{s^2 + 6s + 8}$

Solution:

$Y(s)$  satisfies all the properties

Apply partial fraction,

$$\begin{aligned} Y(s) &= \frac{2s^2 + 16s + 30}{s^2 + 6s + 8} \\ &= 2 + \frac{4s + 14}{s^2 + 6s + 8} \end{aligned}$$

$$\begin{aligned} (s^2 + 6s + 8) \frac{2s^2 + 16s + 30}{s^2 + 6s + 8} &= \frac{2s^2 + 16s + 30}{s^2 + 6s + 8} \\ &= \frac{4s + 14}{s^2 + 6s + 8} \end{aligned}$$



$$Y(s) = 2 + \frac{A}{s+2} + \frac{B}{s+4}$$

using Heaviside Method,

$$A = (s+2) \frac{4s+14}{(s+2)(s+4)} \Big|_{s=-2} = 3$$

$$B = (s+4) \frac{4s+14}{(s+2)(s+4)} \Big|_{s=-4} = 1$$

The residues are positive. Hence

$$Y(s) = 2 + \frac{3}{s+2} + \frac{1}{s+4}$$

$$\therefore Y(s) = \frac{P_0}{s} + \frac{P_1}{s+\sigma_1} + \frac{P_2}{s+\sigma_2}$$

$$R_{\infty} = H = 2 \Omega$$

$$P_1 = 3, \sigma_1 = 2 \Rightarrow R_1 = \frac{\sigma_1}{P_1} = \frac{2}{3} \Omega$$

$$L_1 = \frac{1}{P_1} = \frac{1}{3} H$$

$$P_2 = 1, \sigma_2 = 4 \Rightarrow R_2 = \frac{\sigma_2}{P_2} = 4 \Omega$$

$$L_2 = \frac{1}{P_2} = 1 H$$

The RL network's second Foster form is

