

Problem -2**Given Data****Motor Rating**


$$V=200 \text{ Volts}$$

$$N = 1500 \text{ rpm}$$

$$I_a = 10 \text{ A}$$

$$R_a = 10 \Omega$$
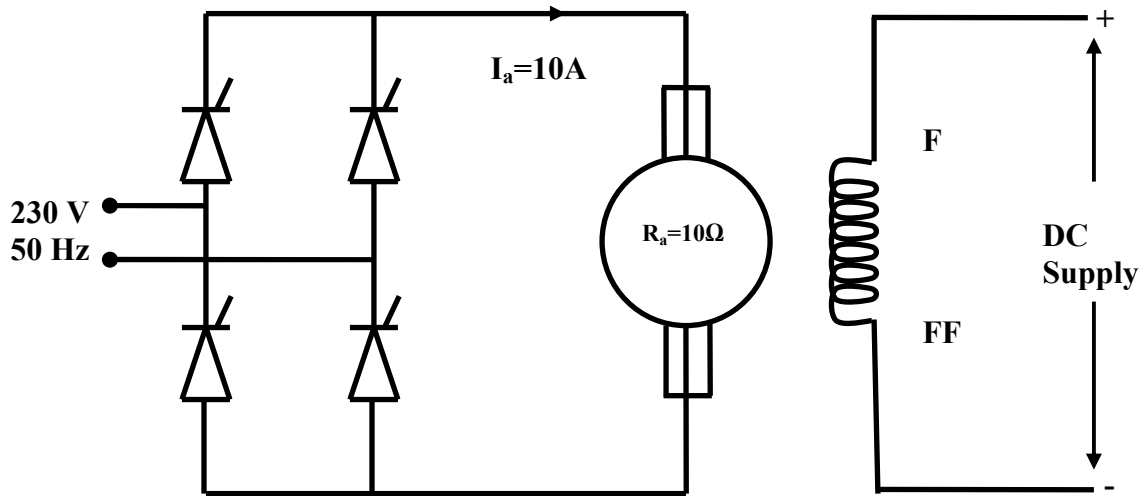
$$\text{Source Voltage } V_s = 230 \text{ volts}$$



Under operating Conditions of separately excited DC motor

$$V_a = E_b + I_a R_a$$

$$V_a = K_b \phi \omega_m + I_a R_a$$

$$\text{Let } K_b \phi = K_m$$

$$\therefore V_a = K_m \omega_m + I_a R_a$$

$$220 = K_m \left[\frac{2\pi \times 1500}{60} \right] + (10 \times 10)$$

$$K_m = K_b \phi = 0.7639 \text{ Volts Seconds/Radians}$$

i. For a torque of 5 Nm, motor armature current is

$$T = K_m I_a$$

$$I_a = \frac{T}{K_m} = \frac{5}{0.7639} = 6.545 \text{ A}$$

The equation giving the operation of converter motor is

$$V_a = E_b + I_a R_a = \frac{2V_m}{\pi} \cos \alpha$$

$$\frac{2V_m}{\pi} \cos \alpha = K_m \omega_m + I_a R_a$$

$$\frac{2 \times \sqrt{2} \times 230}{\pi} \cos \alpha = K_m \omega_m + I_a R_a$$

$$\frac{2 \times \sqrt{2} \times 230}{\pi} \cos 30^\circ = 0.7639 \times \omega_m + 6.545 \times 10$$

$$179.33 = 0.7639 \times \omega_m + 65.45$$

$$\omega_m = 149.07 \text{ rad / sec}$$

$$\text{Motor Speed in RPM} = N = \frac{149.07 \times 60}{2\pi}$$

$$\boxed{N = 1423.58 \text{ rpm}}$$

ii. For $\alpha = 45^\circ$

$$\frac{2V_m}{\pi} \cos \alpha = K_m \omega_m + I_a R_a$$

$$\frac{2 \times \sqrt{2} \times 230}{\pi} \cos \alpha = 0.7639 \times \frac{2\pi \times 1000}{60} + (I_a \times 10)$$

$$146.4 = 79.99 + 10I_a$$

$$\boxed{I_a = 6.641 \text{ Amps}}$$

Motor developed torque

$$T = K_m I_a = 0.7639 \times 6.641$$

$$\boxed{T = 5.07 \text{ Nm}}$$

Problem 3

The input current to the motor at rated conditions

$$= \frac{10 \times 10^3}{0.87} = 11.494 \times 10^3 \text{ W}$$

The supply current to the motor is

$$= \frac{11.494 \times 10^3}{240} = 47.89 \text{ A}$$

Neglecting the field copper loss the armature current = 47.89A

The back EMF at the rated conditions is

$$= 240 - 47.89 \times 0.4 = 220.843 \text{ Volts}$$

At $\alpha = 0$, the converter voltage is

$$V_a = \frac{2V_m}{\pi} \cos \alpha = \frac{2 \times \sqrt{2} \times 250}{\pi} \cos 0^\circ = 225 \text{ Volts}$$

As the load torque is constant the armature current is same. Therefore the back EMF is

$$= 225 - 47.89 \times 0.4 = 200.844 \text{ Volts}$$

We know that

$$E_b = K\omega$$

$$\omega = \frac{1000 \times 2\pi}{60} = 104.719 \text{ rad / sec}$$

$$\therefore K = \frac{E_b}{\omega} = \frac{220.844}{104.719} = 2.11 \text{ Volts.sec / rad}$$

At $\alpha = 0^\circ$

$$\text{Speed} = \frac{E_b}{K} = \frac{200.844}{2.108} = 95.235 \text{ rad / sec}$$

$$N = \frac{95.235 \times 60}{2\pi} = 909.43 \text{ RPM}$$

Displacement factor $DF = \cos \phi = \cos 0^\circ = 1$

Power Factor $PF = \frac{2 \times \sqrt{2}}{\pi} \cos \alpha = \frac{2 \times \sqrt{2}}{\pi} \cos 0^\circ = 0.9$

Input $= 225 \times 47.89 = 10775.25 \text{ W}$

Output varies linearly with speed

$$\therefore \text{output at } 909.4 \text{ rpm} = 10 \text{ kW}_{(\text{rated})} \times \frac{909.4}{1000} = 9.094 \text{ KW}$$

$$\therefore \eta = \frac{O/P}{i/p} = \frac{9.094}{10.7752} = 84.4\%$$

At $\alpha = 60$, the converter voltage is

$$V_a = \frac{2V_m}{\pi} \cos \alpha = \frac{2 \times \sqrt{2} \times 250}{\pi} \cos 60^\circ = 112.5 \text{ Volts}$$

As the load torque is constant the armature current is same. Therefore the back EMF is

$$= 112.5 - 47.89 \times 0.4 = 93.344 \text{ Volts}$$

We know that

$$E_b = K\omega$$

$$\omega = \frac{1000 \times 2\pi}{60} = 104.719 \text{ rad / sec}$$

$$\therefore K = \frac{E_b}{\omega} = \frac{220.844}{104.719} = 2.11 \text{ Volts.sec / rad}$$

At $\alpha = 60^\circ$

$$\text{Speed} = \frac{E_b}{K} = \frac{93.344}{2.108} = 44.28 \text{ rad / sec}$$

$$N = \frac{44.28 \times 60}{2\pi} = 422.8 \text{ RPM}$$

Displacement factor $DF = \cos \phi = \cos 60^\circ = 0.5$

Power Factor $PF = \frac{2x\sqrt{2}}{\pi} \cos \alpha = \frac{2x\sqrt{2}}{\pi} \cos 60^\circ = 0.45$

Input $= 112.5 \times 47.89 = 5.387 \text{ KW}$

Output varies linearly with speed

$$\therefore \text{output at } 909.4 \text{ rpm} = 10 \text{kw}_{(\text{rated})} \times \frac{422.8}{1000} = 4.227 \text{ KW}$$

$$\therefore \eta = \frac{O/P}{i/p} = \frac{4.227}{5.387} = 78.46\%$$

Problem 4

At rated Conditions

$$E_{b1} = V - I_a R_a = 200 - 150 \times 0.06 = 191 \text{ Volts}$$

$$N_1 = 875 \text{ rpm}$$

$$\omega_1 = \frac{875 \times 2\pi}{60} = 91.629 \text{ rad / sec}$$

We know that

$$E_{b1} = K\omega_1$$

$$\therefore K = \frac{191}{91.629} = 2.08 \text{volts. sec/ rad}$$

I. E_{b2} at 750 rpm

$$\omega_2 = \frac{750 \times 2\pi}{60} = 78.54 \text{rad / sec}$$

$$\therefore E_{b2} = 2.08 \times 78.54 = 163.37 \text{volts}$$

$$\therefore V_a = E_{b2} + I_a R_a = 163.37 + (150 \times 0.06) = 172.7 \text{Volts}$$

We know that

$$V_a = \frac{2V_m}{\pi} \cos \alpha$$

$$172.7 = \frac{2 \times \sqrt{2} \times 220}{\pi} \cos \alpha$$

$$\alpha = 29.3^\circ$$

II. At $\alpha = 160^\circ$ N=? at rated torque

$$V_a = \frac{2V_m}{\pi} \cos \alpha = \frac{2 \times \sqrt{2} \times 220}{\pi} \cos 160^\circ = -186.12 \text{Volts}$$

We know that $V_a = E_b + I_a R_a$

$$-186.12 = E_b + (150 \times 0.06)$$

$$E_b = -195.12 \text{Volts}$$

$$\therefore \omega = \frac{-195.12}{2.08} = -93.81$$

$$N = \frac{-93.81 \times 60}{2\pi} = -895.79 \text{rpm}$$

Problem 5

For 3 phase controlled rectifier the average output voltage is given by

$$V_a = \frac{3V_m}{\pi} \cos \alpha$$

Given that $V_a = 220$ Volts

$$\therefore 220 = \frac{3V_m}{\pi} \cos 0^\circ$$

$$\Rightarrow V_m = 230.4 \text{Volts}$$

At 1500 rpm

$$E_{b1} = V_a - I_a R_a = 220 - (10 \times 0.5) = 215 \text{ volts}$$

We know that

$$\therefore E_{b1} = K \omega_1$$

$$\omega_1 = \frac{1500 \times 2\pi}{60} = 157.08$$

$$K = \frac{215}{157.08} = 1.37 \text{ volt.sec/rad}$$

At 1200 rpm

$$\therefore E_{b2} = K \omega_2$$

$$\omega_2 = \frac{1200 \times 2\pi}{60} = 125.66 \text{ rad/sec}$$

$$K = 1.37 \text{ volt.sec/rad}$$

$$E_{b2} = 1.37 \times 125.66 = 172.2 \text{ Volts}$$

Average output voltage is

$$V_a = E_{b2} + I_a R_a = 172.2 + (10 \times 0.5) = 177 \text{ Volts}$$

$$\therefore V_a = \frac{3V_m}{\pi} \cos \alpha$$

$$\Rightarrow \cos \alpha = \frac{V_a \pi}{3V_m} = \frac{177 \times \pi}{3 \times 230.4} = 0.8$$

$$\Rightarrow \alpha = 36.4^\circ$$

At -800 rpm, $\alpha = ?$ $T = 2 \times I_{\text{rated}}$

$$\omega = \frac{-800 \times 2\pi}{60} = -83.77 \text{ rad/sec}$$

$$\therefore E_b = 1.37 \times -83.77 = -114.77 \text{ volts}$$

$$\text{Current} = 2 \times \text{Rated} = 20 \text{ A}$$

$$\therefore V_a = E_b + I_a R_a = -114.77 + (20 \times 0.5) = -104.77 \text{ Volts}$$

$$V_a = \frac{3V_m}{\pi} \cos \alpha$$

$$-104.77 = \frac{3 \times 230.4}{\pi} \times \cos \alpha$$

$$\cos \alpha = \frac{-104.67 \times \pi}{3 \times 230.4} = -0.475$$

$$\Rightarrow \alpha = 118.4^\circ$$